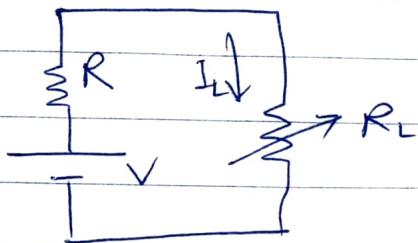


Maximum Power Transfer Theorem



Consider a ckt. with SC vting same V and resistance $R \Omega$ connected to variable load resistance R_L .

Load current ~~can~~ can be calculated here as,

$$I_L = \frac{V}{R + R_L}$$

The power consumed by the load resistance R_L is,

$$\begin{aligned} P &= I_L^2 R_L \\ &= \left(\frac{V}{R + R_L} \right)^2 \cdot R_L \end{aligned}$$

If R_L is changed, I_L will also change and at a particular value of R_L , the power transferred to the load will be max.

Hence the power depends on the value of R_L . To get the ~~max~~ value of R_L at which power will be max, let's differentiate above eqn of power w.r.t. R_L . & equate to zero.

$$\therefore \frac{dP}{dR_L} = 0$$

$$\therefore \frac{d}{dR_L} \left[\frac{V}{R+R_L} \right]^2 \cdot R_L = 0$$

$$\therefore \frac{d}{dR_L} \left[\frac{R_L}{(R+R_L)^2} \right] = 0$$

;


After solving this, we get,

$$R + R_L - 2R_L = 0$$

$$\therefore \boxed{R_L = R}$$

Thus when load resistance is equal to ~~internal~~ resis. of the ckt; max power transfer takes place.

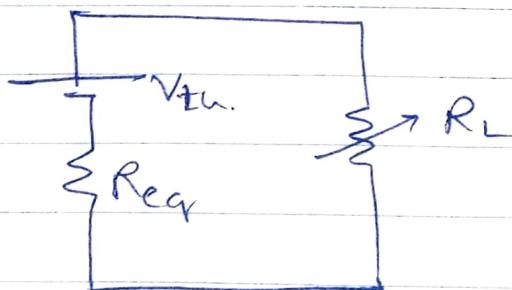We represent the complex n/w with Thvenin's equi. ckt



If we compare ~~to~~ this ckt. with above drawn ckt., we get;

$$R_L = R_{eq}$$

For max. power transfer.

And max. power will be calculated as,

$$P_m = \left[\frac{V_{th}}{R_{eq} + R_L} \right]^2 \cdot R_L$$


With $R_L = R_{th}$,

$$P_m = \left[\frac{V_{th}}{2 R_{eq}} \right]^2 \cdot R_{eq}$$

$$P_m = \frac{V_{th}^2}{4 R_{eq}}$$

Watts.

Example.

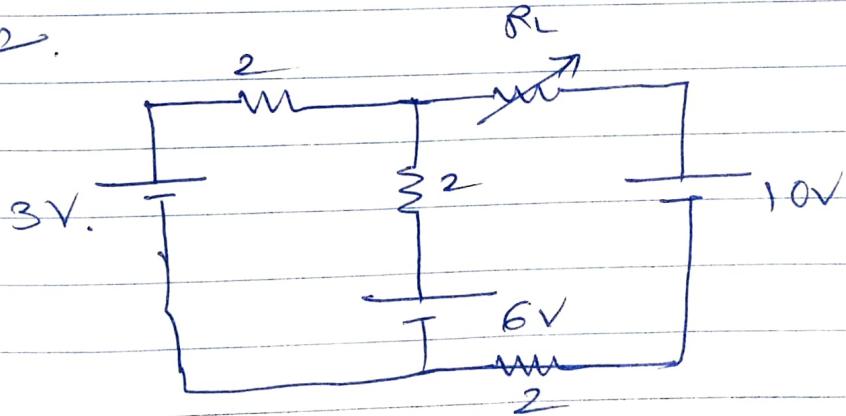

$$V_{th} = 5.5V$$

$$R_{eq} = 3\Omega$$


$$P_m = 2.5208W$$

Norton's Theorem

This theorem is an alternative to the Thévenin's theorem. Actually, it is the dual of Thévenin's ~~theorem~~ theorem. Norton's theorem replaces the network by an equivalent current source and a parallel resistance.

The Norton's theorem can be stated as, "Any two-terminal active network containing voltage sources and ~~series~~ resistances, when viewed from its output terminals, is equivalent to the constant current source and a parallel resistance. The constant current source is equal to the current which would flow in a short circuit placed across the terminals; and the parallel resistance is the resistance of the network when viewed from these open circuited terminals after all voltage & current sources have been removed and replaced by their ~~short~~ internal resistance."

Norton's equivalent circuit is,

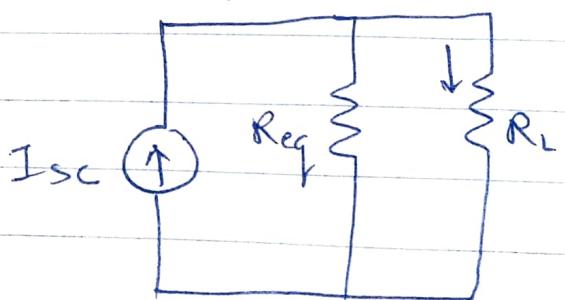

$$\therefore I_L = I_{ss} \times \frac{R_L}{R_{eq} + R_L}$$


Steps:

1. Remove R_L and short circuit the terminals.
 2. Calculate current through short circuit (I_{sc})
 3. Remove s.c., replace sources and calculate R_{eq} as done in Thvenin's theorem.
 4. Draw the ~~or~~ Nortni's equivalent circuit with I_{sc} & R_{eq} parallel with each other.
 5. Connect R_L in parallel with the equi. ckt.
 6. Calculate I_L using formula,
- $$I_L = I_{sc} \times \frac{R_{eq}}{R_{eq} + R_L} \text{ A.}$$


Example:



calculate current in AB using Nortni's.

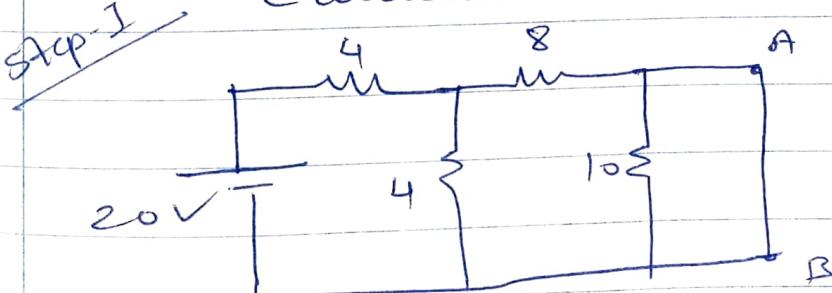

Now 10 ohm has become redundant.

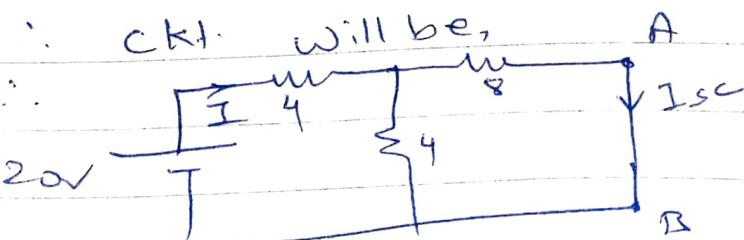


$$\therefore (8114) + 4 = \frac{32}{12} + 4 = 6.667 \text{ or}$$

$$\therefore I = \frac{20}{6.667} = 3 \text{ A}$$

$$\therefore I_{sc} = I \times \frac{4}{4+8}$$

$$= 3 \times \frac{4}{12} = 1 \text{ A}$$

~~Step II~~ To calculate R_{eq} ,

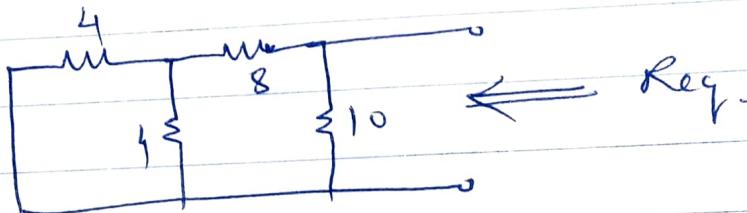


$$(4114) = 2$$

$$2 + 8 = 10$$

$$(101110) = 5 = R_{eq}$$



~~Step III~~ Equivalent circuit is,

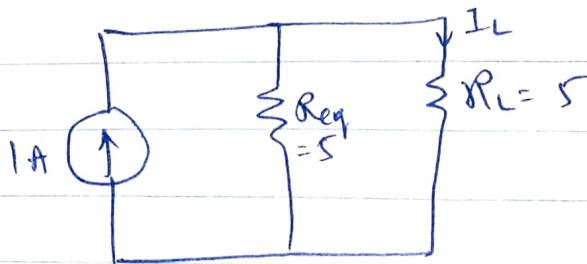

$$\therefore I_L = 1 \times \frac{5}{5+5}$$

$$= \underline{\underline{0.5 \text{ A}}}$$

2.

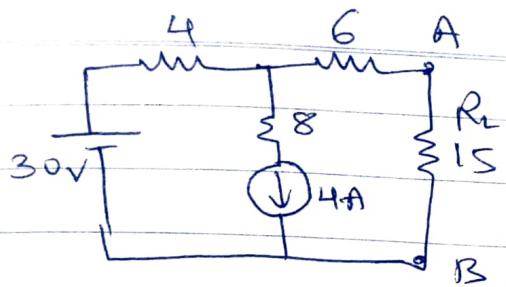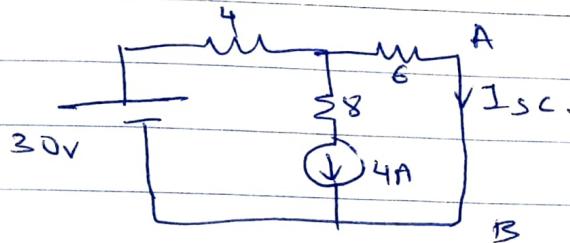
 Calculate current in 15Ω


Step I * Calculate I_{sc} by using superposition

- I_{sc}' with current source only.


$$I_{sc}' = 4 \times \frac{4}{10} = 1.6 \text{ A } \uparrow$$

- I_{sc}'' with voltage source only

$$I_{sc}'' = \frac{30}{10} = 3 \text{ A } \downarrow$$


$$\therefore I_{sc} = I_{sc}'' - I_{sc}' = 3 - 1.6 = 1.4 \text{ A}$$

Step II To calculate R_{eq} ,




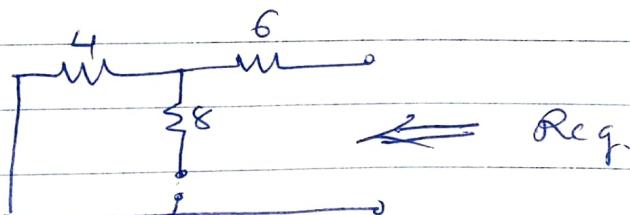


$$\therefore R_{eq} = 4 + 6 = 10 \Omega$$


Step III Equi. ckt.


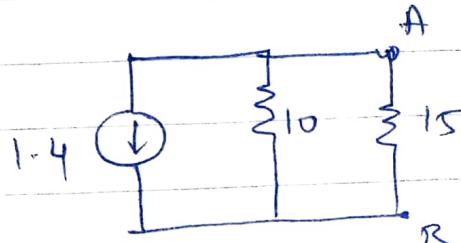

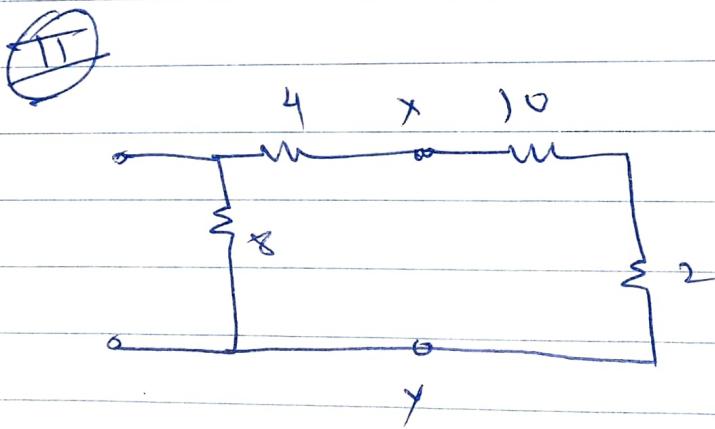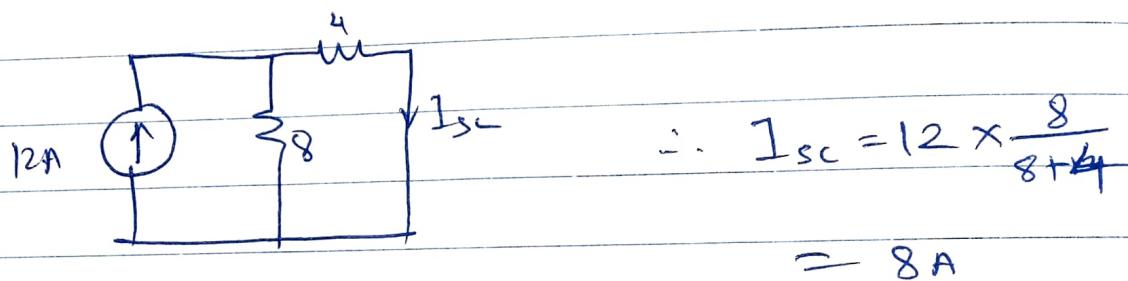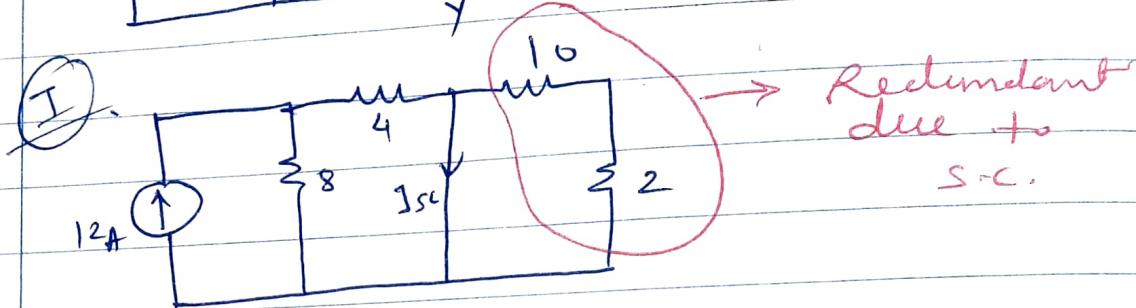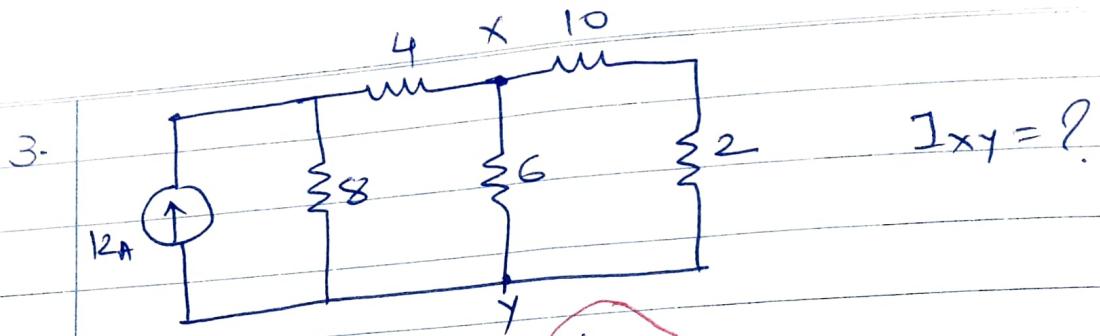
$$I_L = 1.4 \times \frac{10}{25} = 0.56 \text{ A}$$



Equi. ckt

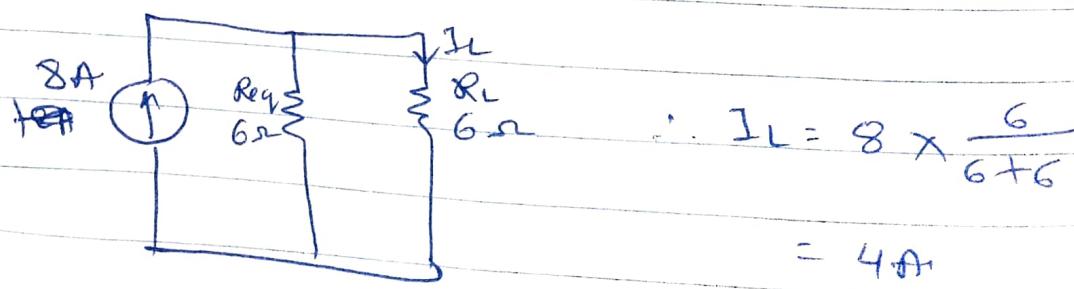


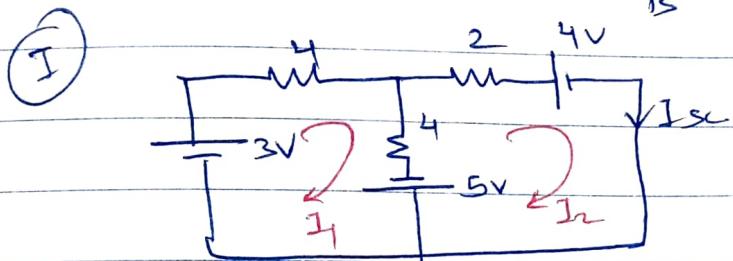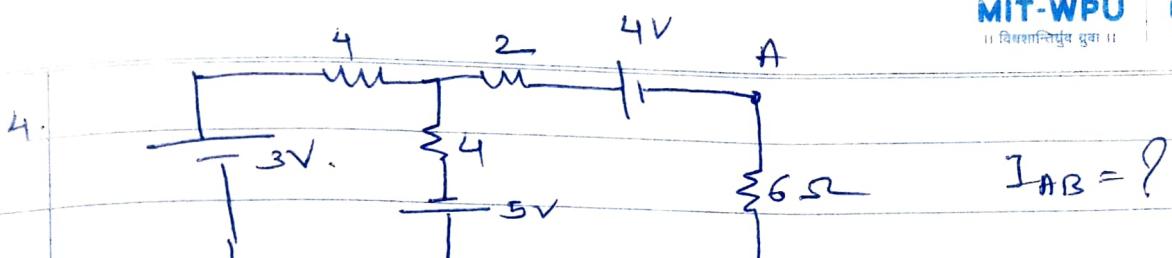

$$3 - 4I_1 - 4(I_1 - I_2) + 5 = 0$$


$$-2I_2 - 4 - 5 - 4(I_2 - I_1) = 0$$

$$\therefore I_2 = -5/4 \text{ A}$$

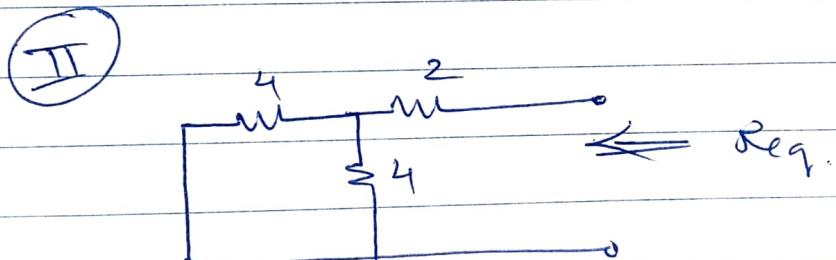

$$R_{eq.} = (4 \parallel 4) + 2 = 4 \Omega$$

Equi. ckt

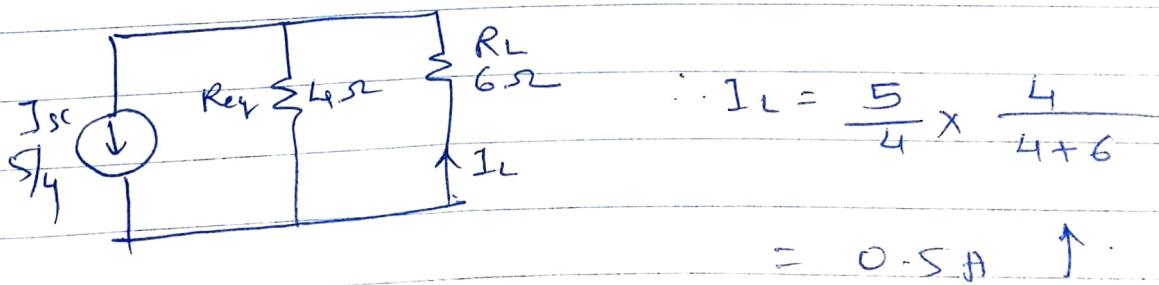


Millman's Theorem

This theorem can be stated either in terms of voltage sources or current sources or both.

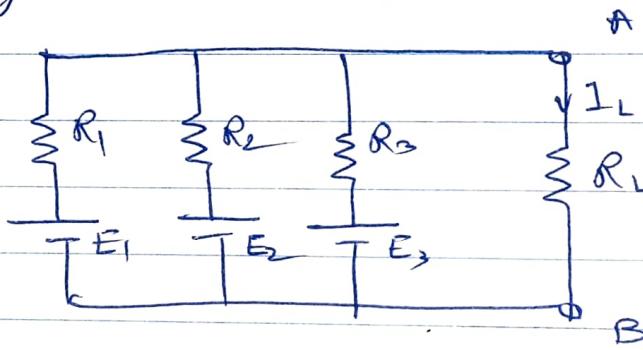a) As applicable to voltage sources:-

This theorem is a combination of Thévenin's & Norton's theorems. It is used for finding common voltage across any o/p which contains a no. of parallel voltage sources as shown below:-



The common voltage V_{AB} which appears across the o/p terminals A & B is affected by the voltage sources E_1 , E_2 and E_3 . The value of the voltage is given by,

$$V_{AB} = \frac{E_1/R_1 + E_2/R_2 + E_3/R_3}{1/R_1 + 1/R_2 + 1/R_3}$$
$$= \frac{I_1 + I_2 + I_3}{G_1 + G_2 + G_3} = \frac{\sum I}{\sum G}$$

This voltage V_{AB} represents the Thévenin


Voltage V_{th} :

The resistance R_{th} or R_{eq} can be calculated as usual, by replacing each v.tg. source by a s.c.. If there is a load resistance R_L across terminal A & B, the load current I_L is given by,

$$I_L = \frac{V_{th}}{R_{eq} + R_L}$$

* if a branch does not contain a v.tg.-source, then the v.tg.-is equated to zero.

Example.

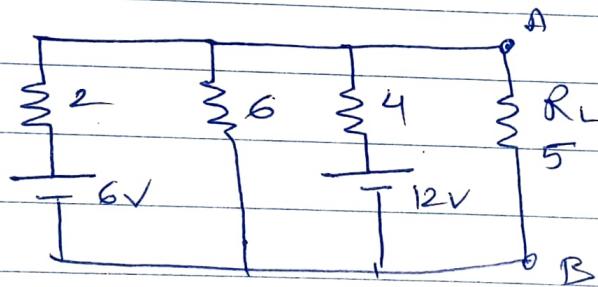

$$V_{AB} = \frac{6/2 + 0/6 + 12/4}{1/2 + 1/6 + 1/4} = 6.55V = V_{th}$$


$$R_{th} = 2/11 6/11 4 = 12/11 \Omega$$

$$\therefore I_L = \frac{6.55}{(12/11) + 5} = 1.07 A..$$

b) As applicable to current sources


This theorem is applicable to a mixture of parallel voltage & current sources that are reduced to a single final equivalent source which is either a constant current or a constant voltage source. The theorem can be stated as, "Any no. of constant current sources which are directly connected in parallel can be converted into a single current source whose value is algebraic sum of the individual source currents and whose total internal resistance equals the combined individual source resistances in parallel."

Ex:

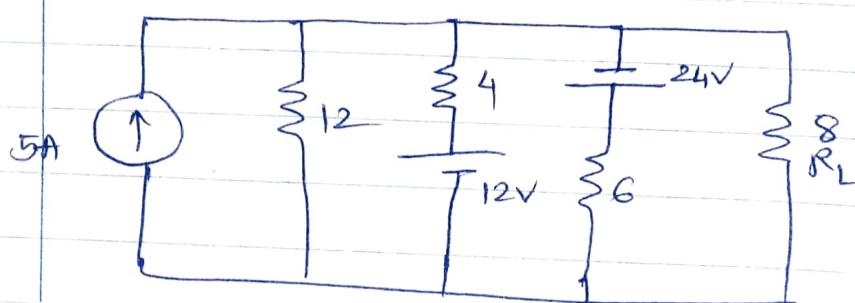

Calculate voltage across & current in R_L


Converting
current sources

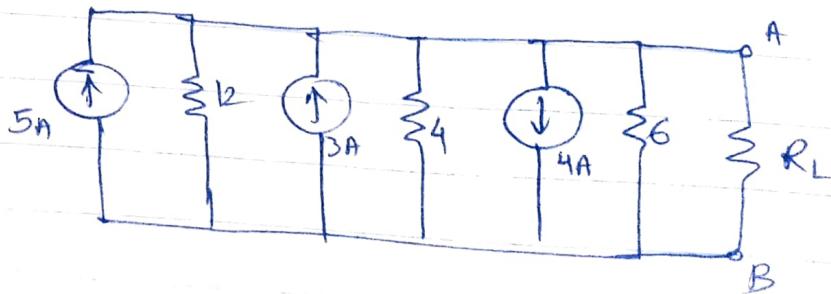

$$\therefore \text{Net Current} = 5 + 3 - 4 = 4 \text{ A} \uparrow$$

$$\text{Combined resis.} = 12 || 4 || 6 = 2 \Omega$$


\therefore Simplified circuit is,

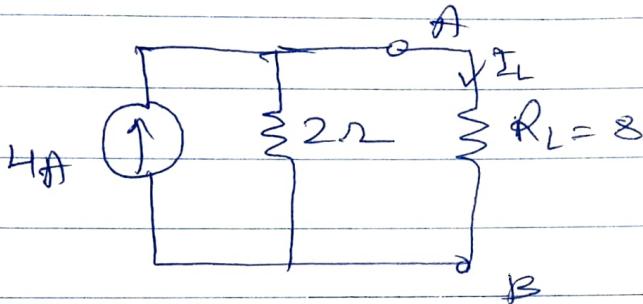

$$\therefore I_L = 4 \times \frac{2}{2+8} = 0.8 \text{ A}$$


$$V_L = 8 \times 0.8 = 6.4 \text{ V}$$

OR convert it into v-tg. form

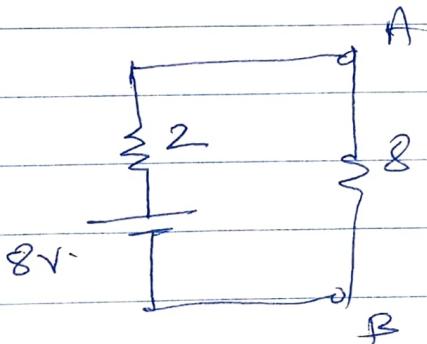

$$I = \frac{8}{2+8} = 0.8 \text{ A}$$

Generalized form of Millman's theorem

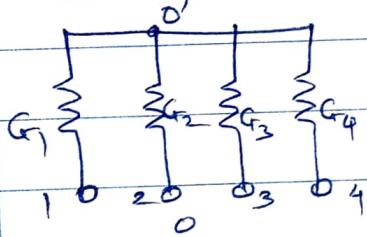


Consider no. of admittances $G_1, G_2, G_3, \dots, G_n$ terminate at common point O' . The other ends of admittances are named as $1, 2, 3, \dots, n$.

Let O be any other point in the network. Acc. to this theorem, the vltg. drop from O to O' ($V_{OO'}$) is given by,

$$V_{OO'} = \frac{V_{O_1}G_1 + V_{O_2}G_2 + V_{O_3}G_3 + \dots + V_{On}G_n}{G_1 + G_2 + G_3 + \dots + G_n}$$

* Note:- Only those resistances or admittances are taken into consideration which terminate at the common point. All those admittances are ignored which do not terminate at the common point even though they are connected in the circuit.

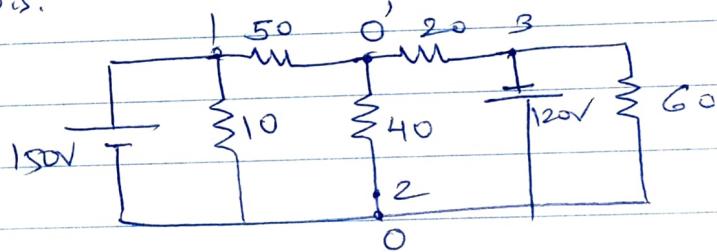Ex. calculate v_{tg}. developed across 40Ω resis.



Let two ends of 40Ω resistor be marked as O & O'.

The end points of the three resistors terminating at the common point O' have been marked 1, 2, and 3.

- 10Ω & 60Ω resistors will not come in calculation because they are not directly connected to common point O'.


$$\text{Here voltage } V_{O1} = -150V$$

$$V_{O2} = 0V$$

$$V_{O3} = 120V.$$

$$\therefore V_{OO'} = \frac{(-150/50) + (0/40) + (120/20)}{Y_{50} + Y_{40} + Y_{20}}$$

$$= 31.6V.$$

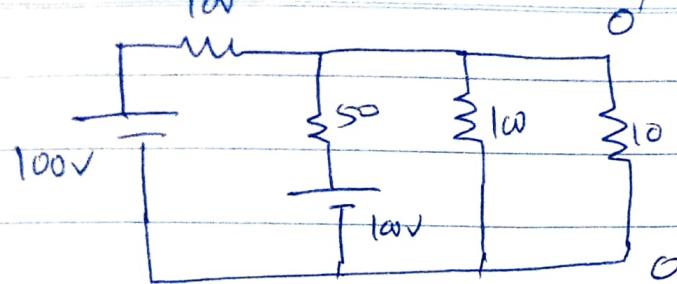


$$V_{O1} = -10V, \quad V_{O2} = -10V, \quad V_{O3} = 0, \quad V_{O4} = 0$$

$$\therefore V_{O0'} = \frac{(-10/10) + (-10/50) + (0/100) + (0/10)}{(Y_{100} + Y_{50} + Y_{10} + Y_{10})}$$


$$= -21.4$$

Method - II.

Use source conversion

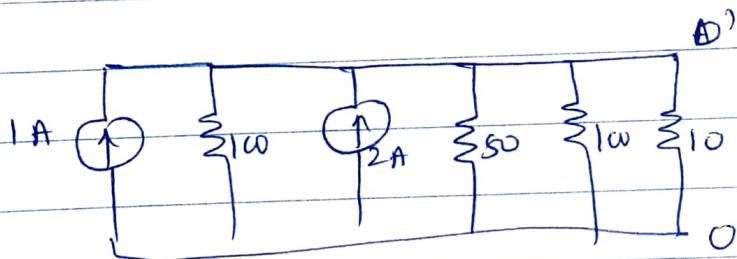

$$10\Omega || 50\Omega || 10\Omega = 25\Omega$$

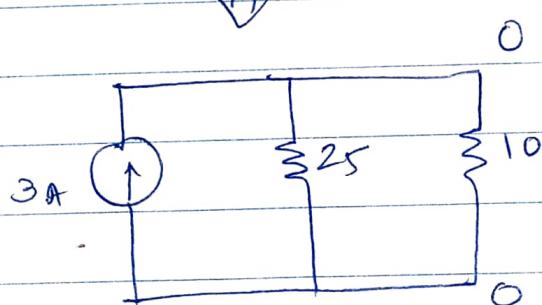

$$I_L = 3 \times \frac{25}{35} = 2.1428 \text{ A.}$$

$$\therefore V_{O1} = 10 \times 2.1428 = 21.4 \text{ V.}$$