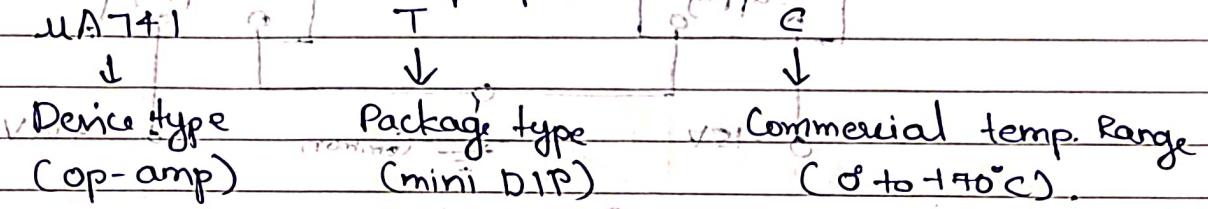


ADIC

Unit - 1

i) Ordering information: Generally in ordering IC following info must be specified.



Temp. Ranges:

- 1. Military: -55°C to +125°C
- 2. Industrial: -40°C to +85°C
- 3. Commercial: 0°C to +70°C

ii) Manufacturer's Designation for Linear ICs:

Manufac.	Prefix
Fairchild	FA, MAF
National Semiconductor	LM, LH, LF, TBA
Motorola	MC, MRC
RCA	CA, CD
Texas Instruments	SN
Signetics	N/S, NE, SE, SU
Burr-Brown	BB

741 - Military grade op-amp

741C - Commercial "

741A - Improved version of 741

741E - Improved " of 741C

741S - Military grade op-amp with higher slew rate

741SC - Commercial grade op-amp with higher slew rate.

Practical Fundamentals of Electronics

Date _____
Page _____

ii) Power Supply Connections:


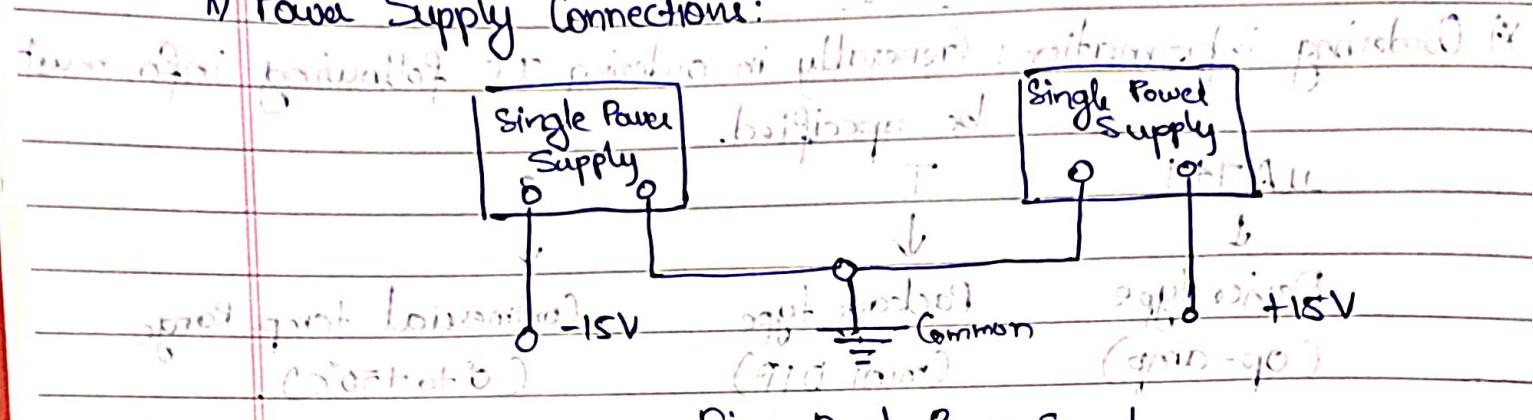


Fig: Dual Power Supply

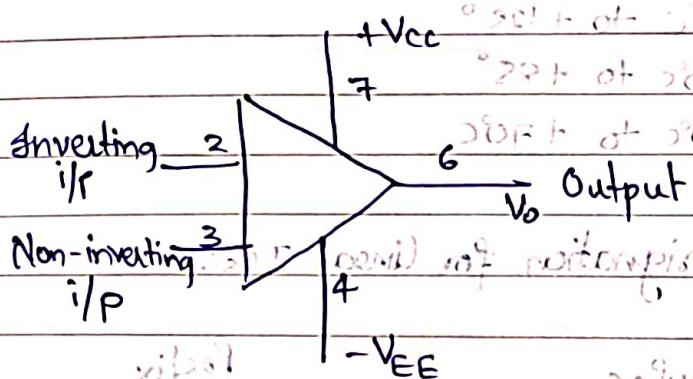


9. In. Op-Amp's schematic symbol.

ABT 11.11.1988 8-pin mini-DIP IC op-amp


$$I_E = I_C = \frac{N_{BE} - V_{BE}}{2R_E + R_S/R_{DC}}$$

$$I_E = I_C = \frac{N_{BE} - V_{BE}}{2R_E}$$


ii) Output offset voltage:

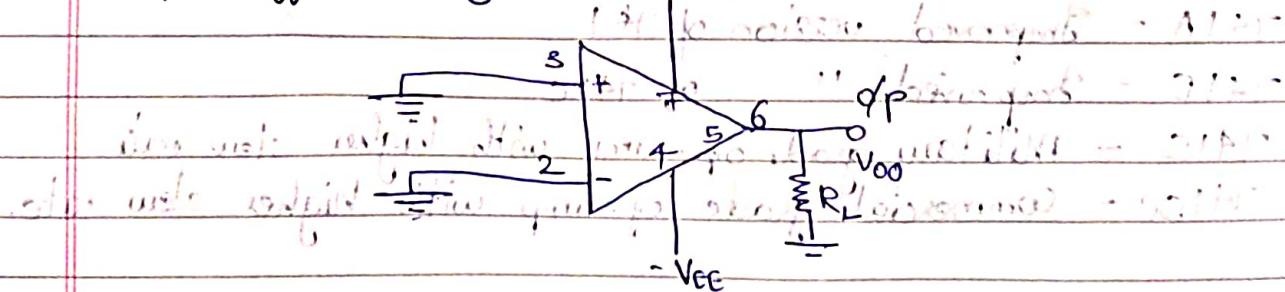

*) Input Bias Current

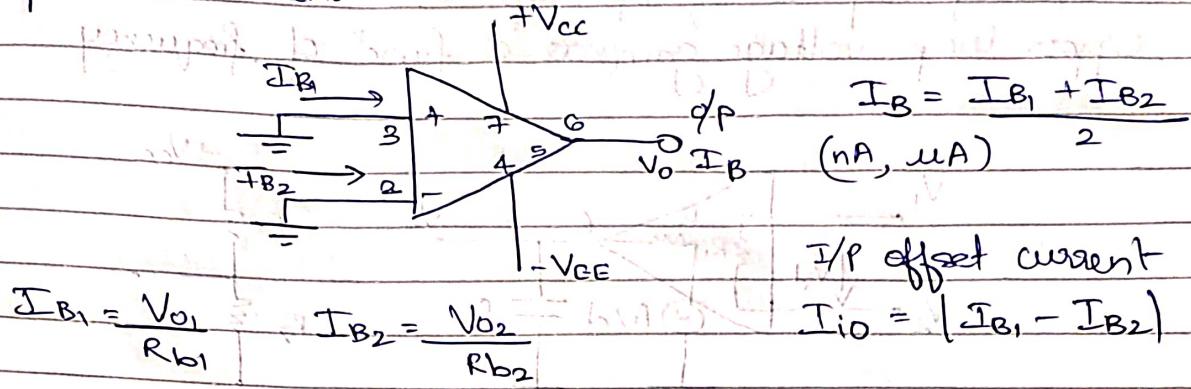

*) Offset Voltage Adjustment Range

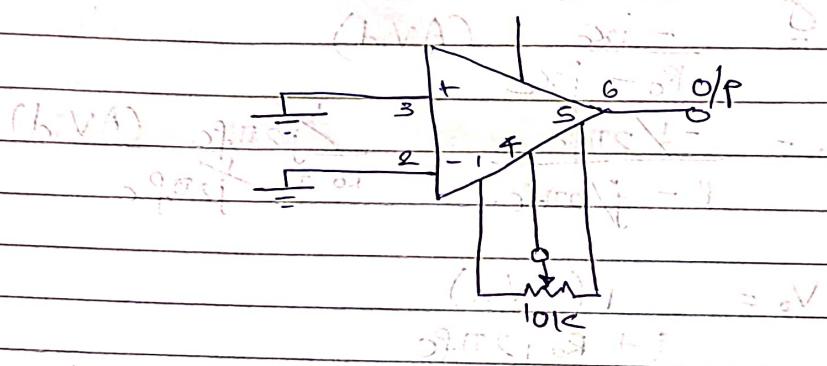

Q. For certain opamp, CMRR is 100dB, and differential gain is 10^5 , find common mode gain.

Ans:

$$\text{CMRR} = \frac{\text{Diff gain}}{\text{Common mode gain}}$$

$$\text{CMRR} = 20 \log_{10} \left[\frac{A_d}{A_{cm}} \right]$$

$$100 \text{dB} = 10^5 \text{ Common mode gain}$$

$$10^5 = \frac{10^5}{\text{Common mode gain}}$$

$$\text{Common mode gain} = A_{cm} = 1 \text{ mA}$$

$$10^5 = \frac{10^5}{A_{cm}}$$

$$A_{cm} = 1$$

Q. An opamp has $I_{B1} = 400 \text{nA}$, $I_{B2} = 300 \text{nA}$. Determine bias current I_B and offset current I_{IO} .


Ans:

$$\text{Bias cur } I_B = \frac{400 + 300}{2} = 350 \text{nA}$$

$$I_{IO} = 100 \text{nA}$$

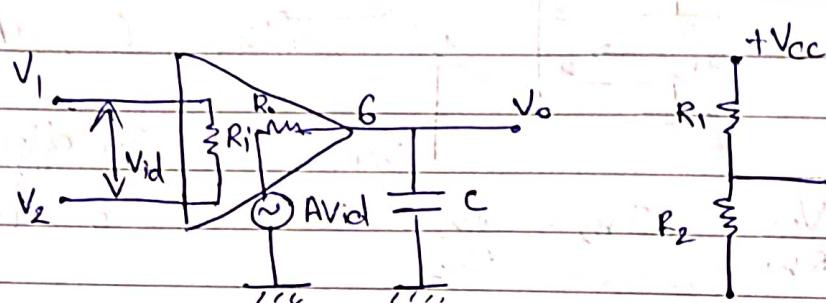X) Frequency response of op-Amp.

Open loop voltage gain as a funcⁿ of frequency



a) High freq' model of an op-Amp with single break frequency
Apply voltage divider rule.

$$V_o = \frac{-j\omega c}{R_o - j\omega c} (A V_{id})$$

$$V_o = \frac{-j/2\pi f_c}{R - j/2\pi f_c} = \frac{j/2\pi f_c}{R_o + j/2\pi f_c} (A V_{id})$$

$$V_o = \frac{1}{1 + R_o j/2\pi f_c} (A V_{id})$$

$$V_o = \frac{A (V_{id})}{1 + j/2\pi f_c R_o}$$

$$\boxed{\frac{V_o}{V_{id}} = \frac{A}{1 + j/2\pi f_c R_o}}$$

$$A_{OL}(f) = \frac{A}{1 + j/2\pi f_c R_o}$$

$A \rightarrow \text{gain}$
 $f = \text{Hz}$

$$f_0 = \frac{1}{2\pi R_o C}$$

$$A_{OL}(f) = \frac{A}{1 + j(f/f_0)}$$

$$\phi(f) = -\tan^{-1}\left(\frac{f}{f_0}\right)$$

$$A_{OL}(f) = \frac{A}{\sqrt{1 + \left(\frac{f}{f_0}\right)^2}} \quad (\text{Open-loop gain magnitude})$$

The same eqn in dB

$$A_{OL}(f) = 20 \log A - 20 \log \sqrt{1 + \left(\frac{f}{f_0}\right)^2}$$


$$f_0 = 5 \text{ Hz} \quad A = 200,000 \text{ for } 741 \text{C} \quad (f=0 \text{ Hz}).$$

∴ DC gain = 100 dB.

$$BW = \frac{0.35}{\sqrt{1 + \left(\frac{f}{f_0}\right)^2}}$$

$$\left[\frac{V_o}{V_i} = \frac{R_f}{R_i} \left(1 + \frac{R_f}{R_i} \right) \right] \Rightarrow \frac{V_o}{V_i} = 1 + \frac{R_f}{R_i}$$

f) Gain of non-inverting amplifier.

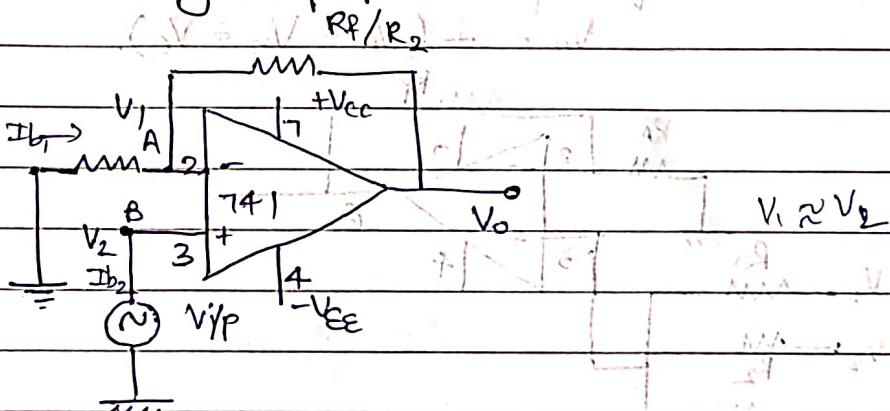


Applying KCL at node A: $0 - V_1 = V_i - V_o$

$$R_1 = \frac{R_f}{R_p}$$

$$\frac{V_o}{V_i} = 1 + \frac{R_f}{R_p}$$

Non-invert gain = $1 + \frac{R_f}{R_p}$

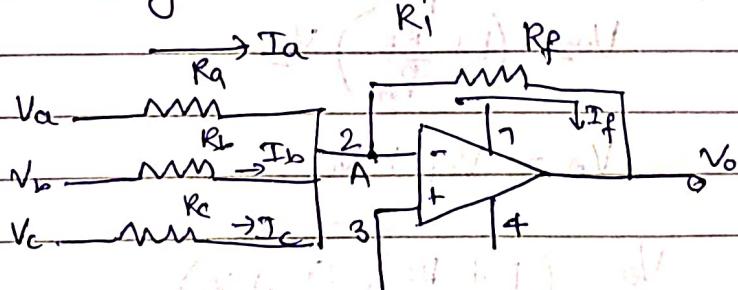

(Inverting) fig(a) Summing amplifier.

KCL at node A.

$$I_a + I_b + I_c = I_f$$

$$\frac{V_a - V_A}{R_A} = I_a$$

$$I_a = \frac{V_a}{R_A}, I_b = \frac{V_b}{R_b}, I_c = \frac{V_c}{R_c}$$

$$I_f = \frac{V_o}{R_f}$$


$$I_a + I_b + I_c = I_f$$

$$\frac{V_a}{R_A} + \frac{V_b}{R_b} + \frac{V_c}{R_c} = -\frac{V_o}{R_f}$$

$$\therefore V_o = - \left[\frac{R_f}{R_A} V_a + \frac{R_f}{R_b} V_b + \frac{R_f}{R_c} V_c \right]$$

$$R_f = R_A = R_b \neq R_c = R_f \text{ (Non-inverting)} \quad (f)$$

$$V_o = -(V_a + V_b + V_c),$$

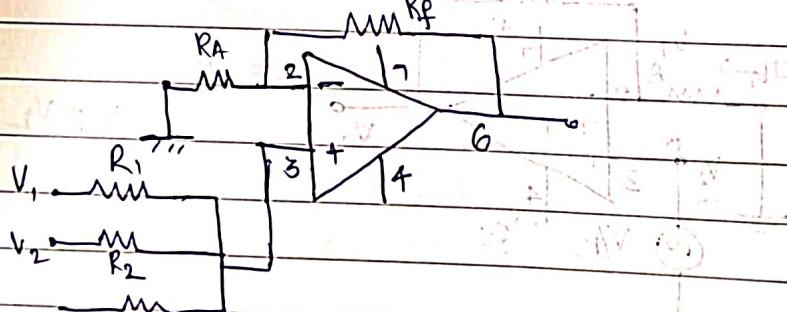

Non-Inverting Summing Amplifier
Assume V_1 acting alone

$$V_{o1} = \left(1 + \frac{R_f}{R_A}\right) V_1 \quad \text{--- (1)}$$

Only V_2 source is present

$$V_{o2} = \left(1 + \frac{R_f}{R_A}\right) V_2$$


$$V_o = V_{o1} + V_{o2}$$

$$V_o = \left(1 + \frac{R_f}{R_A}\right) (V_1 + V_2)$$

~~$\propto \log$~~ Integrator

$$\text{gain } dB = 20 \log \left(\frac{V_o}{V_i} \right)$$

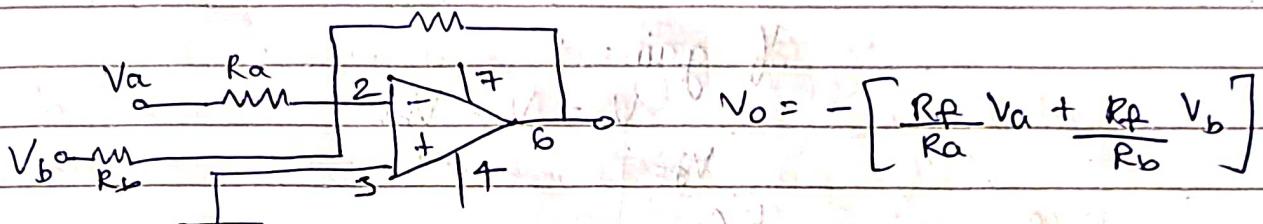
Inverting summing / averaging / scaling amplifier.



$$R_f = R_a = R_b = R.$$

$$V_o = -(V_a + V_b).$$

Non-Inverting Summing

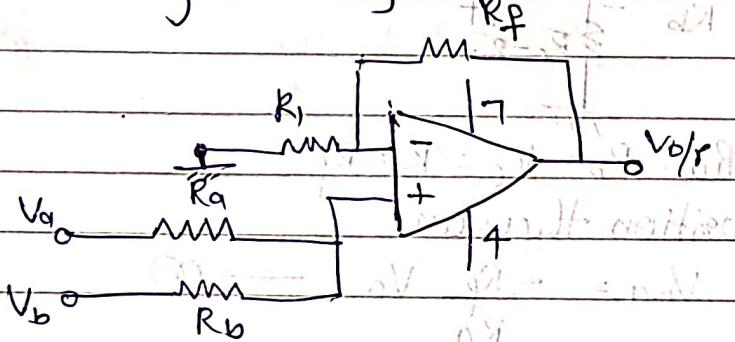

$$V_{oa} = \left(1 + \frac{R_f}{R_a} \right) V_a$$

$$\text{Voltage divider rule } V_1 = \left(\frac{R_b}{R_a + R_b} \right) V_a.$$

$$V_{oa} = \left(1 + \frac{R_f}{R_a} \right) \left(\frac{R_b}{R_a + R_b} \right) V_a \quad \text{--- (1)}$$

$$V_{ob} = \left(1 + \frac{R_f}{R_a} \right) V_1$$

$$V_1 = \left(\frac{R_a}{R_a + R_b} \right) V_b$$

$$V_{ob} = \left(1 + \frac{R_f}{R_a} \right) \left(\frac{R_a}{R_a + R_b} \right) V_b. \quad \text{--- (2)}$$

$$V_{ob} = V_{oa} + V_{ob}$$

$$- \left[1 + \frac{R_f}{R_a} \right] \left\{ \left(\frac{R_b}{R_a + R_b} \right) V_a + \left(\frac{R_a}{R_a + R_b} \right) V_b \right\}$$


$$R_a = R_b = R.$$

$$V_{ob} = \left(1 + \frac{R_f}{R_a} \right) \left(\frac{V_a + V_b}{2} \right)$$

If gain = 1

$$V_o = V_a + V_b.$$

Difference amplifier

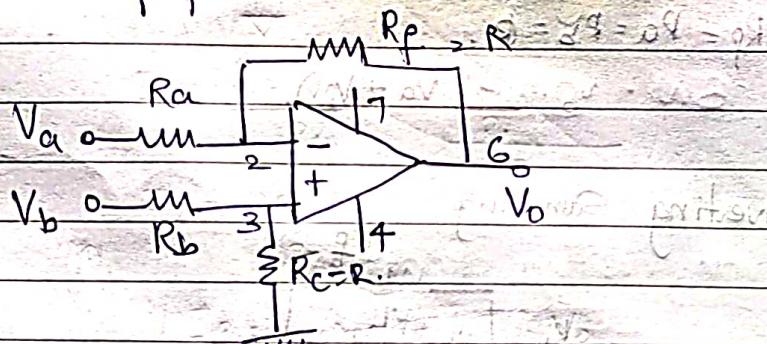

$$R_a = R_b = R_c = R = R_f$$

Apply superposition theorem

$$V_{oa} = -\frac{R_f}{R_a} V_a = 0.$$

$$V_{ob} = \left(1 + \frac{R_f}{R_a} \right) V_b$$

$$V_1 = \left(\frac{R_b}{R_a + R_b} \right) V_b$$

$$V_{ob} = \left(1 + \frac{R_f}{R_a} \right) \left(\frac{R_b}{R_a + R_b} \right) V_b$$

$$V_o = V_{oa} + V_{ob}$$


$$V_o = -\frac{R_f}{R_a} V_a + \left(1 + \frac{R_f}{R_a} \right) \left(\frac{R_b}{R_a + R_b} \right) V_b$$

$$R_f = R_a = R_b = R$$

$$V_o = -V_a + V_b$$

710012

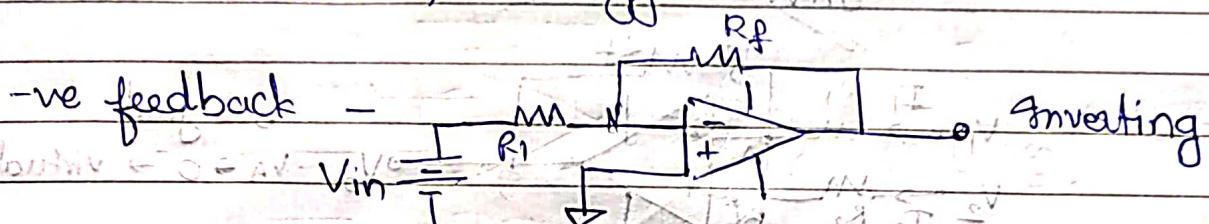
- * Whenever we apply the input \rightarrow topology.
- * 98% applications of op-amp \rightarrow -ve feedback
2% \rightarrow +ve feedback
oscillator, mult. trigger.



$$V_o = -\frac{R_f}{R_1} V_{in}$$

gain \uparrow
BW \uparrow
 $R_i \downarrow$
 $R_o \downarrow$

Non-Inverting

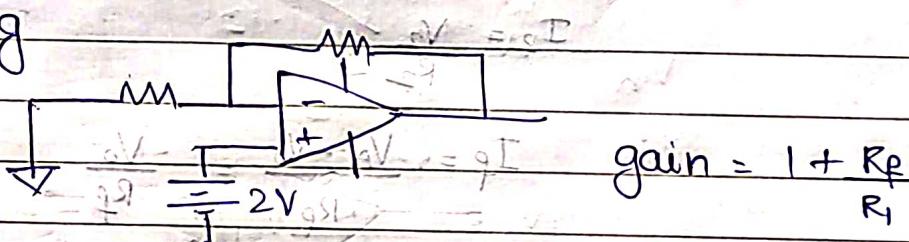

$$\text{gain} = 1 + \frac{R_f}{R_1}$$

$$V_o = \frac{1 + \frac{R_f}{R_1}}{\frac{1}{2} R_1} V_{in}$$

gain

180°

 $-\frac{R_f}{R_1}$

Non-gain

360° or 0°

 $1 + \frac{R_f}{R_1}$

Input impedance = R_{in}
(R_i)

Input impedance = R_{in}

very high avoids clct loading.

± 5 to ± 18 V


80 to 90% of ± Vcc.

$$(V_+ - V_-) = V_o$$


* Summing / Adder: \rightarrow Input with phasing controls
 more than one input.

Addressing to both sides A & B

Gnd. Non. Gnd. output

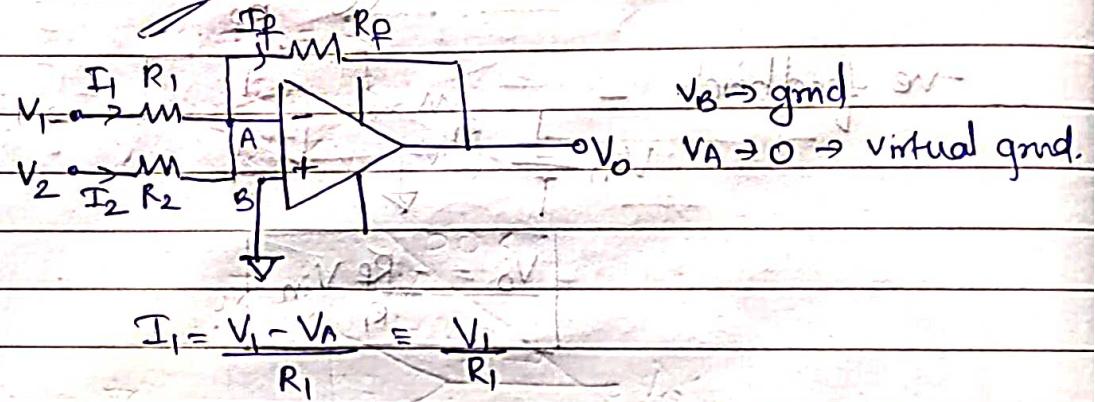

* Scalar / Average:

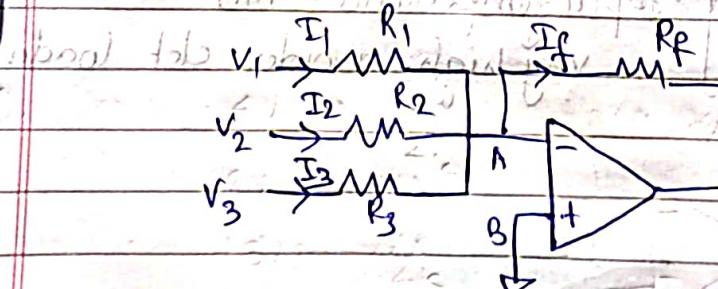


x) Voltage follower: follower:

$$V_o = V_{in}$$


→ Non-Inverting

$$R_f = 0$$

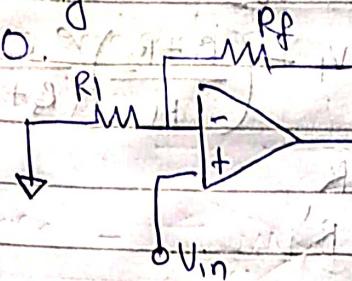


When the non-inverting amplifier is configured for unity gain, it is called voltage follower because the o/p voltage is equal and in phase with the i/p.
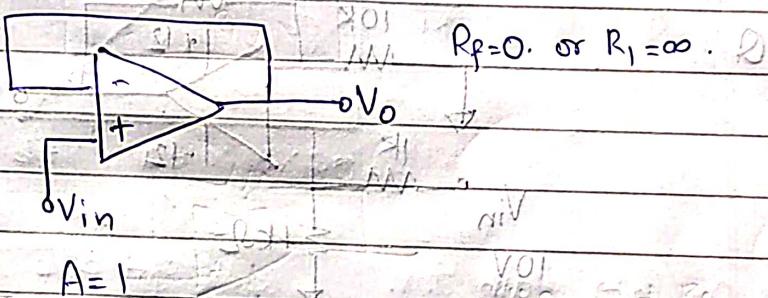
$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_{in}$$



x) Differential amplifier/subtractor:

$$V_o = A(V_2 - V_1)$$

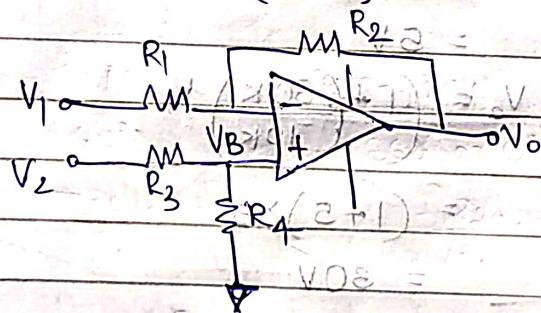

V_1 acting V_2 ground $\rightarrow V_{o1}$

V_2 acting V_1 ground $\rightarrow V_{o2}$

$$V_o = V_{o1} + V_{o2}$$

$$\textcircled{1} \quad V_{o1} = -\frac{R_2}{R_1} V_1$$

$$\textcircled{2} \quad V_B = \frac{R_4}{R_3 + R_4} V_2$$

$$\left(\frac{R_2}{R_1} + \frac{R_4}{R_3 + R_4}\right) V_1 + V_2 = V_o$$

$$V_{O2} = \left(1 + \frac{R_2}{R_1}\right) V_B$$

$$V_O = V_{O1} + V_{O2}$$


$$= -\frac{R_2}{R_1} V_1 + \left(\frac{R_1 + R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_2$$

$$R_1 = R_3 = R$$

$$R_2 = R_4 = R'$$

$$V_O = \frac{R'}{R} (V_2 - V_1)$$

$$50K = 0V$$

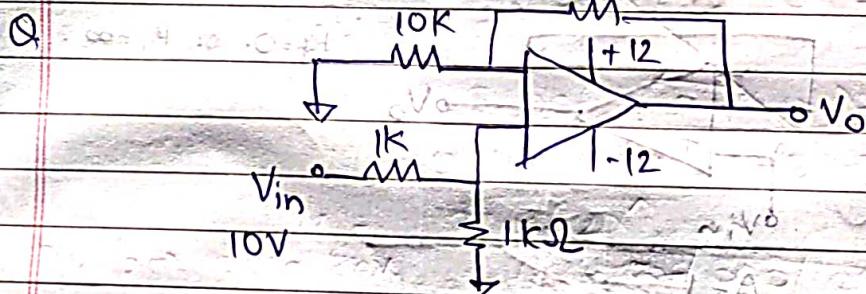

$$V_B = \frac{1K}{1K+1K} V_{in}$$


$$= 0.5 \times 10V = 5V$$

$$V_o = \left(1 + \frac{50K}{10K}\right) V_B$$

$$= (1+5) \times 5$$

$$= 30V$$

But $V_B = 10.8V$

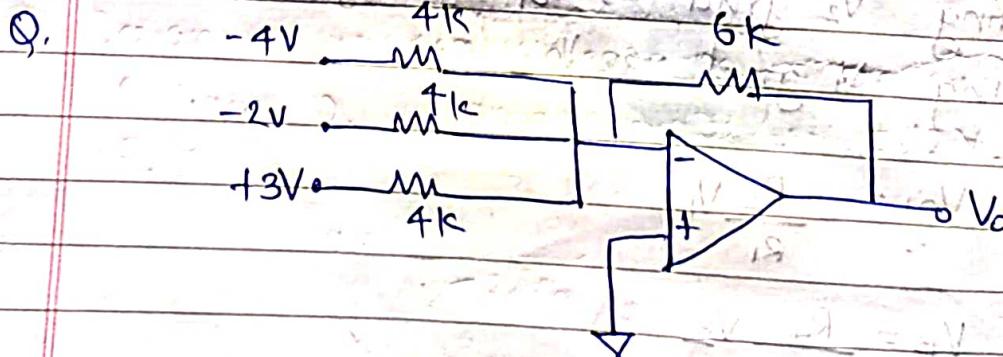


Soln:

$$V_o = - \left(\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 + \frac{R_F}{R_3} V_3 \right)$$


$$V_o = - \left(\frac{6 \times (-1)}{4} + \frac{6 \times (-2)}{4} + \frac{6 \times 3}{4} \right)$$

$$= - (-6 - 3 + 1.5)$$

$$V_o = 4.5V$$

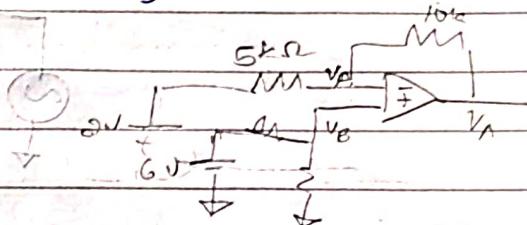
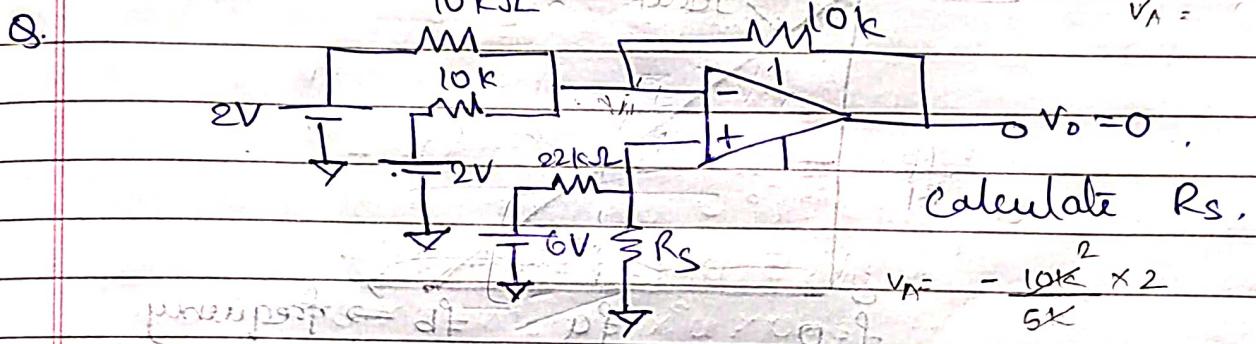
$$Q. \quad V_o = - (2V_1 + 3V_2 + 5V_3)$$




calculate R_S .

$$V_A = - \frac{10k^2 \times 2}{5k}$$

$$V_A = -4V$$

7) Integrator:

Inverting.

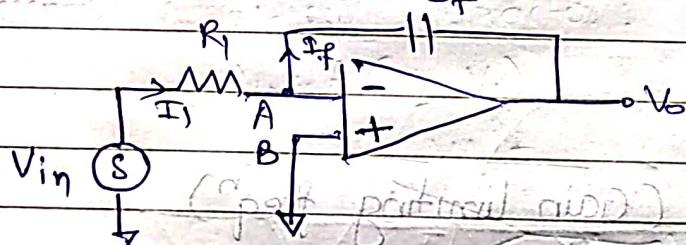

$$I_i = I_f$$

$$I_i = \frac{V_{in}}{R_i}$$

$$Q = CV$$


$$\frac{dQ}{dT} = C_f \frac{dV_f}{dT}$$

~~$$V_{in} = -C_f \frac{dV_o}{dt} \quad I_f = C_f \frac{d}{dt} (V_A - V_B)$$~~


~~$$V_{in} = \frac{d}{dt} V_o \quad = -C_f \frac{d}{dt} (V_o)$$~~

$$V_o = - \frac{1}{R_i C_f} \int V_{in} dt + C$$

$$0.1 \times 10.0 \times 10^{-6} \times 10^{-3}$$

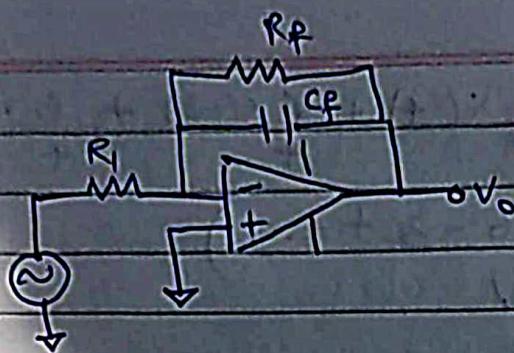Practical

$$\frac{R_f}{R_i} = \text{dc gain}$$

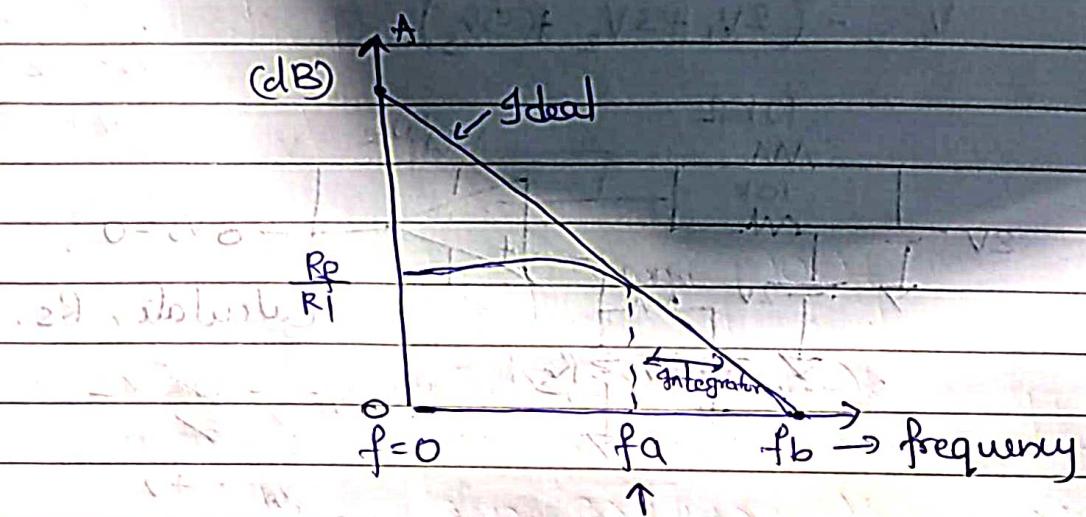

$0 - f_a \rightarrow$ plain inv.
amplifier

Cut-off / 3dB / cornered freq. (corner freq.)
 $f_b = \text{Unity gain freq.}$

*) Formulas:

$$f_a = \frac{1}{2\pi R_f C_f} \quad (\text{Gain limiting freq.})$$

$$f_b = \frac{1}{2\pi R_i C_f}$$

- Q Design a practical integrator where cut-off freq is 1.5kHz
DC gain 10. Op-amp operates at $\pm 12V$. Assume $C_f = 0.01\mu F$.

soln:

$$f_a = \frac{1}{2\pi R_f C_f}$$

$$1.5 \times 10^3 = \frac{1}{2\pi \times R_f \times 0.01 \times 10^{-6}}$$

$$R_f = 10.6 \Omega$$


$$\frac{R_f}{R_i} = 10$$

$$R_i = R_f = 1.06 \Omega$$


$$\frac{10}{\sqrt{2}} = 7.07$$

$$f_b = \frac{1}{2\pi \times 1.06 \times 0.01 \times 10^{-6}}$$

$$f_b = 15 \text{ kHz}$$

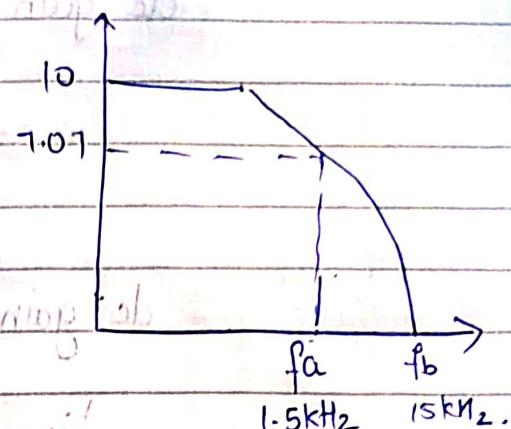

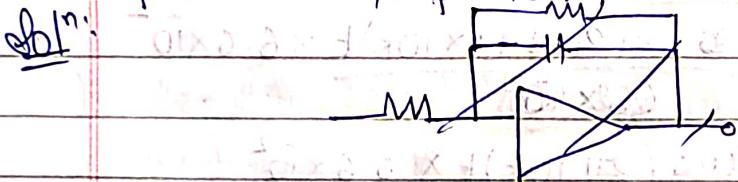- Q. Design a practical integrator component values $R_i = 120 \text{ k}\Omega$, $R_f = 1.2 \text{ M}\Omega$, $C_f = 10 \text{ nF}$. Determine the same frequency above which self integration will take place.




Determine dc gain.

Find the peak value for output voltage with sine wave input of 5 V and freq. 10 kHz.

Draw the rough sketch of freqⁿ response.

Soln:

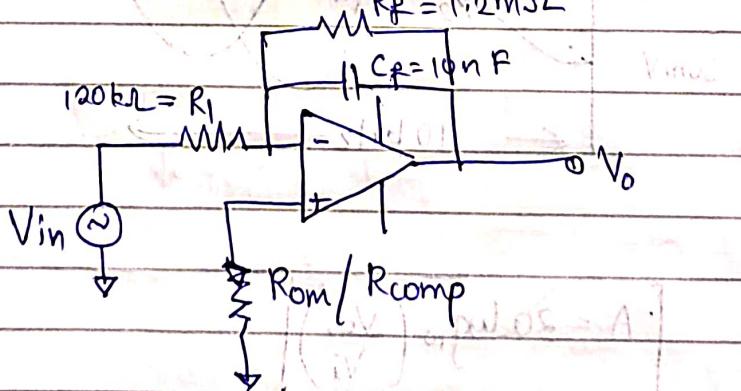

$$f_a = \frac{1}{2\pi R_f C_f}$$

$$= \frac{1}{2\pi \times 1.2 \times 10^6 \times 10 \times 10^{-9}}$$

$$f_a = 13.28 \text{ Hz}$$

$$\text{dc gain} = \frac{R_F}{R_I}$$

$$= \frac{1.2 \times 10^6}{120 \times 10^3}$$

$$= 10^6 \times 10^{-3} \times 10^{-2}$$

$$\text{dc gain} = 10$$


$$V_{in} = V_m \sin \omega t$$

$$V_o = -\frac{1}{R_I C_p} \int 5 \sin(2\pi 10k) t$$

$$= -\frac{1}{120 \times 10^3 \times 10 \times 10^{-9}} \times 2\pi \times 10^4$$


$$V_o = \cos(2\pi 3.14 \times 10k) t \times 6.6 \times 10^2$$
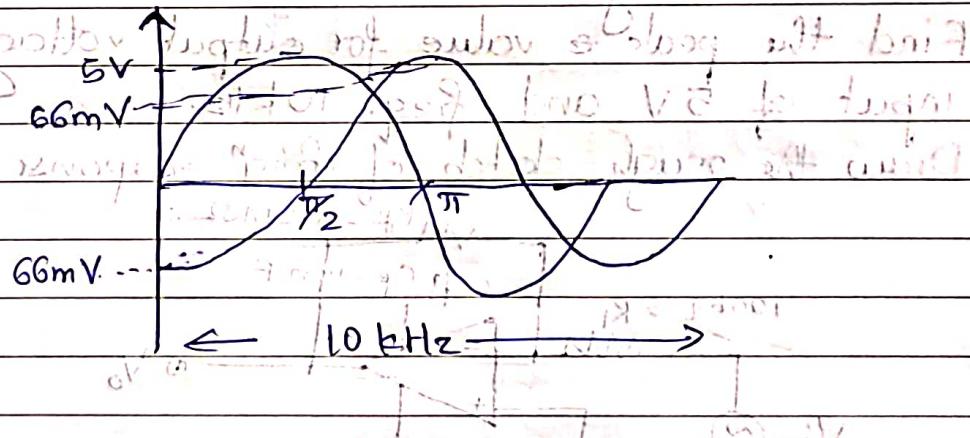
$$V_o = \cos(2\pi 10k) t \times 6.6 \times 10^{-2}$$





$$A = 20 \log_{10} \left(\frac{V_o}{V_i} \right)$$

X) Differentiator:

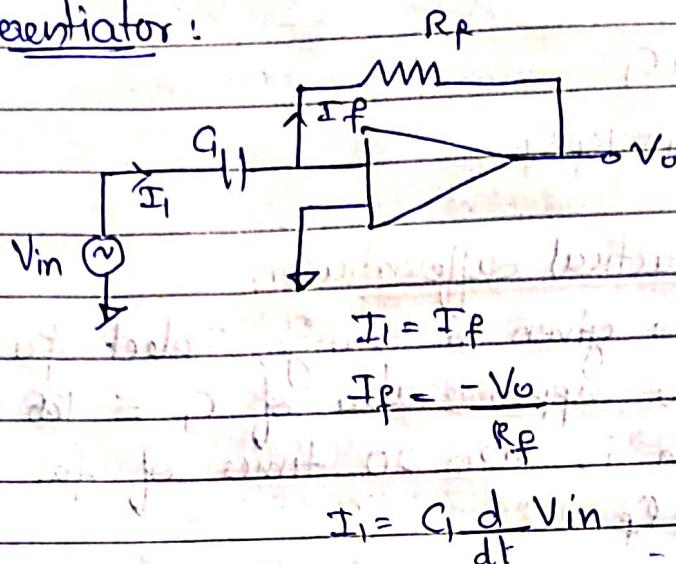

- 1) When $R_f \uparrow$, circuit becomes unstable.
- 2) Input impedance goes low, so ckt becomes susceptible.
→ noise overdriven overnight.

Practical Differentiator:

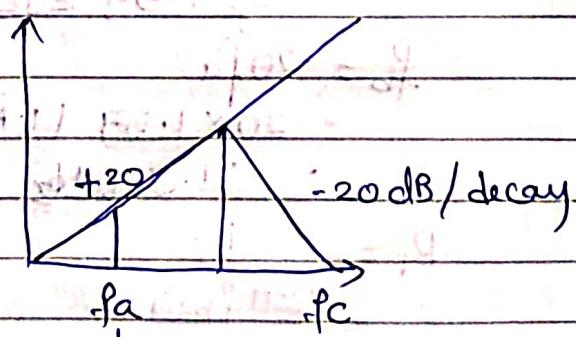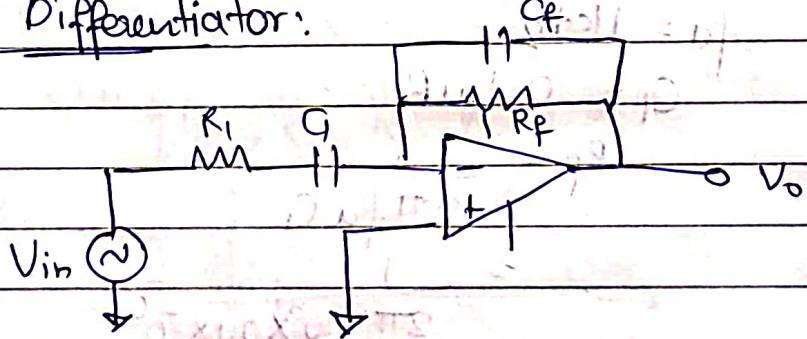

$$f_a = \frac{1}{2\pi R_f C_1}$$

$$f_b = \frac{1}{2\pi R_1 C_1}$$


$$R_1 C_1 = R_p C_p$$

*) Steps to design practical differentiator.

- If input signal is given in range, select f_a as the max.
- Select f_b . Assume approx. value of $C_1 \leq 100 \text{ nF}$.
- Select f_b which is 10 or 20 times of f_a .
- Use $R_1 C_1 = R_p C_p$

Q. Design a differentiator where input signal varies from 10 Hz to 1 kHz. If a sine wave of 1V, 1kHz is applied to the differentiator at input. Plot its output waveform.

Soln:

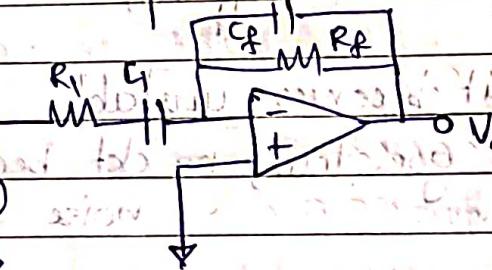

$$f_a = 1 \text{ kHz}$$

$$C_1 = 0.1 \text{ nF}$$

$$R_f = \frac{1}{2\pi f_a C_1}$$

$$= \frac{1}{2\pi \times 10^3 \times 0.1 \times 10^{-9}}$$

$$= 1.59 \text{ k}\Omega$$

$$f_b = 20 f_a$$

$$= 20 \times 1.59 \text{ kHz}$$

$$= 31.8 \text{ kHz}$$

$$R_1 = \frac{1}{2\pi f_b C_1}$$

$$= \frac{1}{2\pi \times 3.14 \times 20 \times 10^3 \times 0.1 \times 10^{-9}}$$

$$= 25.46 \text{ k}\Omega$$

$$= 10^4 \times 0.0079 \\ = 79 \mu\text{F}$$

$$R_1 C_1 = R_f C_p$$

$$\frac{79 \times 0.10^4}{1.59 \times 10^3} = C_p$$

$$49.6 \times 10^{-10} = C_p$$

$$C_p = 4.96 \text{ nF}$$

$$R_{\text{om}} = R_f \parallel R_1$$

$$R_{\text{om}} = 79 \Omega \text{ (approx)}$$


$$V_o = -R_f C_1 \frac{d}{dt} V_{\text{in}} = V_{\text{in}} \sin \omega t \\ = 18 \sin 2\pi 10^3 t$$

$$= -1.59 \times 10^3 \times 10^{-7} \frac{d}{dt} \sin \omega t$$

$$= -1.59 \times 10^4 \times \omega \times \cos \omega t$$

$$= -1.59 \times 10^4 \times 2 \times 3.14 \times 10^3 \cos \omega t$$

$$= -0.99 \cos \omega t$$

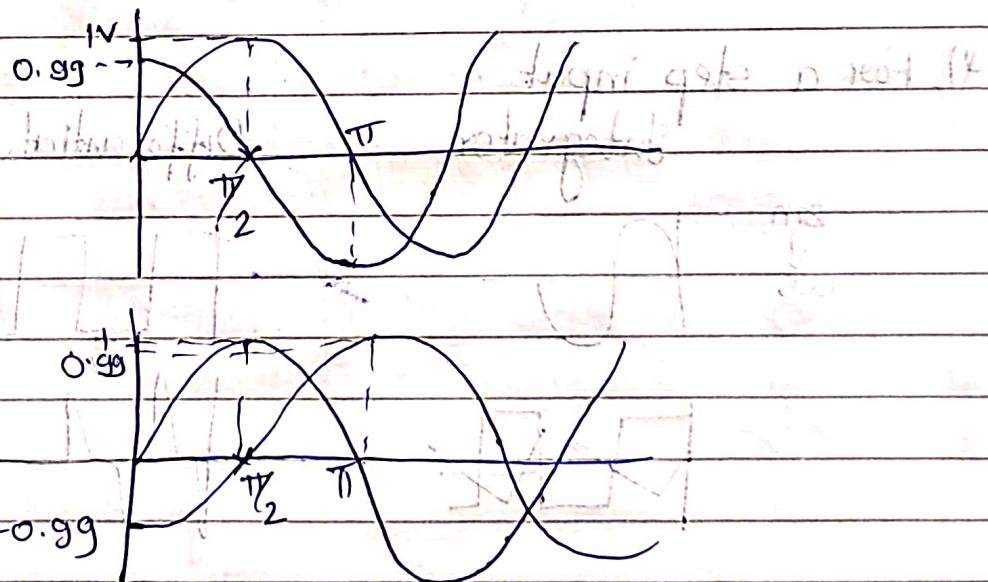

- Q. Design a practical differentiator that would differentiate an input signal from 150 Hz. Assume C_1 to be $1 \mu\text{F}$ and $\beta_b = 10^4$

Soln:

$$f_a = 150 \text{ Hz}$$

$$C_1 = 1 \mu\text{F}$$

$$R_f = \frac{1}{2\pi R_p f_a C_1} = \frac{1}{2\pi \times 10^3 \times 150 \times 10^{-6}} = 1.08 \text{ k}\Omega$$

$$= \frac{1}{2\pi \times 10^3 \times 150 \times 10^{-6}} = 1.08 \text{ k}\Omega$$

$$= 1.08 \text{ k}\Omega$$

$$f_b = 10 f_a$$

$$= 10 \times 150 = 1500 \text{ Hz}$$

$$f_b = 1500 \text{ Hz}$$


$$R_1 = \frac{1}{2\pi R_f f_b C_1} = \frac{1}{2\pi \times 10^3 \times 1500 \times 10^{-6}} = 106.1 \text{ }\Omega$$

$$R_1 C_1 = R_f C_f$$

$$C_f = \frac{106.1 \times 10^{-6}}{10^3 \times 1.08 \times 10^3} = 1.08 \times 10^{-9}$$

$$C_f = 0.088 \text{ nF} = 0.1 \mu\text{F}$$

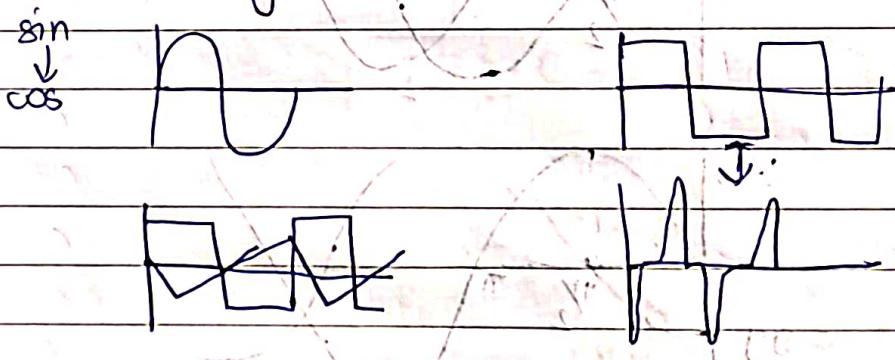* For a step input
 Integrator Differentiator



- Q. Design a differentiator which differentiates an input signal which varies from 10 Hz to 500 Hz. If a sine wave of 2V peak at 500 Hz is applied to the differentiator input. Write exp. for its output and plot the waveform.
- $C_1 = 0.1 \mu\text{F}$ $f_b = 10 f_a$


Instrumentation Amplifier:

→ High gain

→ $R_i \uparrow$

→ $R_o \downarrow$

→ High CMRR

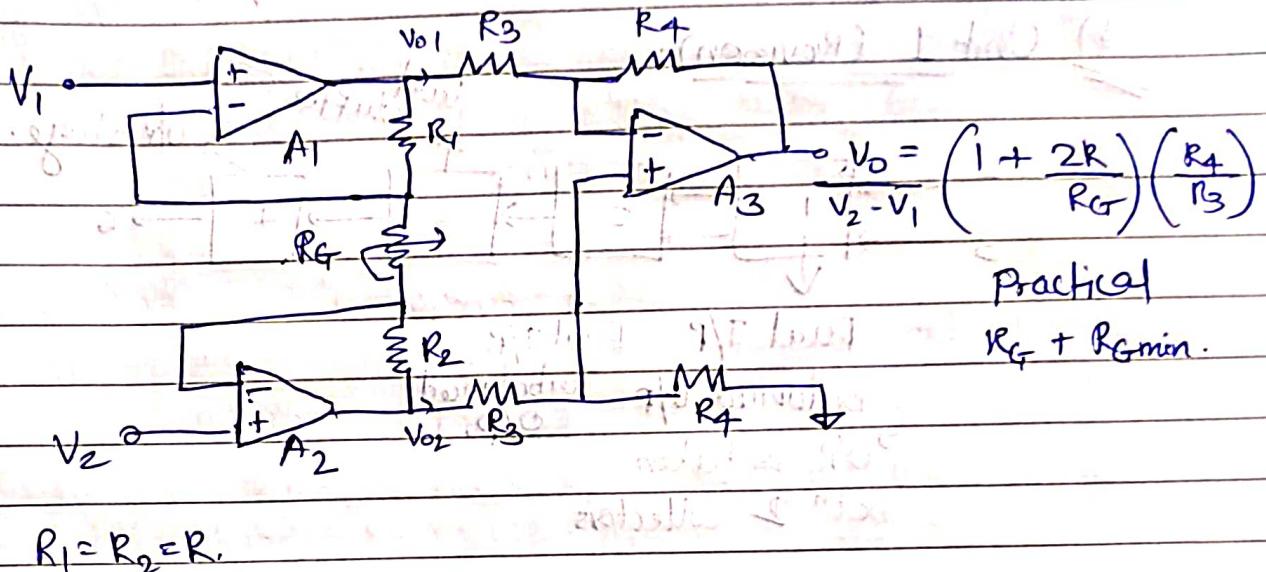

Q. Calculate the gain offered by 3 Op-Amp based IA for given

$$R_1 = R_2 = 100 \text{ k}\Omega, R_f = 5 \text{ k}\Omega, R_4 = R_3 = 1 \text{ k}\Omega.$$

Soln: $V_o = (1 + \frac{2 \times 100 \times 10^3}{5 \times 10^3}) (1)$

gain = 41.66

Q. Design an IA using 3 Op-Amps where gain can be varied from 1 to 500. Assume $R_1 = R_2 = 100 \text{ k}\Omega$ $\left(\frac{R_f}{R_3}\right) = 0.5$

Soln: $A = \left(1 + \frac{2R_f}{R_{G\max}}\right) (0.5)$

$$1 = \left(1 + \frac{2 \times 100 \times 10^3}{R_{G\max}}\right) 0.5$$

$$2 = 1 + \frac{200 \times 10^3}{R_{G\max}}$$

$$1 = \frac{200 \times 10^3}{R_G}$$

$R_G = 5$

$R_G = 200 \text{ k}\Omega$


$$500 = \left(1 + \frac{200k}{R_{Gmin}}\right) 0.5$$

$$1000 = 1 + \frac{200k}{R_{Gmin}}$$

$$R_{Gmin} = 4.99k\Omega, 0.2k\Omega$$

most of the voltage gain is input resistance

Unit 1 (Revision):

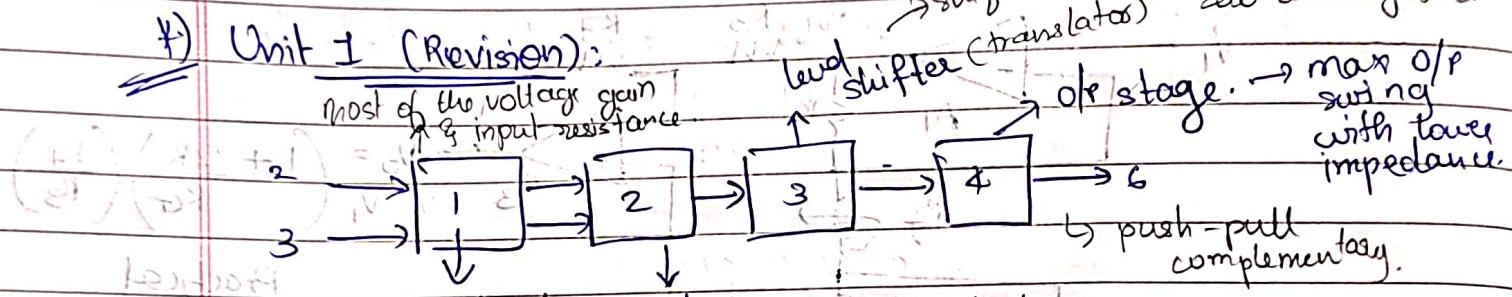

shift the o/p of inter. stage to zero w.r.t ground.

level shifter (translator) o/p stage. \rightarrow max o/p swing with lower impedance.

push-pull complementary.

Dual I/P Dual I/P (Intermediate)

Balanced O/P unbalanced o/p.

O/P is taken output is well above ground potential
betn 2 collectors due to direct coupling.

$$A_d = \frac{R_c}{R_s} \quad \text{Balanced.}$$

$$A_d = \frac{R_c}{R_s} \quad \text{unbalanced}$$

Ideal

CMRR - ability to reject common mode signal.

A

∞

R_i

∞

- any signal

source can drive it

- can drive ∞ no. of other

devices

V_{cm} = 0

CMRR = $\frac{Ad}{Ac}$ \rightarrow Differential gain

Common mode gain.

R_o

0

- output voltage change simultaneously

= 96 dB.

CMRR

∞

- o/p V is zero with i/p voltage

when i/p is zero

$$= 20 \log_{10} (61356).$$

PSRR

0

- output voltage change simultaneously

= 96 dB.

Slew Rate

∞

- output voltage change simultaneously

= 96 dB.

offset voltage

0

- o/p V is zero with i/p voltage

A_c = $\frac{V_{cm}}{V_{om}}$

offset current

0

- when i/p is zero

bias current

0

Q. CMRR (P) = 100 dB, $A_c = 0.1$, calculate Ad.

$$\text{Soln: } 100 = 20 \log_{10} (A)$$

$$5 = \log_{10} (A)$$

$$10^5 = A$$

$$10^5 = \frac{Ad}{A_c}$$

$$10^5 = \frac{Ad}{0.1}$$

$$Ad = 10,000.$$

Ans: $10^5 = \frac{Ad}{0.1}$

\downarrow PSRR (SVRR). \rightarrow change in output voltage caused by variation in supply voltage
Power Supply Rejection Ratio: offset V should not change with input voltage.

* Slew Rate: Rate of change of output w.r.t. time.
↳ associated with AC

* Practical values of 741C

$$A_{vP} = 1.2 \times 10^5 \text{ for } 741C$$

$$R_i = 2M\Omega \rightarrow \text{equi } \pi \text{ measured at either inv. or non-inv. inp. terminal with other terminal connected to ground.}$$

$$R_o = 75\Omega$$

$$\text{CMRR} = 90 \text{ dB}$$

$$\text{S.R.} = 0.5 \text{ V/us}$$

Inp. offset V - 6 mV - without applying I/P, still get some finite amount of o/p voltage.

$$\text{offset I} = 200 \text{ nA}$$

$$\text{Bias current} = 500 \text{ nA} \rightarrow |I_{B1} + I_{B2}| \text{ (crossover).}$$

$$\text{PSRR} = 96 \text{ dB. } = \frac{\Delta V_{oP}}{\Delta V}$$

$$\text{SR} = \frac{V_o}{t}$$

$$\frac{dV_o}{dt} = V_m \omega \cos \omega t$$

$$\text{SR} = \omega V_m$$

$$(i) V_o = V_{in}$$

$$(ii) V_o = V_m \sin \omega t$$

$$+0.5$$

$$SR = 2\pi f V_m$$

$$f = \frac{SR}{2\pi V_m}$$

↑

full power B.W.

Q. Calculate full power B.W. for 741 IC which operates at (max operating freq) $\pm 12V$.

Soln:

$$S.R. = 0.5 \text{ V/us}$$

$$f = \frac{0.5}{2 \times 3.14 \times 10.8 \times 10^6}$$

$$= 7.3 \text{ kHz}$$

Q. LM356 IC, $SR = 10V/\mu s$, calculate full power B.W.

$$V_m = 2V$$

Soln:

Q. Assume $S.R. = 0.5 \text{ V/us}$, justify whether it is possible to amplify a square wave of peak to peak 500mV . Rise time - $0.4 \mu \text{s}$. Peak to Peak output 5V .

Soln:

$$V_b = (0.9 - 0.1) \times 5$$

$$V_b = 4V$$

$$\frac{dV_b}{dt} = \frac{4V}{4 \mu s}$$

$$= 1 \text{ V/us.}$$

Q. Calculate O/P Voltage for Op-Amp whose open loop gain is 2×10^5 , Non - inv. $V_2 = 10\text{mV}$ $V_1 = 5\text{mV}$.

Soln:

$$V_o = A(V_2 - V_1)$$

$$= 2 \times 10^5 (2 \times 10^{-6})$$



$$= 0.4$$

BJT / FET / CMOS,

$R_i \uparrow$

$$\alpha_e = \frac{26mV}{I_E} \Rightarrow \frac{25.8}{I_C}$$

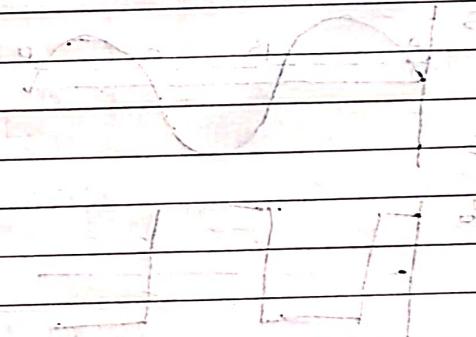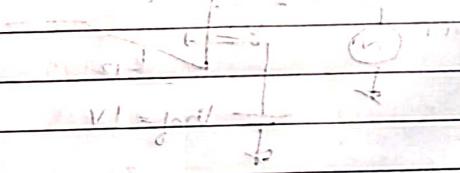Inp. off. set. Vol. - V that must be applied to null the output.
 Op voltage swing - indicate the value of +ve and -ve saturation voltages of the op-Amp. Never exceeds $+V_{CC}$ and $-V_{EE}$.



Op-amp has a saturated output voltage. It can't change its output voltage until it reaches the saturation voltage. This is because the output voltage is controlled by the error voltage.

Op-amp has a saturated output voltage. It can't change its output voltage until it reaches the saturation voltage. This is because the output voltage is controlled by the error voltage.

Op-amp has a saturated output voltage. It can't change its output voltage until it reaches the saturation voltage. This is because the output voltage is controlled by the error voltage.

Op-amp has a saturated output voltage. It can't change its output voltage until it reaches the saturation voltage. This is because the output voltage is controlled by the error voltage.

Op-amp has a saturated output voltage. It can't change its output voltage until it reaches the saturation voltage. This is because the output voltage is controlled by the error voltage.

Op-amp has a saturated output voltage. It can't change its output voltage until it reaches the saturation voltage. This is because the output voltage is controlled by the error voltage.

Op-amp has a saturated output voltage. It can't change its output voltage until it reaches the saturation voltage. This is because the output voltage is controlled by the error voltage.

Op-amp has a saturated output voltage. It can't change its output voltage until it reaches the saturation voltage. This is because the output voltage is controlled by the error voltage.




Op-amp has a saturated output voltage. It can't change its output voltage until it reaches the saturation voltage. This is because the output voltage is controlled by the error voltage.

Unit - 3

3/11/22

*) Schmitt Trigger:

Working with the help of hysteresis and forms direct AC to direct DC applications.

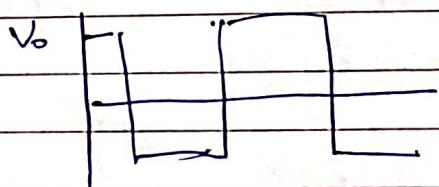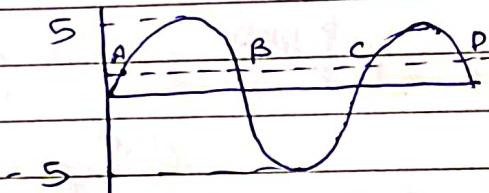
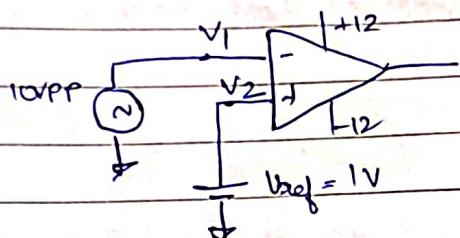
*) Comparator:


Schmitt

*) Schmitt Trigger / Regenerative Comparator

Schmitt Trigger is the only circuit which employs the feedback.


(Noise Immunity)

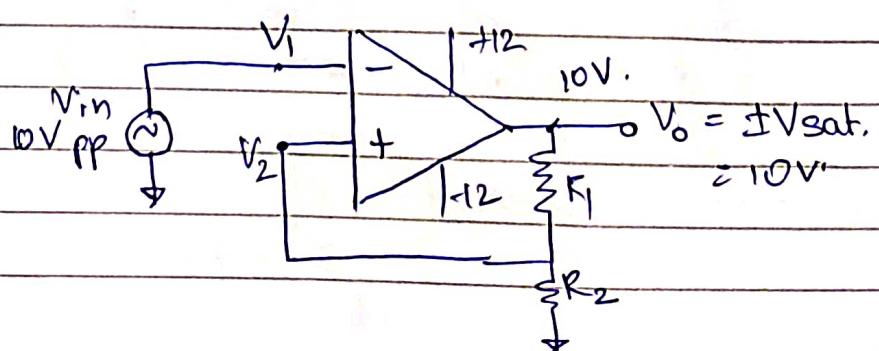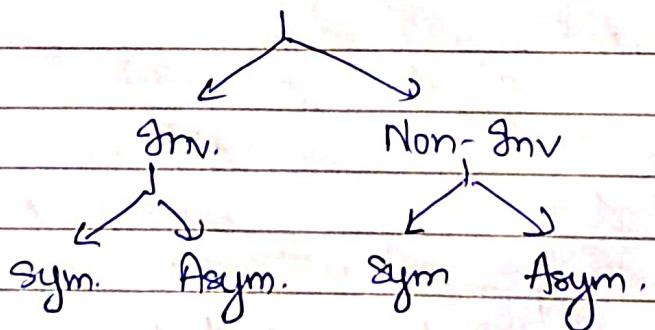

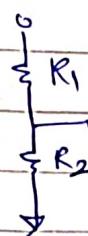

$$V_x = \frac{R_2}{R_1 + R_2} \times 10$$

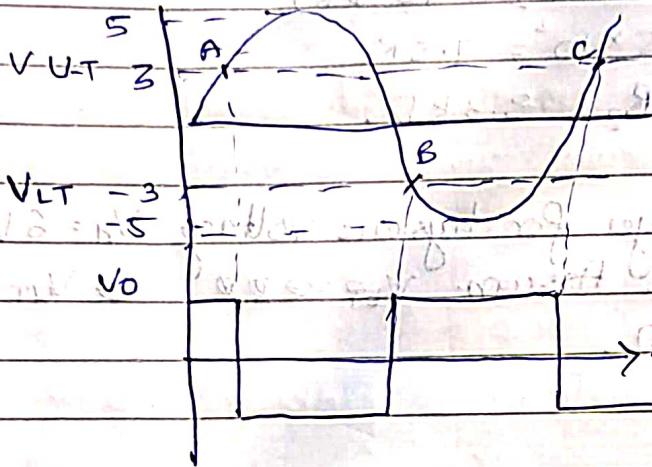V_{LT} up to
upper trigger
 V_{LT} . lower trigger.




V_1	V_2
0	3V
1	3.
3.1	3

V_1	V_2
+3V	-3V
3	-3V.
0	-3V
-1	-3V

$$V_{LT} = \frac{R_2}{R_1 + R_2} V_{sat}$$

$$V_{LT} = -\frac{R_2}{R_1 + R_2} V_{sat}$$

Transfer characteristic:

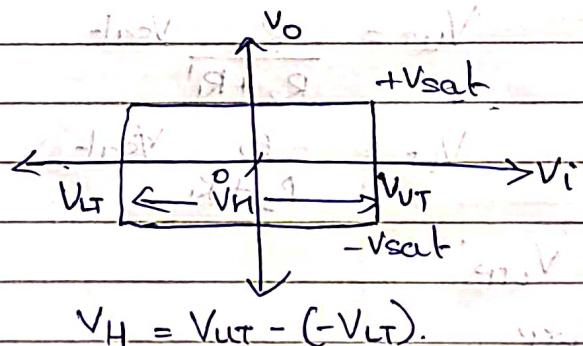

$$V_H = V_{LT} - (-V_{LT})$$

- Q. Design an inverting type schmitt trigger to get trigger levels as ± 3.3 V. Assume Op-Amp operates at ± 12 V. Assume R_1 to be 7.5 k Ω . Input signal applied is $10V$ ptoP sine wave.

Ans: Assume Op-Amp 90% of saturation

$$V_o = f(V_i)$$

Design of ptoP

$$V_{UT} = \frac{R_2}{R_1 + R_2} V_{sat}$$

$$3.3 = \frac{R_2}{7.5 \times 10^3 + R_2} \times 10^{-8}$$

$$24.75 \times 10^3 + 3.3R_2 = 10.8R_2$$


$$24.75 \times 10^3 = 7.5R_2$$

$$R_2 = 3.3 \text{ k}\Omega$$

Q. Design a schmitt trigger for hysteresis voltage $V_H = 6 \text{ V}$. Op-amp saturate at $\pm 10.8 \text{ V}$. Assume $V_{LTP} = -2 \text{ V}$. ~~$V_{UT} = 4 \text{ V}$~~ .

Soln.: Assume $R_1 = 10 \text{ k}\Omega$.

i) Asymmetry:

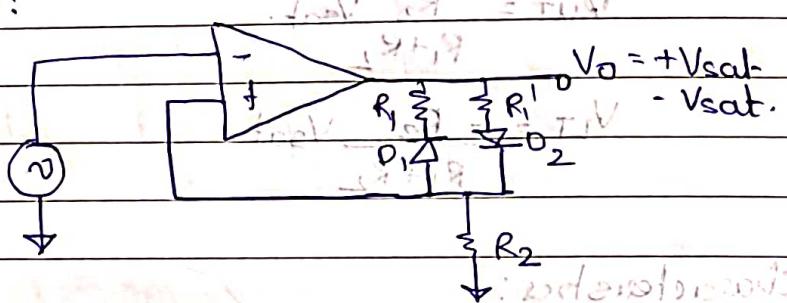

$$V_{UT} = \frac{R_2}{R_2 + R_1'} V_{sat} -$$

$$V_{LT} = -\frac{R_2}{R_2 + R_1'} V_{sat}.$$

$$V_H = V_{UTP} - V_{LTP}$$

$$6 = 4 - V_{LTP} \quad (4 \text{ V} - 2 \text{ V}) = 2 \text{ V}$$

$$V_{LTP} = -2 \text{ V}.$$

$$V_{UTP} = \frac{R_2}{R_2 + R_1'} \times 10.8$$

$$4 = \frac{10^4}{10^4 + R_1'} \times 10.8$$

$$4 \times 10^4 + 4R_1' = 10.8 \times 10^4$$

$$4R_1' = 6.8 \times 10^4$$

$$R_1' \approx 0.67$$

$$4R_1' = 6.8 \times 10^4$$

$$R_1' = 1.7 \times 10^4$$

$$R_1' = 17 \text{ k}\Omega$$

$$V_{LT} = -\frac{R_2}{R_2 + R_1} V_{sat}$$


$$R_2 + R_1$$

$$= -\frac{10^4 \times 10.8}{10^4 + R_1}$$



$$2 \times 10^4 + 2R_1 = 10.8 \times 10^4$$

$$2R_1 = 8.8 \times 10^4$$

$$R_1 = 4.4 \text{ k}\Omega$$

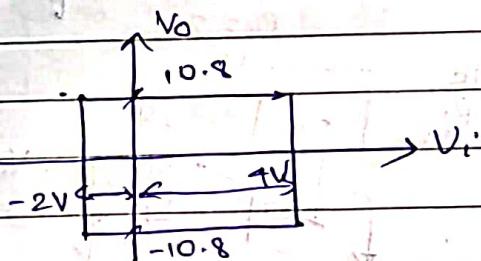


f.) Voltage limiter

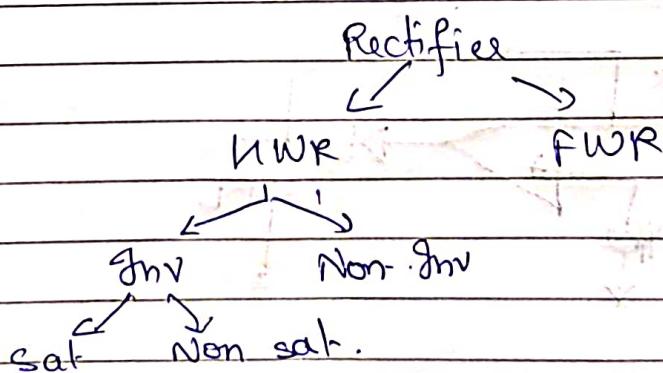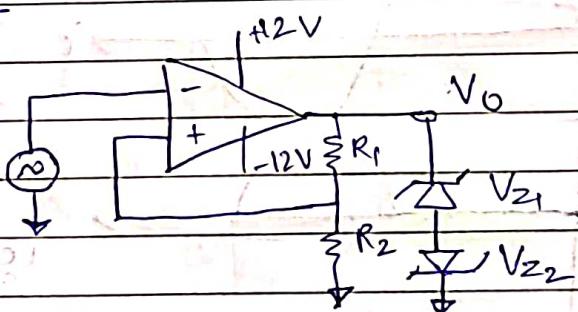

Rectifier:

Inv. HWR
Non-saturating

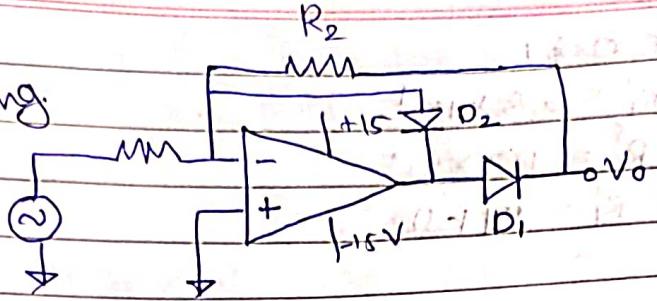


D₂ - avoiding Op-Amp from going into saturation.

If the input signal is less than the barrier potential of the diode, then that signal cannot be rectified by conventional rectifier.

∴ We need precision rectifier.


Op-Amp with the diode in the feedback loop → Super diode

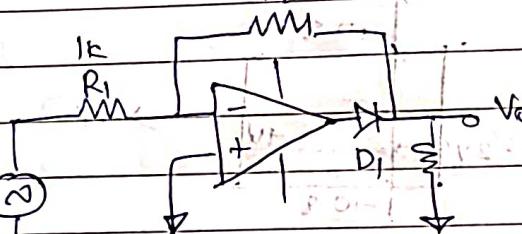Inv. HWR
Half wave precision
saturating type







$$R_2 = 2k\Omega$$

D sen.

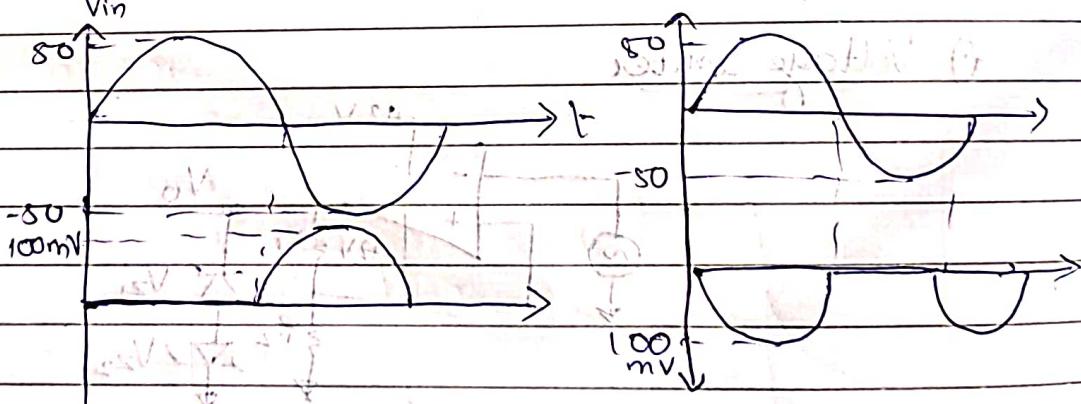

Non-inv. HWR
Saturating type

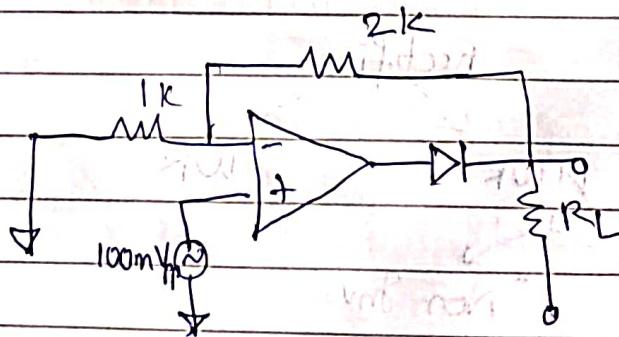

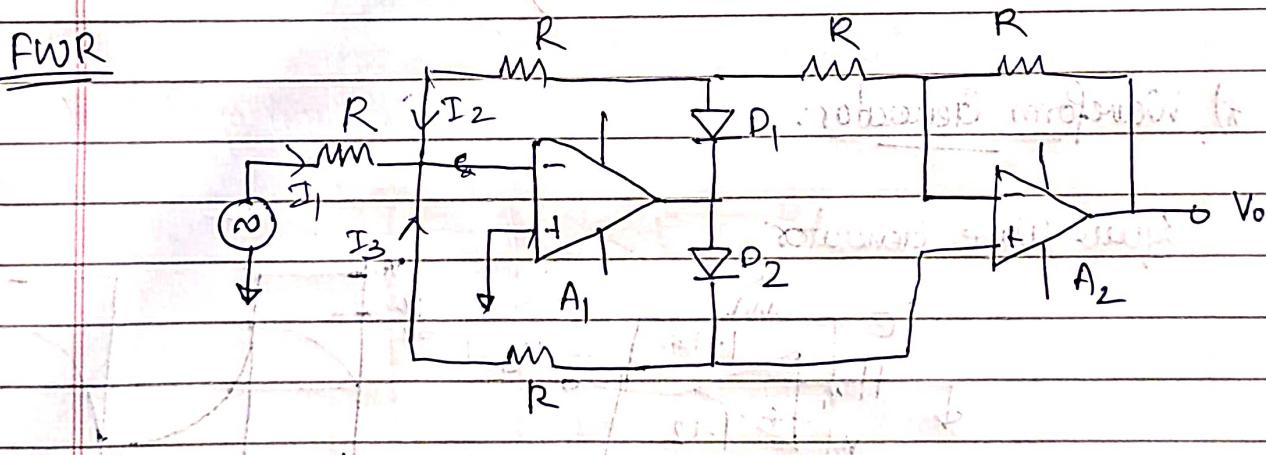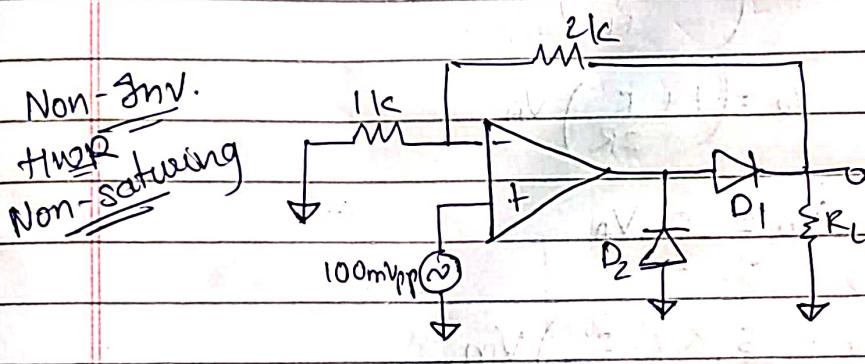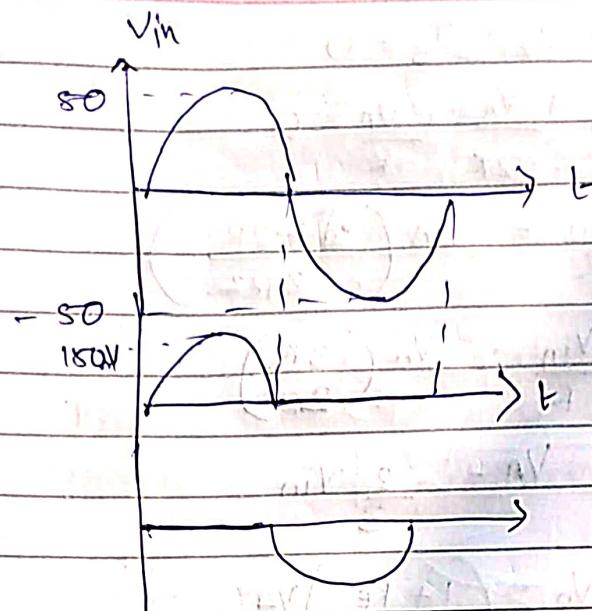

For -ve cycle:

$$I_1 = \frac{V_{\text{ain}}}{R}$$

$$I_2 = \frac{V_A}{2R}$$

$$I_3 = \frac{V_A}{R}$$

$$I_1 + I_2 + I_3 = 0$$

$$\frac{V_{in}}{R} + \frac{V_A}{2R} + \frac{V_A}{R} = 0$$

$$\frac{V_{in}}{R} = -V_A \left(\frac{\frac{R}{2} + 2R}{2R^2} \right)$$

$$\frac{V_{in}}{R} = -V_A \left(\frac{3R}{2R^2} \right)$$

$$V_A = -\frac{2}{3} V_{in}$$

$$V_o = \left(1 + \frac{R_f}{R_1} \right) V_A$$


$$V_o = \left(1 + \frac{R}{2R} \right) V_A$$

$$V_o = \frac{3}{2} V_A$$

$$V_o = \frac{3}{2} \times \left(-\frac{2}{3} \right) V_{in}$$

Q) Waveform Generator:

Square Wave Generator

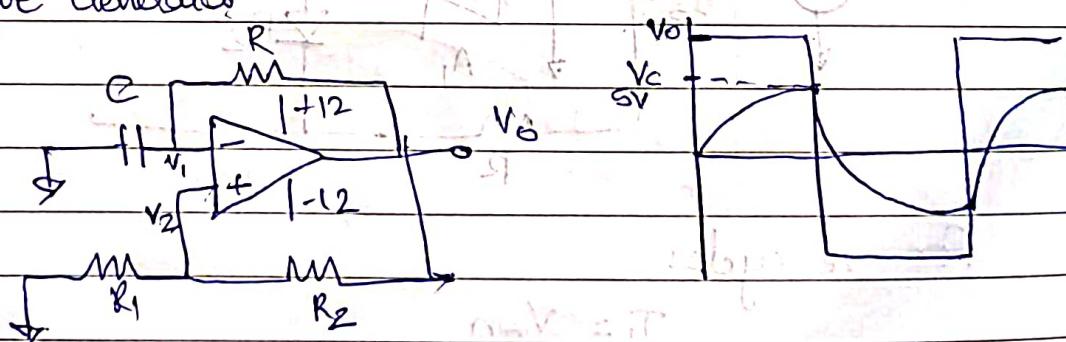

$$V_2 = \frac{R_1}{R_1 + R_2} V_{sat}$$

$$\beta = \frac{R_1}{R_1 + R_2}$$

Stable multivibrator.

$$f_0 = \frac{1}{2RC \ln\left(\frac{2R_1 + R_2}{R_2}\right)}$$

$$= \frac{1}{2RC \ln\left(\frac{1+\beta}{1-\beta}\right)}$$


Q. Design a square wave generator for f_0 as 1 kHz. Assume $\beta = 0.5$. Assume $C = 0.1 \mu F$. Assume Op-Amp operates at $\pm 15V$.

soln:

$$f_0 = \frac{1}{2RC \ln\left(\frac{1+\beta}{1-\beta}\right)}$$

$$10^3 = \frac{1}{2 \times R \times 0.1 \times 10^{-6} \ln\left(\frac{1+0.5}{1-0.5}\right)}$$
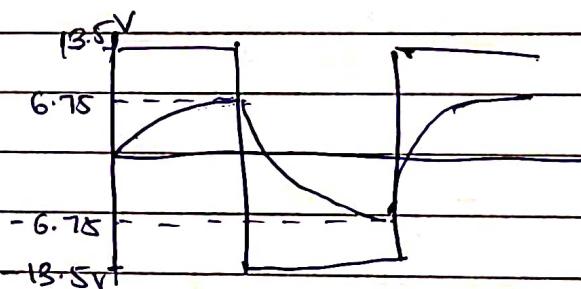
$$\begin{aligned} R &= \frac{1}{10^7 \times 2 \times 1.09} \\ &= 0.1 \times 10^{-4} \\ &= 1.6 \times 10^{-5} \text{ or } 0.45 \times 10^4 \\ &= 4.5 k\Omega. \end{aligned}$$



Q. Design a wave-form generator for $f_0 = 10$ kHz. Duty cycle = 50%. Assume $\beta = 0.5$, $C = 0.1 \mu F$.

soln:

$$T = \frac{1}{f} = \frac{1}{10 \times 10^3}$$

$$0.1 \times 10^{-3} = 0.1 \text{ ms}$$



$$0.5 = \frac{T_{on}}{T_{total}}$$

$$T_{on} = 0.03 \text{ ms}$$

$$T_{off} = 0.1 - 0.03 \\ = 0.07 \text{ ms.}$$

$$T_{on} = R_i C \ln \left(\frac{1+B}{1-B} \right)$$
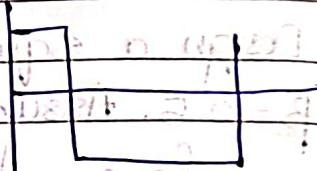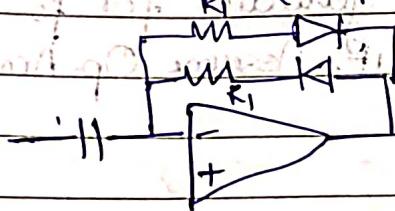
$$T_{off} = R_i' C \ln \left(\frac{1+B}{1-B} \right).$$



$$I = 0.03 \text{ ms} \times 10^6 \text{ A} = 30 \mu\text{A}$$

$$(e^{-0.03})^{10^6} = 0.001$$


$$= 1$$

$$1 - e^{-0.03} \approx 0.03$$

$$1 - 0.001 \approx 0.999$$

$$e^{-0.03} \approx 0.97$$

$$1 - e^{-0.03} \approx 0.03$$

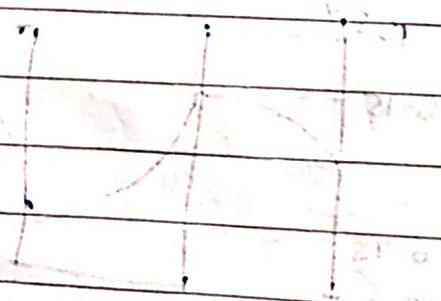

$$I_{max} = 0.03 \text{ ms} \times 10^6 \text{ A} = 30 \mu\text{A}$$

$$R = \frac{V}{I} = \frac{10 \text{ V}}{30 \mu\text{A}} = 333 \text{ M}\Omega$$

$$R = \frac{V}{I} = \frac{10 \text{ V}}{30 \mu\text{A}} = 333 \text{ M}\Omega$$


14/11/22

classmate

Data
Page

Unit - 4

Active filters & Convertors
ADC · DAC.

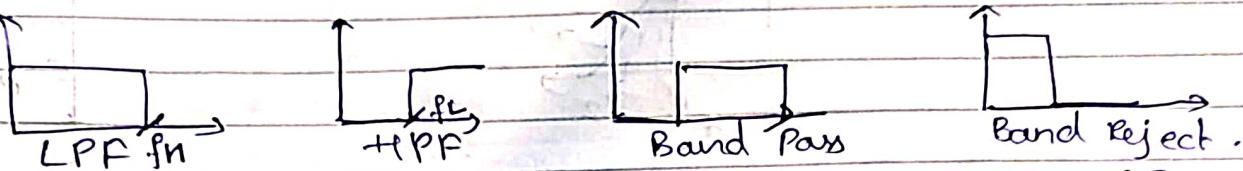


Filters
Passive Active


$$X_L = 2\pi f L$$

$$X_C = \frac{1}{2\pi f C}$$



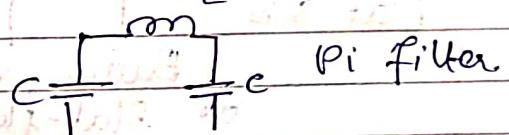
Filters (Type of f)
Act. poles. LPF NPF. Band Pass Band Reject



Passive

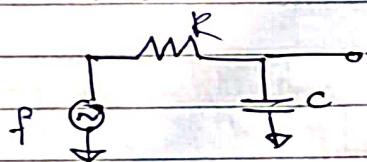


Active

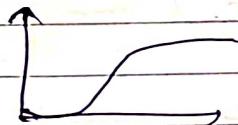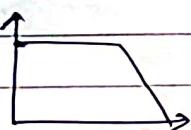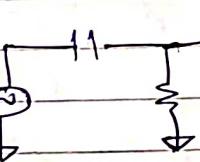

- Voltage drop
- Circuit would get loaded
- \rightarrow L → eddy current losses.



Active:

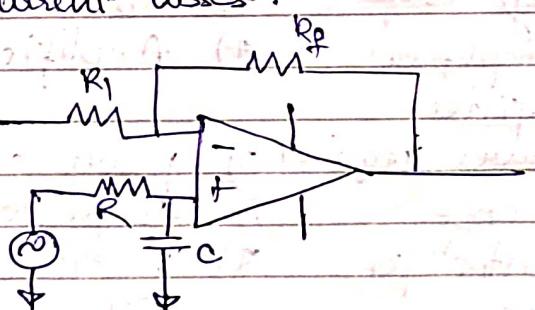

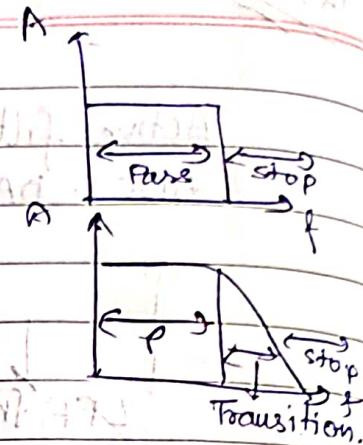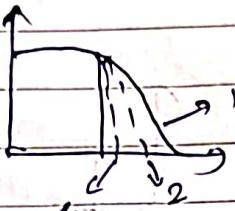- 1) S/p impedance ↑
- 2) No loading effect.
- 3) Amplification along with filtering.
- 4) No 'L'. No eddy current losses.


* On the basis of order.

→ Higher the order, better is the performance.



i) Alignment curve:


Flat P.B.
Flat S.B.

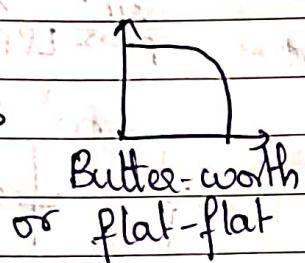


Flat P.B.
Rippled S.B.

Chebyshov

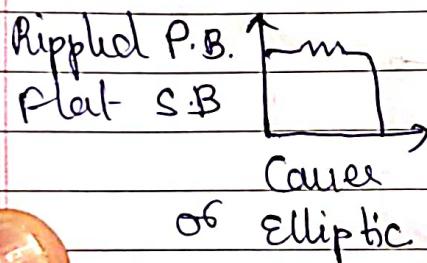Roll off Rate
-20dB / decade.
-6dB / octave



Passive	Active
1) R, C, L	1) R, C (good stability)
2) Loading	2) No loading limitation
3) Voltage drop	3) No "ringing" problem
4) No amplification with filter	4) Amplification with filter
5) No power required	5) power req.
6) low cost	6) high cost.
7) No restriction for f usage	7) Restriction for f usage. (S.R. is a criteria).
8) Diag.	8) Diag.
9) Eddy current losses	9) No Eddy current losses.

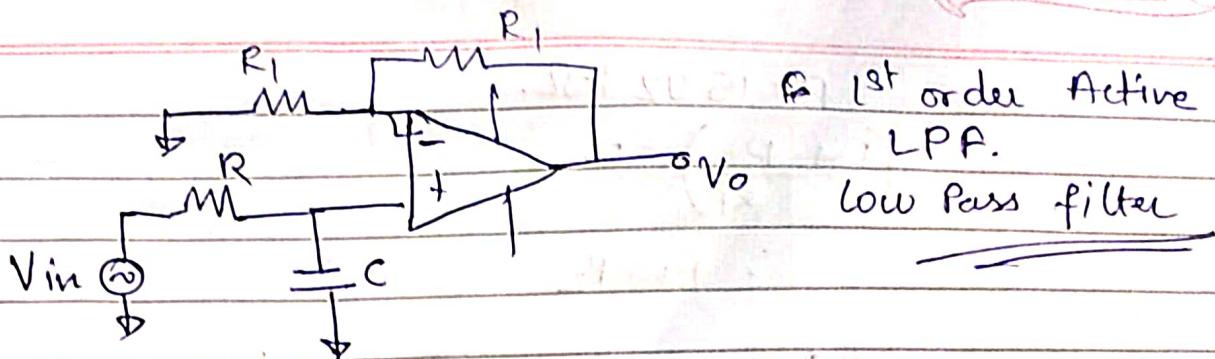

$$f_p = \frac{1}{2\pi RC}$$

$$v' = -X_C V_{in}$$

$$v' = \frac{-1}{j2\pi f C} V_{in}$$

$$R + \frac{1}{j2\pi f C}$$

$$v' = \frac{V_{in}}{R_j 2\pi f C + 1}$$


Assume $f = f_p$.

$$A_f = \frac{A}{(1 + j f/f_p)}$$

$$A_f = \frac{A}{\sqrt{1 + f^2/f_p^2}}$$

$A_f \rightarrow$ gain with f

$A \rightarrow$ gain without f .

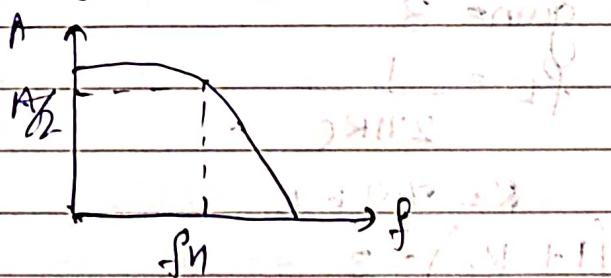

Q Design a 1st order L.P.F for cutoff freq 1 kHz. Assume $C = 0.01 \mu F$

soln: $f_p = 1 \text{ kHz}$ Pass bound gain = 2. Draw freq response



$$f_p = \frac{1}{2\pi RC}$$

$$R = \frac{1}{2\pi 10^3 \times 0.01 \times 10^{-6}}$$

$$R = 15.92 \text{ k}\Omega.$$

$$\left(1 + \frac{R_2}{R_1}\right) = 2$$

$$\therefore R_1 = R_2$$

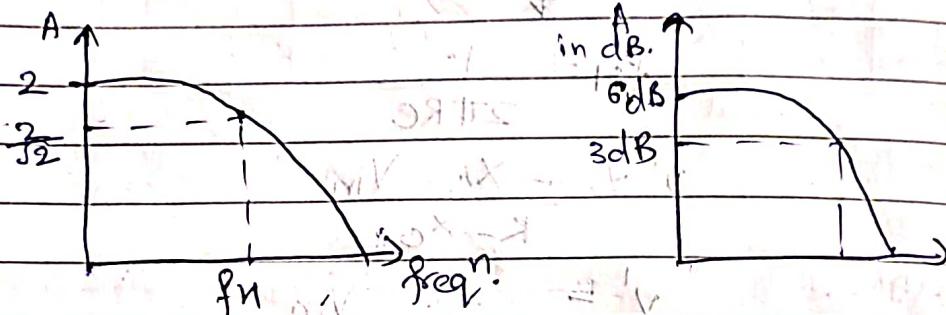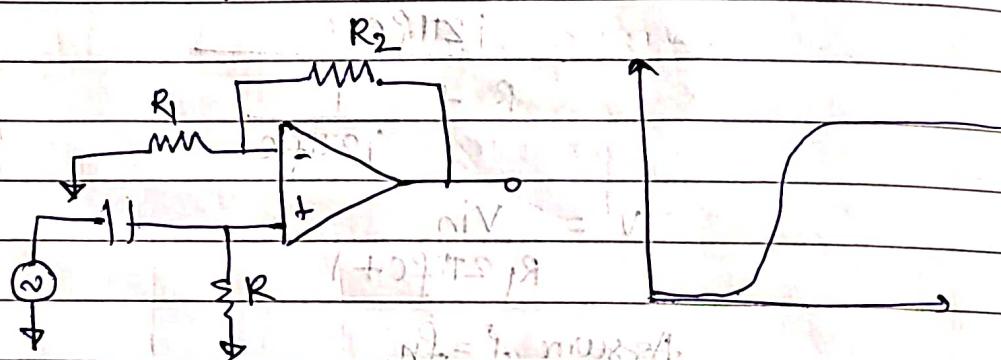~~HPF~~~~1st order.~~

$$A_{\text{pass}}/f_p = \frac{1}{2\pi RC}$$


- Q. Design 1st HPF for cutoff freqn = 2 kHz. Assume C = 0.01 μF
Pass band gain = 3

Soln:


$$f_p = \frac{1}{2\pi RC}$$

$$R = 7.9 \text{ k}\Omega$$

$$\left(1 + \frac{R_2}{R_1}\right) = 3$$

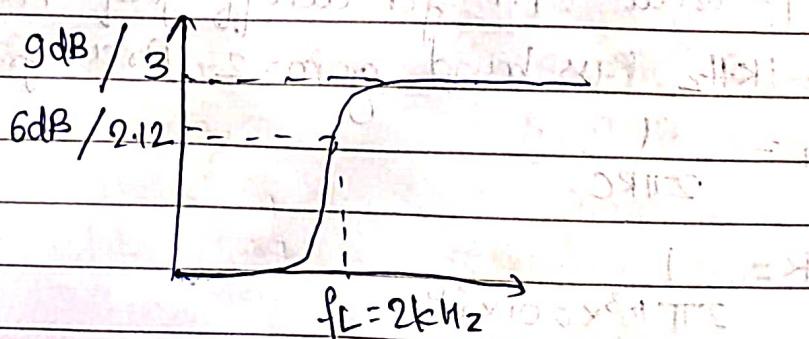


x) BPF

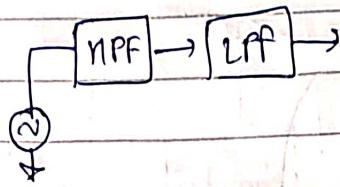

Q. Design a BPF for $f_L = 400\text{Hz}$ and $f_H = 4\text{kHz}$, Pass band gain = 5
Draw freq'n response. Calculate the bandwidth. Assume $C = 0.01\mu\text{F}$

Soln:

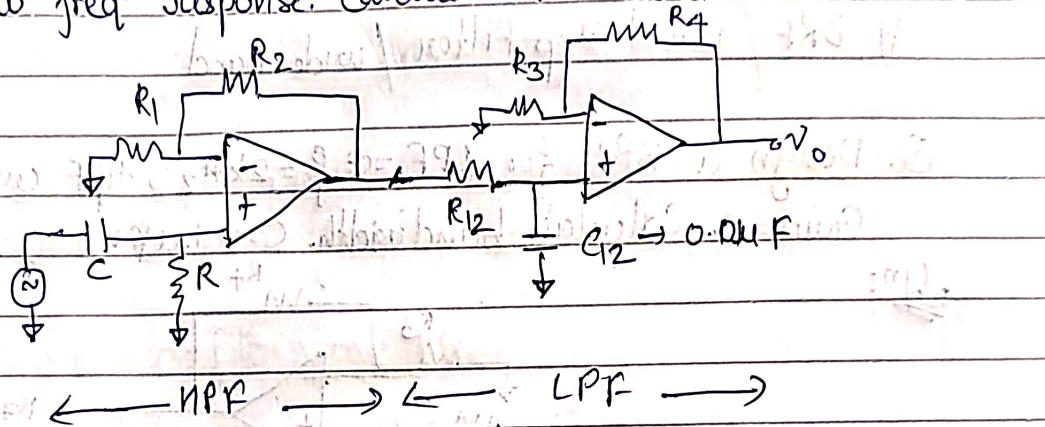

$\leftarrow \text{NPF} \rightarrow \leftarrow \text{LPF} \rightarrow$

$$f_L = \frac{1}{2\pi RC}$$

$$400 = \frac{1}{2\pi R \times 10^{-8}}$$

$$R = \frac{1 \times 10^8}{2512}$$

$$R = 39.8 \text{ k}\Omega$$

$$f_H = 4\text{kHz}$$

$$f_H = \frac{1}{2\pi R_C}$$

$$R_{12} = \frac{1 \times 10^8 \times 4 \times 10^3 \times 10^{-8}}{2 \times \pi \times 4 \times 10^3 \times 10^{-8}}$$

$$= \frac{1}{25.12 \times 10^5}$$

$$= 8.98 \text{ k}\Omega$$

$$1 + \frac{R_2}{R_1} = 2.23$$


$$\frac{R_2}{R_1} = 1.23 \quad R_1 = 1 \text{ k}\Omega$$

$$R_2 = 1.23 \text{ k}\Omega$$

$$R_3 = 1 \text{ k}\Omega$$


$$R_4 = 1.23 \text{ k}\Omega$$

998 (V)

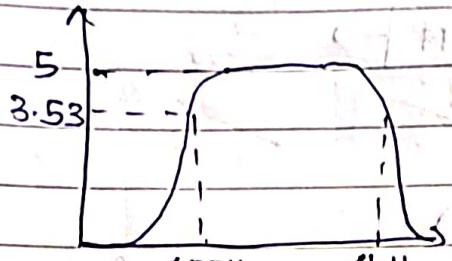

*1) BRF / Band stop filter / wide band

Q. Design a BRF for LPF cut off $f = 2\text{kHz}$ & HPF cut off $= 4\text{kHz}$.
Gain = 2. Calculate bandwidth. $C = 0.1\mu\text{F}$.

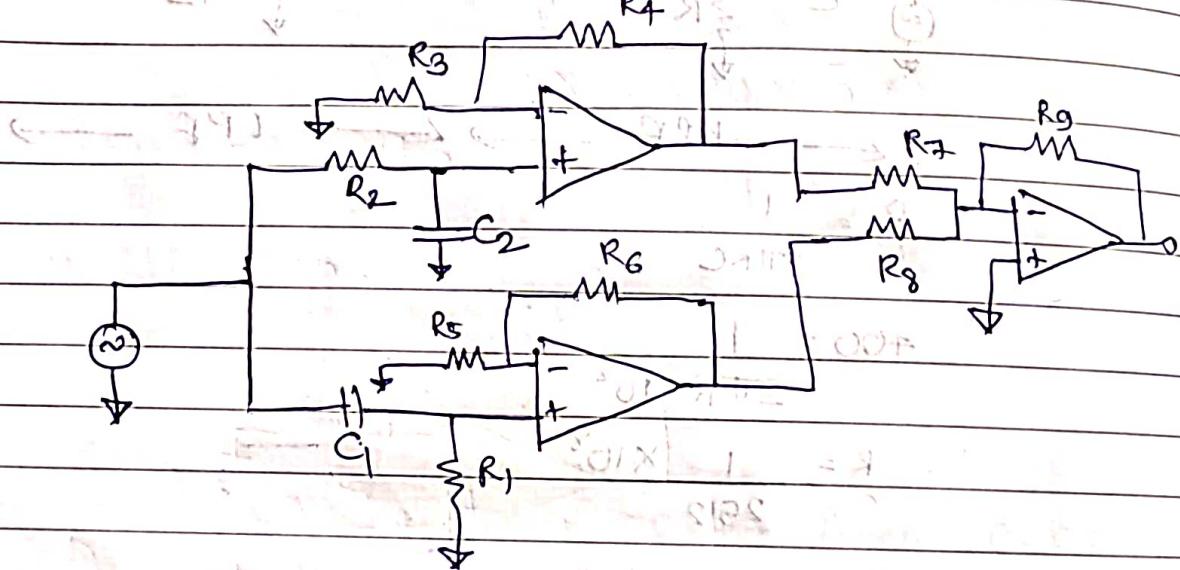Soln:

$$R_3 = R_4 = R_5 = R_6 = 1\text{k}\Omega.$$

$$R_1 = \frac{1}{2\pi f_L C} = \frac{1}{2\pi \times 10^4 \times 4 \times 10^{-6}} = 398\text{ }\Omega$$

$$= \frac{1 \times 10^4 \times 4 \times 10^{-6}}{2\pi \cdot 12} = 398\text{ }\Omega$$

$$= 398\text{ }\Omega$$

$$R_2 = \frac{1}{2\pi f_H C} = \frac{1}{2\pi \times 80 \times 4 \times 10^{-6}} = 398\text{ }\Omega$$

$$f_C = \sqrt{f_L f_H} = \sqrt{20 \times 80} = 40\text{ Hz}$$


$$= 89.44\text{ Hz.}$$

$$x) Q = \frac{f_C}{BW} = \frac{f_C}{f_H - f_L}$$

$$f_C = \sqrt{f_H \cdot f_L}$$


$Q < 10 \rightarrow \text{wide band.}$

$Q > 10 \rightarrow \text{narrow}$

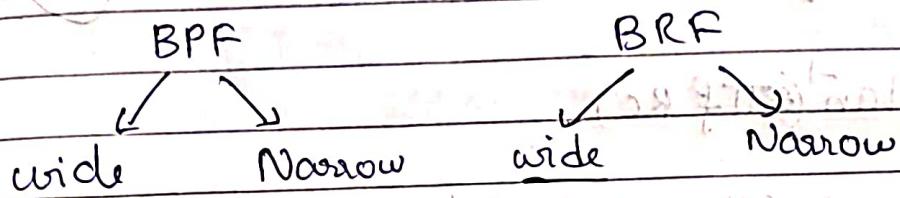

*) Narrow BRF. / Notch Filter:

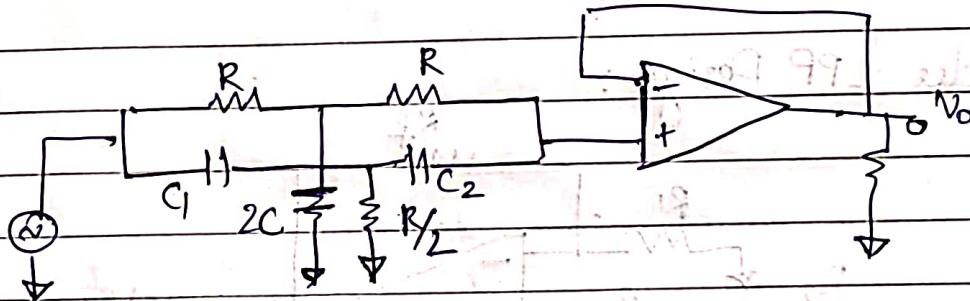Q. Design a Notch filter for 50 Hz.
SOL: Twin 'T' N/W.



$$50 = \frac{1}{2\pi RC}$$


$$R = \frac{1}{2\pi \times 50 \times 0.068 \times 10^{-6}}$$

$$= \frac{1}{1.1 \times 10^6} = 2.7352$$


$$= 46.8 \text{ k}\Omega$$

$$R_1 = 23.4$$

$$2C = 0.12 \mu F$$

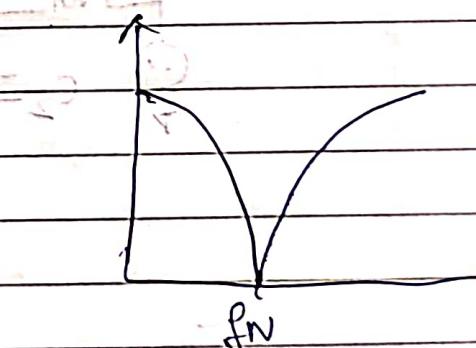

* All pass

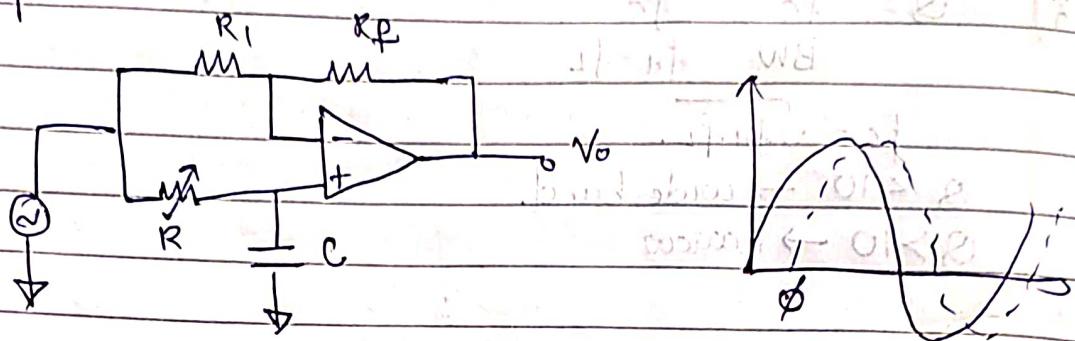


$$\theta = -2 \tan^{-1}(\omega f RC)$$

Q. Design All pass filter Calculate phase angle for a all pass filter whose freq. of input is 1KHz. $R = 15.91\text{k}\Omega$

Soln:

$$\theta = -2 \tan^{-1}(2 \times \pi \times 15.91 \times 10^3 \times 10^{-8} \times 10^3) = -89.6^\circ$$

* 2nd order LPP Design:

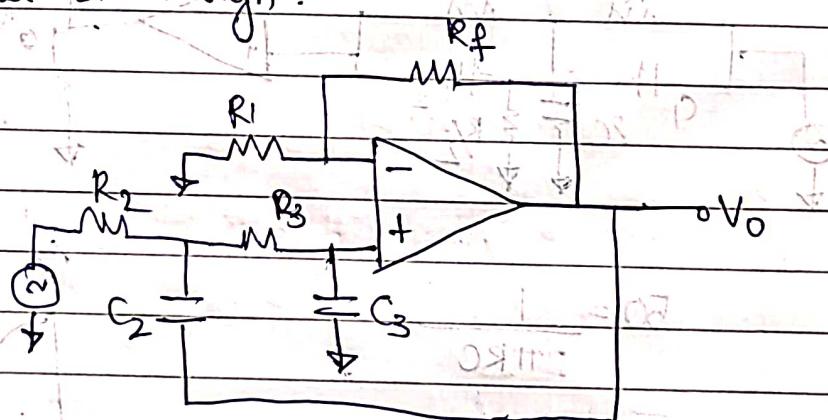

$R_2 = R_3 = R$ equal component

$C_2 = C_3 = C$ version.

$$f_0 = \frac{1}{2\pi\sqrt{R_2 R_3 C_2 C_3}}$$

damping factor $\alpha = \frac{\sqrt{2}}{Q}$ $Q = \frac{1}{\alpha}$

$$A = 3 - \alpha \cdot 9.18 \approx 28$$

Q. Design a 2nd order LPF for cutoff freqn 1 kHz. Assume C = 0.01 μF. Pass band gain = 2.

Sol:

$$R_2 = R_3 = R$$

$$C_2 = C_3 = C$$

$$f_n = \frac{1}{2\pi RC}$$

$$R = \frac{1}{2\pi \times 10^3 \times 10^{-8}}$$

$$= 15.9 \text{ k}\Omega$$

$$A = 3 - \alpha$$


$$= 3 - 1.414$$

$$= 1.586$$


$$1 + \frac{R_f}{R_i} = 1.586$$

$$\frac{R_f}{R_i} = 0.586$$

$$R_f = 0.586 \text{ }\Omega$$

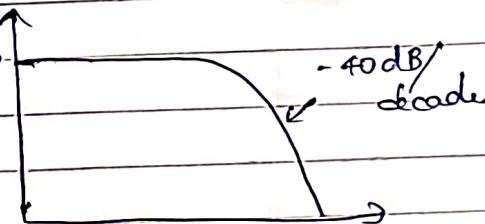

x) 2nd order HPF:

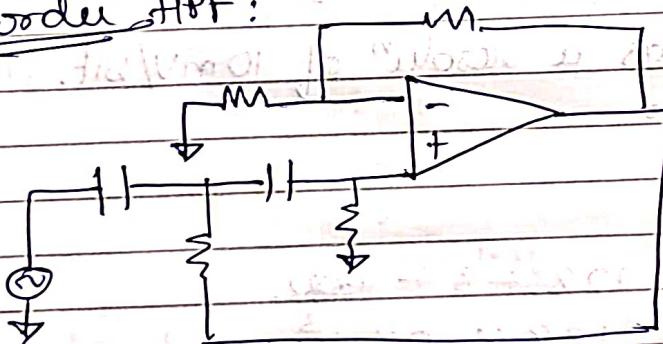

x) DAC

Digital to Analog converter.

→ Binary weighted

→ R to 2R.

Binary - wide range of resistors is required.

Q. A 4 bit DAC uses a reference of 5V. Calculate corresponding Analog voltage. Digit $i/p = (1011)_2$.

Soln:

$$Res = \frac{V_{ref}}{2^n - 1}$$

$$= \frac{5}{2^4 - 1} = \frac{5}{15} = 0.33 \text{ mV/bit}$$

$$= \frac{5}{15} = \frac{1}{3} = 0.33 \text{ mV/bit}$$

$$(1011)_2 = (11)_10$$

$$= 11 \times 0.33$$

$$= 3.66 \text{ V}$$

$$(1111)_2 = (15)_10$$

$$= 15 \times 0.33 = 4.95 \text{ V}$$

$$= 4.95 \text{ V}$$

$$(0001) = (1)_10$$

$$= 0.33 \text{ V.}$$

Q. An 8-bit DAC has a resolution of 10mV/bit. Find Analog O/P voltage for i/p's

a) 10001010

b) 00010000

Soln: a) $(10001010)_2 = 128 + 8 + 4 + 2 = 138 \times 10 \times 10^{-3}$

$$= 138 \times 10^{-2}$$

$$= 1.38 \text{ V}$$

b) $2^4 = 16 \times 10^{-2}$

$$= 0.16 \text{ V.}$$

c) $(11110000)_2 = 240 \times 10^{-2}$

$$= 2.4 \text{ V.}$$

d) $(00001111)_2 = 8 + 4 + 2 + 1$
 $= 15 \times 10^{-2}$
 $= 0.15 \text{ V.}$

e) $(10101010)_2 = 128 + 32 + 8 + 2$
 $= 1.7 \text{ V}$

Q. 8 bit DAC has a voltage range 0 to 2.55 V. Find resoln.

Soln: $R_{\text{es}} = \frac{V_{\text{ref}}}{2^8 - 1}$

$$= \frac{2.55}{255} \quad \text{minimum possible value}$$

$$= 0.01 \text{ V/bit}$$

$$V_{\text{es}} = 10 \text{ mV/bit.}$$

$$R_{\text{es}} = \frac{5}{255}$$

$$= 19 \text{ mV/bit.}$$

Q. A 4 bit R-2R ladder in/w uses resistors $R = 10 \text{ k}\Omega$ $2R = 20 \text{ k}\Omega$.
 Uses $V_R = 10 \text{ V.}$ a) find the resoln of the converter.

Soln: $R_{\text{es}} = \frac{10}{2^4 - 1}$

$$= \frac{10}{15}$$

$$= 0.66 \text{ V/bit.}$$

b) Find I_o for Digital i/p 1101.

$$(1101) = 13$$

$$= 13 \times 0.66$$

$$= 8.58 \text{ V.}$$

$$I_o = 8.58$$

Q.) ADC :

Analog to Digital converter.


- Flash ADC - hardware becomes complex as no. of bits per register.
- Successive approximation converter (SAR).

Comparators - $2^n - 1$

Resistors - 2^n

Black Box - Priority encoder.

2-Bit Flash
ADC

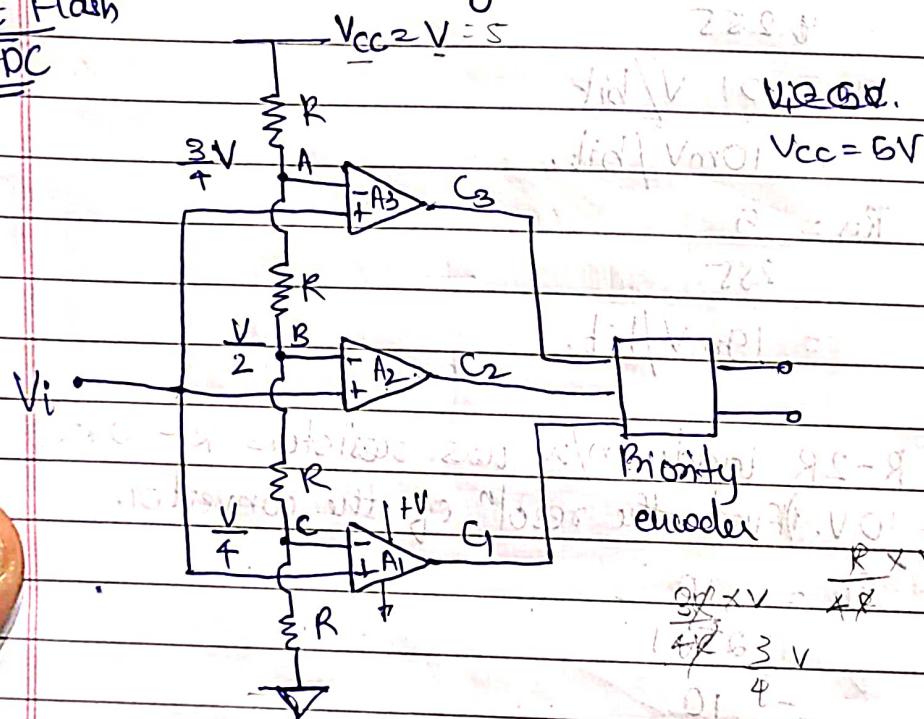

Vi

$$0 \leq Vi \leq 1.25$$

$$1.25 \leq Vi \leq 2.5$$

$$2.5 \leq Vi \leq 3.75$$

$$3.75 \leq Vi \leq 5$$

G1, G2, G3

0

0

0

0

0

0

C1, C2, C3

1

1


1

1

1

1

i) SAR type ADC:

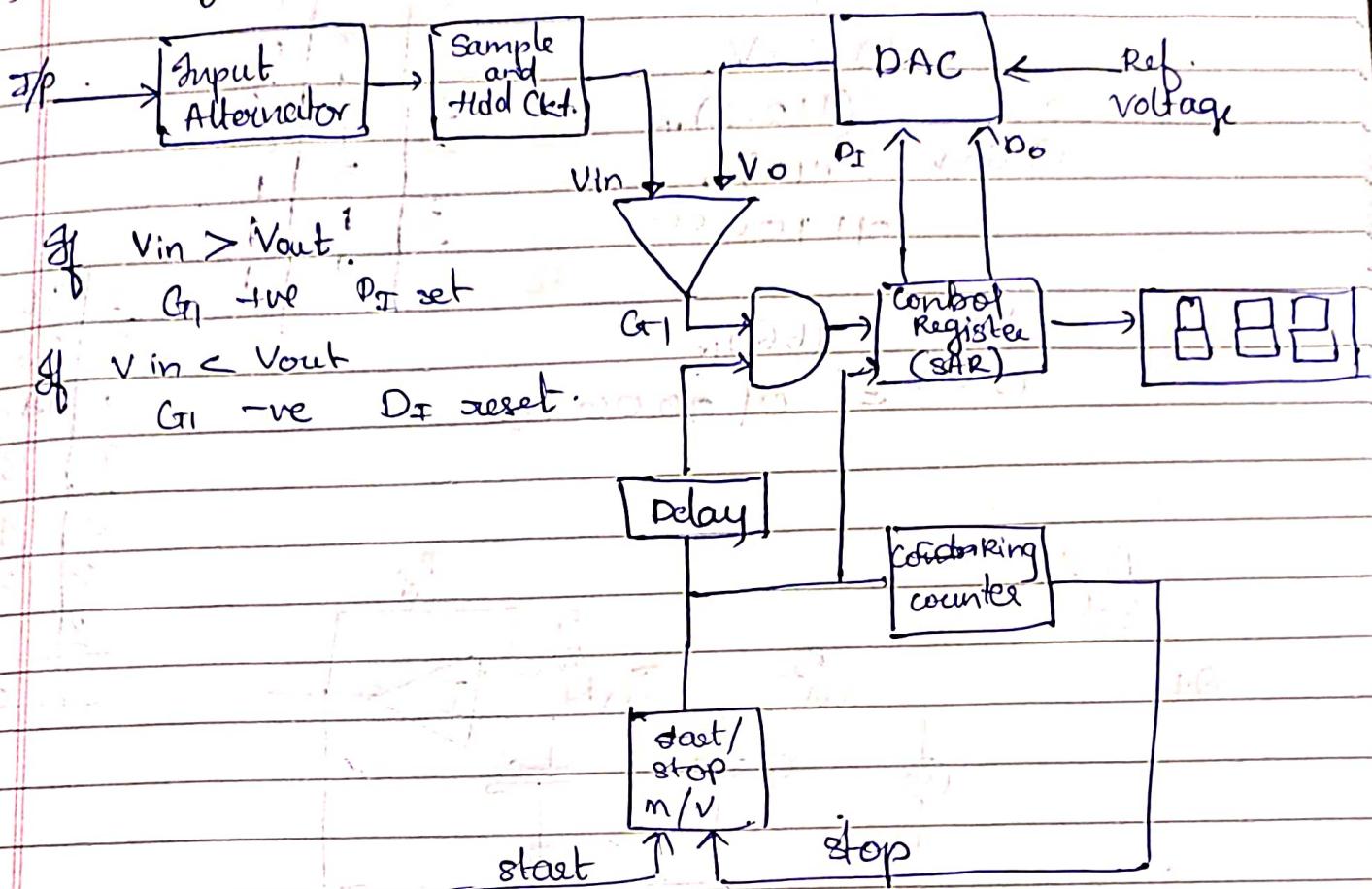

1000

1100 or 0100

Q. An 8-bit ADC accepts i/p voltage in range of 0 to 10V.

a) Minimum voltage req. to cause 1 LSB change. (Ans 39.1mV)

b) What i/p range would cause ADC to become all 1

(Ans : 10 - 39.1mV).

c) What is the digital o/p for i/p 4.8 V.

$$\text{Soln: } d) \frac{4.8}{\text{Resolu}} = \frac{4.8}{39.2 \text{mV}} = (122.44)_{10}$$

$$\begin{aligned} 4.8 &= (122)_{10} \\ &= 10111010 \end{aligned}$$

$$\begin{aligned} \frac{3.6}{39.2 \text{mV}} &= (92.3)_{10} \\ &= (92)_{10} \end{aligned}$$

2	122	0
2	61	0
2	30	1
2	15	0
2	7	1
2	3	1
2	2	1
2	1	0
	0	1

Q.

$$R_{\text{out}} = \frac{5}{2^8 - 1}$$

$$= 19.6 \text{ mV}$$

$$2.2 = (112.2)_{10}$$

$$19.6 \text{ mV} = (12)_{10}$$

$$= 01110000$$

$$1.3 = (66)_{10}$$

$$19.6 \text{ mV} = 01000010$$


2	112	2
2	56	0
2	28	0
2	14	0
2	7	0
2	3	1
2	1	1
	0	1

$$19.6 \text{ mV} = 01110000$$

A-2

Set 1

Q.1

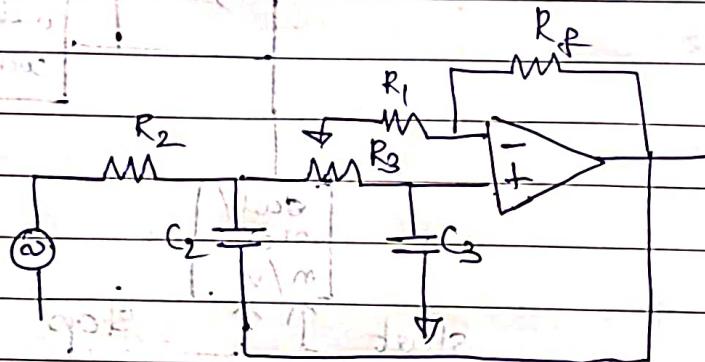

$$f_H = \frac{1}{2\pi R C} \quad R_2 = R_3 = R \quad C_2 = C_3 = C$$

$$R = \frac{1}{2\pi f_H C}$$


$$R = \frac{1}{2\pi f_H C} = \frac{1}{2\pi \times 10^3 \times 10^{-8}} = 1.59 \text{ k}\Omega$$

$$R = \frac{1}{2\pi f_H C} = \frac{1}{2\pi \times 10^3 \times 10^{-8}} = 1.59 \text{ k}\Omega$$

$$A = 3 - \alpha = 1 + \frac{R_f}{R_i} \quad \text{Assume } R_i = 1 \text{ k}\Omega$$

$$A = 1.586 \quad \text{Assume } R_i = 1 \text{ k}\Omega$$
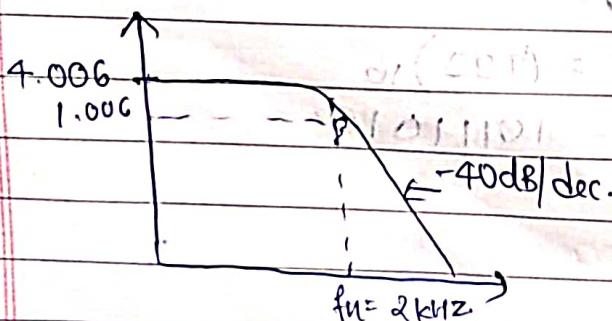
$$A = 1.586 = 1 + \frac{R_f}{R_i} \quad R_f = 1.586 \times 10^3 \text{ k}\Omega$$




$$0.586 = \frac{R_f}{10^3}$$

$$R_f = 0.586 \text{ k}\Omega \quad R_f = 586 \text{ }\mu\text{V}$$

Set 2

Q.1

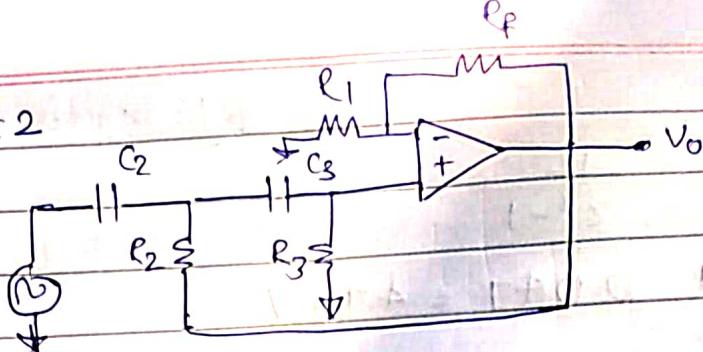

$$\alpha = \sqrt{2}$$

(B.W.)

$$C_2 = C_3 = 0.047 \times 10^{-6} F.$$

$$R_2 = R_3 = 3.3 \times 10^3 \Omega.$$

$$R_1 = 2.7 \times 10^3 \Omega \quad R_f = 15.8 \times 10^3 \Omega.$$

$$f_L = \frac{1}{2\pi R_2 R_3 C_2 C_3}$$


$$1 + \frac{15.8 \times 10^3}{2.7 \times 10^3}$$

$$f_L = \frac{1}{2\pi R C}$$

$$1.58 \cdot \\ 20 \log_{10}(1.58)$$

$$= \frac{1}{2\pi \times 3.3 \times 10^3 \times 0.047 \times 10^{-6}}$$

$$= 1.02 \text{ kHz}$$

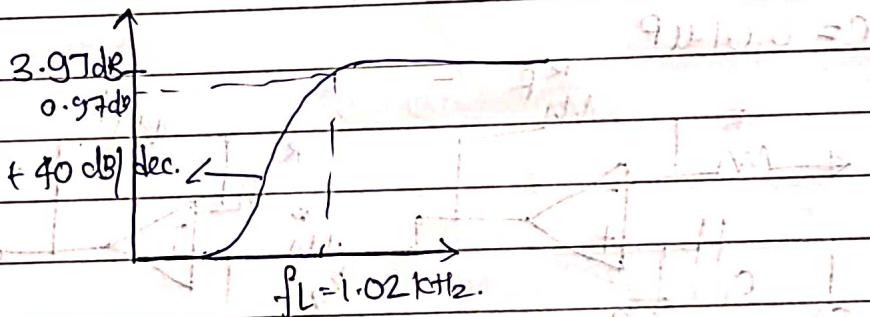

Q.2

~~$$R_{2^n} = \frac{V_{out}}{2^n - 1}$$~~

$$= \frac{10}{2^4 - 1}$$

$$= \frac{10}{15}$$

$$= 0.66$$

$$(1011)_2 = 1 \cdot 8 + 2 + 1$$

$$= 11 \times 0.66$$

$$= 7.26 V$$

$$(0110)_2 = 4 + 2$$

$$= 6 \times 0.66$$

$$= 3.99$$

Set 3

Q.2 a) Resolⁿ = $\frac{12}{2^{\text{Red}}} = \frac{12}{2^8 - 1}$
 $= 0.047 \quad 0.047 = 47 \text{ mV}$

b) $12 - 0.047$

$= 11.953 \text{ V}$

c) $\frac{6}{0.047} \approx (127.65)_{10}$

$= (128)_{10}$

$= (100000000)_2$.

2	28	
2	64	0
2	32	0
2	16	0
2	8	0
2	4	0
2	2	0
2	1	0
0	1	1


Set 1.4

Q.1 $f_L = 400 \text{ Hz}$

$f_H = 2 \text{ kHz}$

$A = 2$

$C = 0.01 \mu\text{F}$

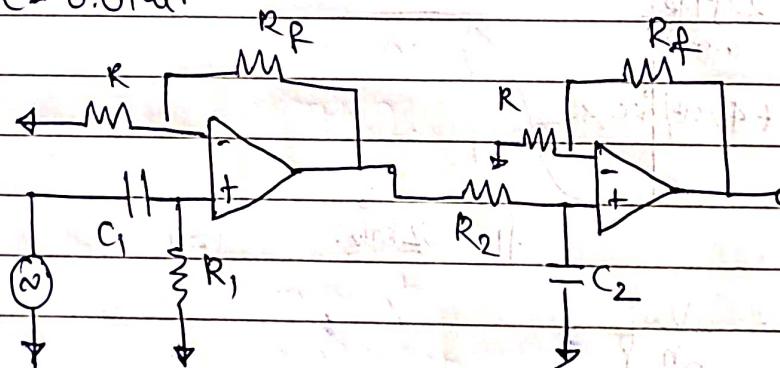

$$f_L = \frac{1}{2\pi R_1 C_1}$$

$$R_1 = \frac{1}{2\pi \times 400 \times 10^{-8}}$$

$$= 39.8 \text{ k}\Omega$$

$$1 + \frac{R_f}{R_2} = \sqrt{2}$$

$$1 + \frac{R_f}{R_2} = 1.414$$

Assume = $\frac{1 + R_f}{1 + R_2}$ $R = 1 \text{ k}\Omega$.

$$1.414 = 1 + \frac{R_f}{10^3}$$

$$0.414 = \frac{R_f}{10^3}$$


$$R_f = 414 \Omega$$

$$f_n = \frac{1}{2\pi R_2 C_2}$$

$$R_2 = \frac{1}{2 \times 3.14 \times 2 \times 10^3 \times 10^{-8}}$$

$$= \frac{1}{4 \times 3.14 \times 10^5}$$

$$R_2 = 7.9 \text{ k}\Omega$$

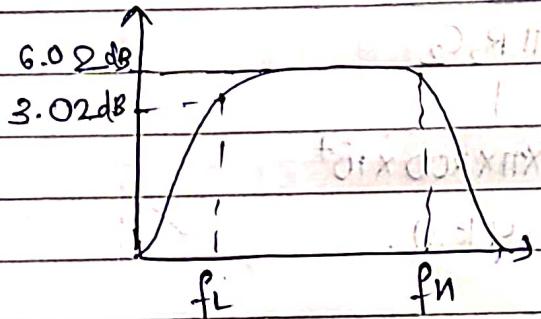

$$BW = 2(f_H - f_L) = 1600 \text{ Hz}$$

$$f_c = \sqrt{f_L \times f_H}$$

$$= 894.42 \text{ Hz}$$

$$Q = \frac{894.42}{1600}$$

$$Q = 0.559$$

$$Q.2. \quad Res = \frac{10}{2^t - 1}$$

$$= 0.66 \text{ V/bit}$$

$$(1001) = 8 + 1$$

$$= 9 \times 0.66$$

$$= 5.94 \text{ V}$$

$$(1110) = 8 + 4 + 2$$

$$= 14 \times 0.66$$

$$= 9.24 \text{ V}$$

Set 5


Q.1

$$f_H = 200\text{Hz}$$

$$f_{BL} = 2\text{kHz}$$

$$A = 1$$

$$C = 0.1\mu\text{F}$$

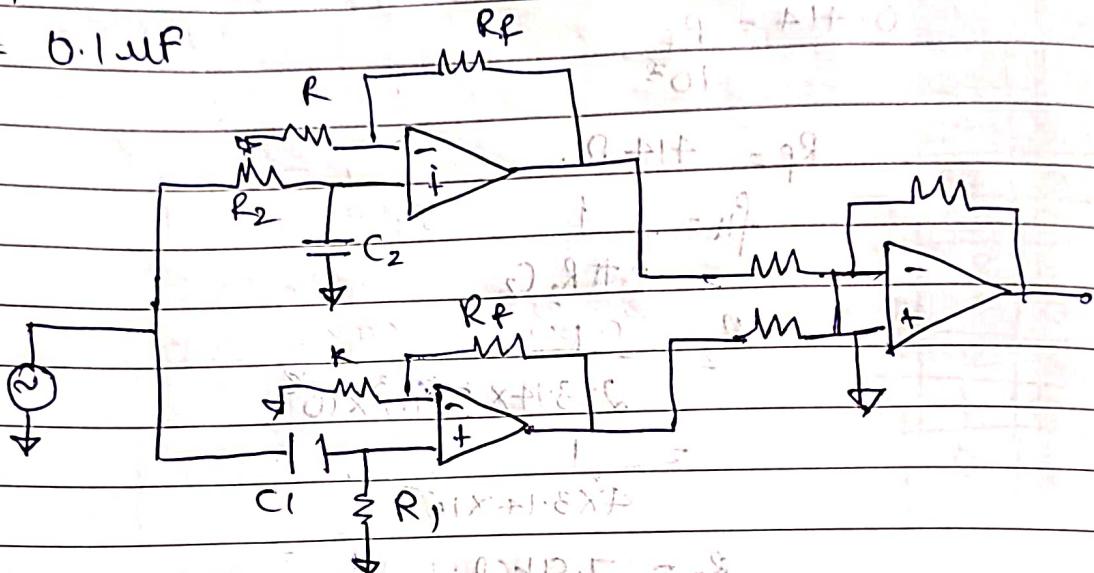

$$200 = \frac{1}{2\pi R_2 C_2}$$

$$R_2 = \frac{1}{2\pi \times 10^3 \times 200 \times 10^{-9}}$$

$$= 7.9\text{k}\Omega$$

$$R_1 = \frac{1}{2\pi \times 10^3 \times 0.1} = 0.79$$


$$= 0.79\text{k}\Omega$$

$$f_C = \sqrt{f_L f_H}$$

$$= 632.45$$

$$Q_C = 1 + \frac{R_f}{1k\Omega} = 1$$


$$R_f = 1\text{k}\Omega$$

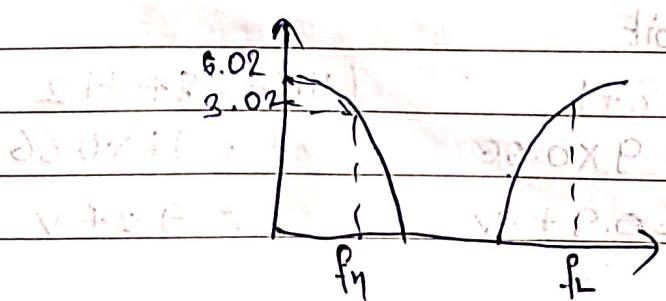

Q.2

$$f_N = 60 \text{ Hz}$$

$$C = 0.068 \mu\text{F}$$

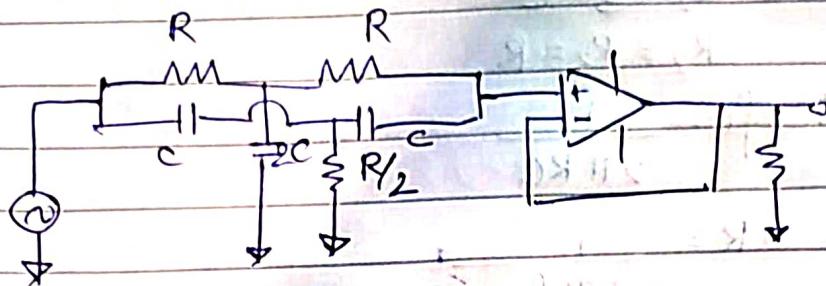

$$f_N = \frac{1}{2\pi RC}$$


$$R = \frac{1}{2\pi f_N C}$$

$$= \frac{1}{2\pi \times 60 \times 68 \times 10^{-9}}$$

$$= 39 \text{ k}\Omega$$

$$\frac{R}{2} = 19.5 \text{ k}\Omega$$

$$2C = 0.136 \mu\text{F}$$

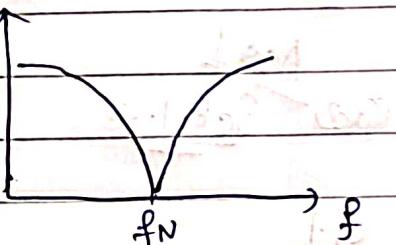

Get 1.6

Q.1

$$f_L = 1.5 \text{ kHz}$$

$$C = 0.01 \mu\text{F}$$


Assume it to be Butterworth filter.

$$\therefore \alpha = \sqrt{2}$$

$$\therefore A = 3 - \alpha$$

$$= 3 - 1.414$$

$$= 1.586$$

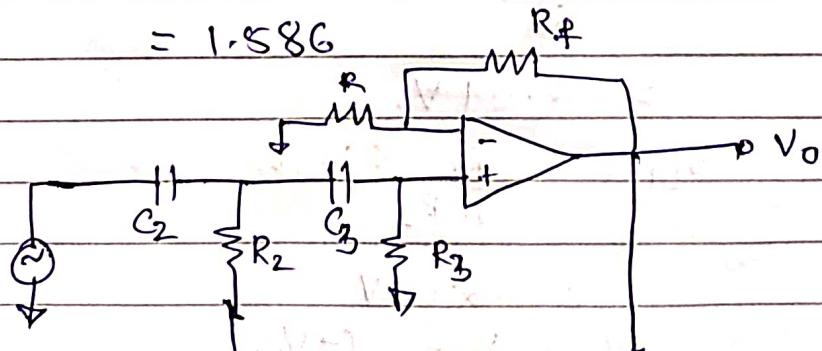

$$f_L = \frac{1}{2\pi R_2 R_3 C_2 C_3}$$

Assume $C_2 = C_3 = C$

$$R_2 = R_3 = R$$

$$\therefore f_L = \frac{1}{2\pi RC}$$

$$R = \frac{1}{2\pi f_L C}$$

$$= \frac{1}{2\pi \times 1.5 \times 10^3 \times 10^{-8}}$$

$$R = 10.6 \text{ k}\Omega$$

$$1 + \frac{R_f}{R} = 1.586$$


Assume $R = 1 \text{ k}\Omega$

$$R_f = 586 \text{ }\Omega$$

~~Ass 1~~

~~Q2 Set 1.4~~

Q.1

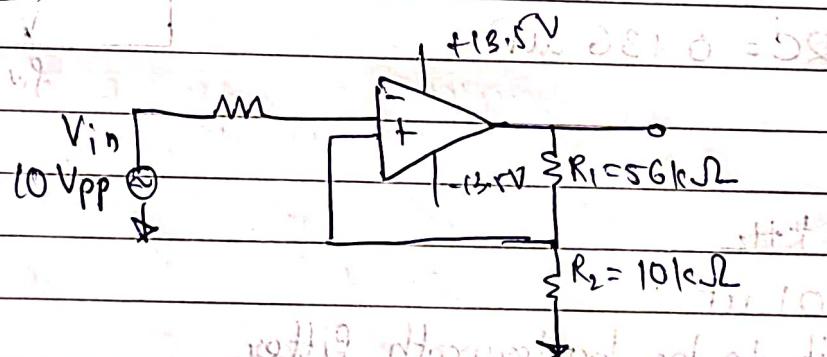

$$V_{out} = \frac{R_2}{R_1 + R_2} \times V_{sat}$$

$$2 \quad \frac{10 + 13.5}{56 + 10} = 8.66$$


$$= 2.04 \text{ V.}$$

$$V_{LT} = -\frac{R_2}{R_1 + R_2} \times V_{sat}$$


$$= -2.04 \text{ V}$$

$$V_n = V_{out} - (-V_{LT})$$

$$= 4.08 \text{ V.}$$


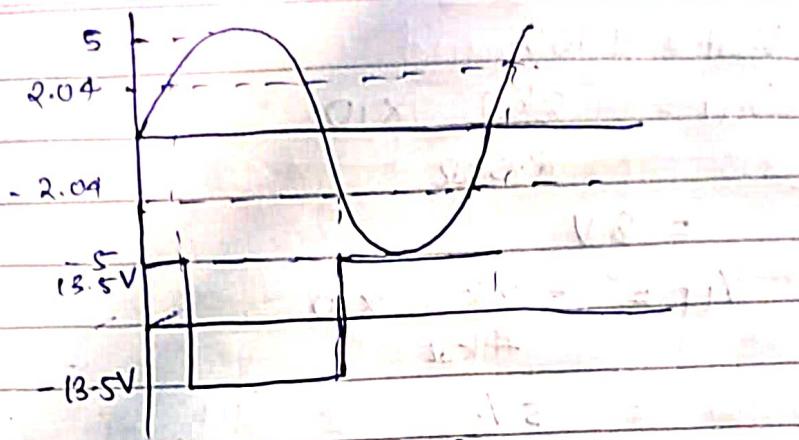


Q.2

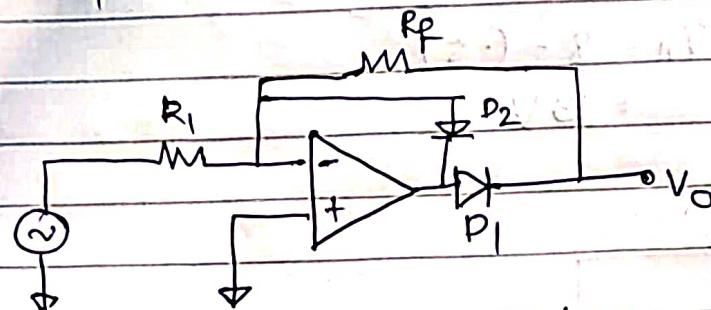


$$A = \frac{R_f}{R_1} = 8$$

$$\therefore R_f = 8 k\Omega \quad R_1 = 1 k\Omega$$

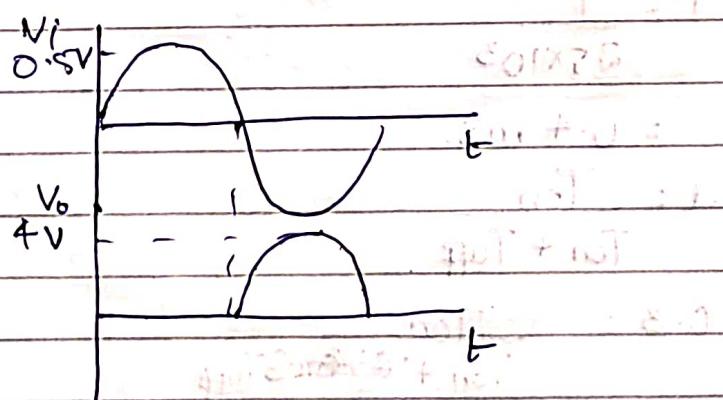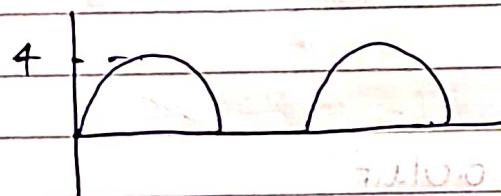

Set 1.5

Q.1

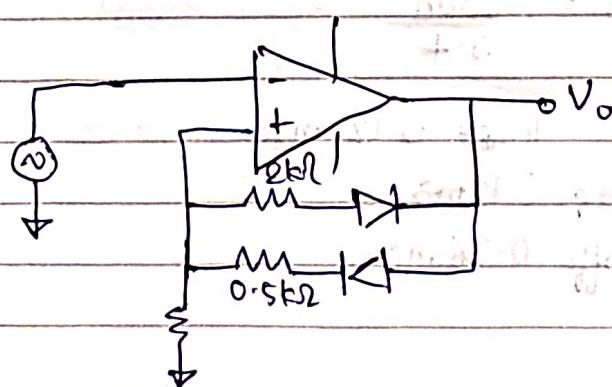


$$V_{sat} = \pm 10V$$

$$V_{LT} = \frac{2k\Omega}{2.5k\Omega} \times 10 \\ = 8V$$

$$V_{LT} = -\frac{2k\Omega}{4k\Omega} \times 10 \\ = -5V$$

$$V_n = 8 - (-5) \\ = 13V$$

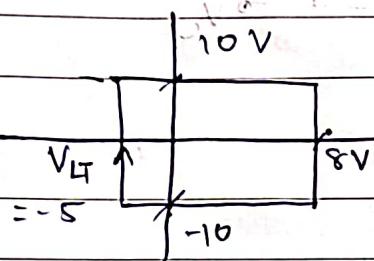

Q.2

$$f_0 = 2.8 \text{ kHz}$$

$$\text{D.C.} = 30\%$$

$$B = 0.5$$

$$R_i = 10 \text{ k}\Omega$$

$$C = 0.1 \mu\text{F} \quad C_p = 0.01 \mu\text{F}$$

$$T = \frac{1}{2.5 \times 10^3}$$

$$= 0.4 \text{ ms.}$$


$$\text{D.C.} = \frac{T_{on}}{T_{on} + T_{off}}$$

$$0.3 = \frac{T_{on}}{T_{on} + 0.4 \text{ ms} T_{off}}$$

$$0.3 = \frac{T_{on}}{0.4}$$

$$T_{on} = 0.12 \text{ ms}$$


$$T_{off} = 0.28 \text{ ms}$$

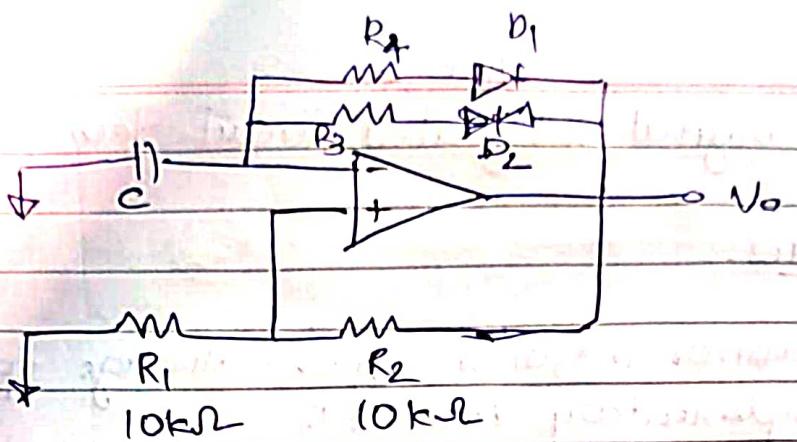

$$T_{on} = R_3 C \ln \left(\frac{1+\beta}{1-\beta} \right) (+V_{sat})$$

$$R_3 = ?$$
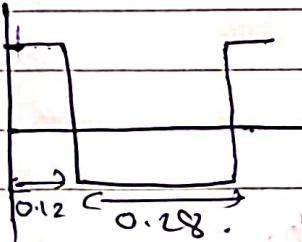
$$T_{off} = R_4 C \ln \left(\frac{1+\beta}{1-\beta} \right) (-V_{sat}).$$



28/11/22

classmate

Date _____

Page _____

Unit-5

Digital Integrated Circuit Technology & Convertors.

f) Logic Families:

- 1) TTL - transistor-transistor logic. - Average speed & power consumption.
- 2) CMOS - Complementary MOSFET.
- 3) ECL - Emitter coupled logic - speed.

CMOS is the best when Power consumption has to be less.

f) Types of TTL

- Standard
- High speed
- Low Power
- Schottky.

3-configuration at the output,

- Totem-Pole
- Open Collector
- Tristate

f) Finite State Machine:

- Mealy
- Moore machine representation.

Mealy

Moore

- | | |
|--------------------------------|------------------------------|
| 3) less no. of states required | 3) More states are required. |
| 4) Complex difficult to design | 4) Easy to design. |
| 5) More hardware. | 5) Less hardware. |


f) To solve

- 1) Draw state diagram.
- 2) Draw state table.
- 3) Solve qf eqⁿ using kernel map.

4) Draw the ckt.

Q. Determine the sequence for 101 using Mealy form.

Ans: Let S_0 be the initial state.

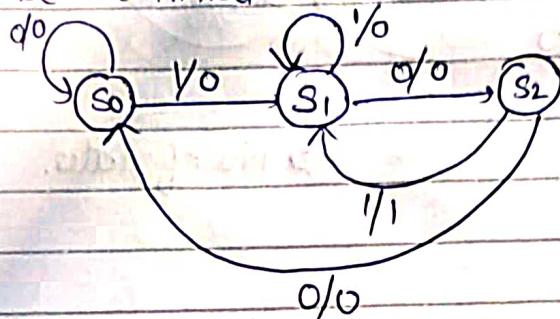

State Table

PS	I/P	NS	O/P.
$Q_1 \ Q_0$	x	$Q_1^+ \ Q_0^+$	y
0 0	0	0 0	0
0 0	1	0 1	0
0 1	0	1 0	0
1 0	0	0 1	0
1 0	1	0 0	1


$$y = Q_1 \bar{Q}_0 x$$

$2^N = 3 \rightarrow N - \text{no. of flip flop.}$

no. of states.

Q: 1001. Design the ckt diag. to determine the seq. using mealy Psm.

Q. 110

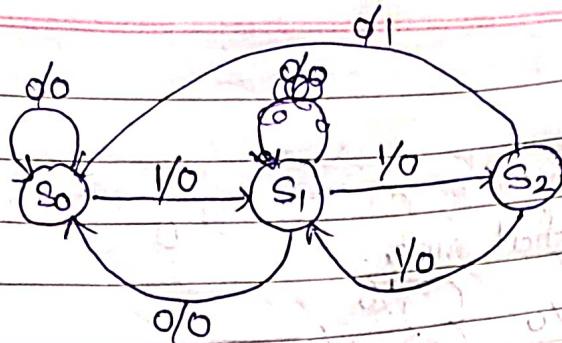

State Table

$S_0 \rightarrow 00$

$S_1 \rightarrow 01$

$S_2 \rightarrow 10$

$2^N \geq \text{No. of states.}$

PS	x	NS	y	FF.
Q_B	Q_A	x	Q_B^+ Q_A^+	D_B DA
0	0	0	0 0	0 0
0	0	1	0 1	1 0
0	1	0	0 0	0 1
0	1	1	1 0	1 0
1	0	0	0 0	0 0
1	0	1	0 1	0 1
1	1	0	1 0	0 0
1	1	1	1 1	0 0

D_B	Q_B	Q_A	DB	Q_B	Q_A	DB	Q_B	Q_A	DB
0	000	01110	0	01	01110	0	1	00	0
1	000	01110	1	02	11110	1	1	00	0
0	000	01110	0	12	11110	0	0	01	1
1	000	01110	1	00	01110	1	0	01	1


$DB = x \cdot Q_A$

$DA = x \cdot \bar{Q}_A$


$DB = x \cdot Q_A$

$DA = \bar{x} \cdot Q_A$

$y = Q_B \cdot S_A$

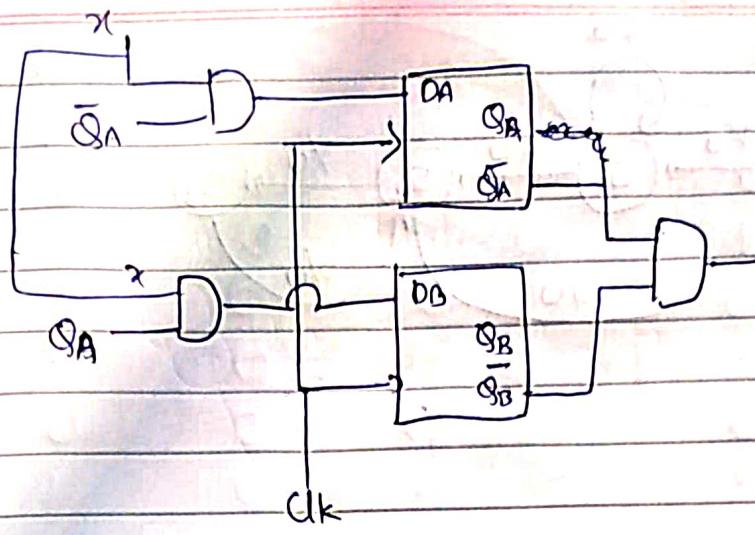

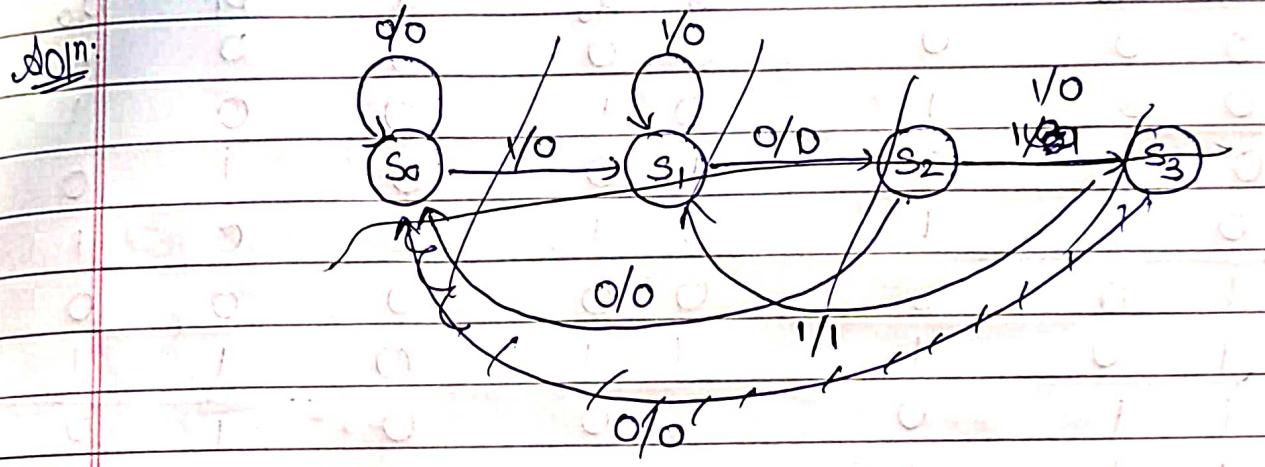Q. Design a mealy type fsm to detect a seq. 1011.




$$S_0 \rightarrow 001$$


$$S_1 \rightarrow 01$$

$$S_2 \rightarrow 10$$

$$S_3 \rightarrow 11$$

PS

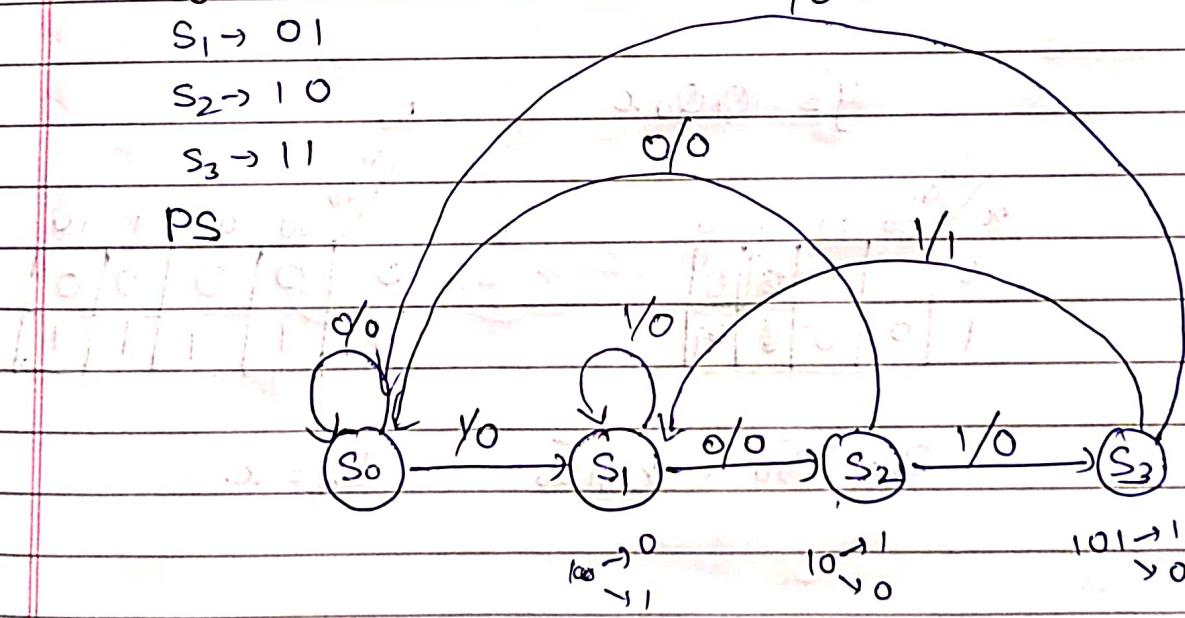

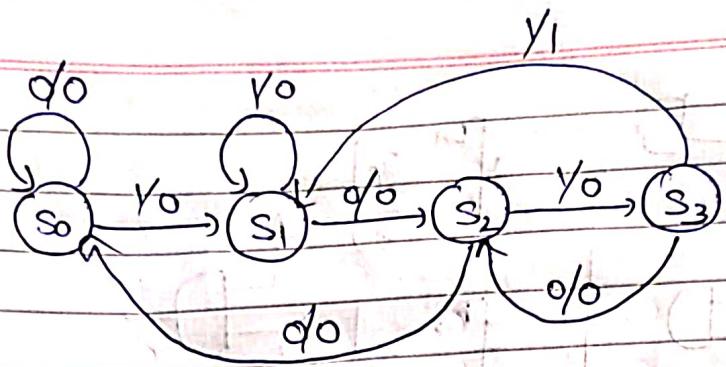

$$S_0 \rightarrow 00$$

$$S_1 \rightarrow 01$$

$$S_2 \rightarrow 10$$

$$S_3 \rightarrow 11$$

PS		x		Q ₁ ⁺ Q ₀ ⁺		y		D ₁	D ₀
Q ₁	Q ₀	x		0	0	0	0	0	0
0	0	0		0	0	0	0	0	1
0	0	1		0	1	0	0	0	1
0	1	0		1	0	0	1	0	0
0	1	1		0	1	0	0	0	1
1	0	0		0	0	0	0	0	0
1	0	1		1	1	0	1	1	1
1	1	0		1	0	0	1	1	0
1	1	1		0	1	100	0	0	1


$$y = Q_1 Q_0 x$$

D ₁ Q ₁		Q ₀ 00		01		11		10	
x		0	1	0	1	0	1	0	1
0	0	0	1	0	1	0	1	0	1
1	0	0	0	1	0	1	0	1	1


D ₀ Q ₀		11		10	
Q ₁	Q ₀	00	01	11	10
0	0	0	0	0	0
1	1	1	1	1	1

$$D_1 = \bar{x} Q_0 + x Q_1 \bar{Q}_0$$


$$D_0 = x.$$

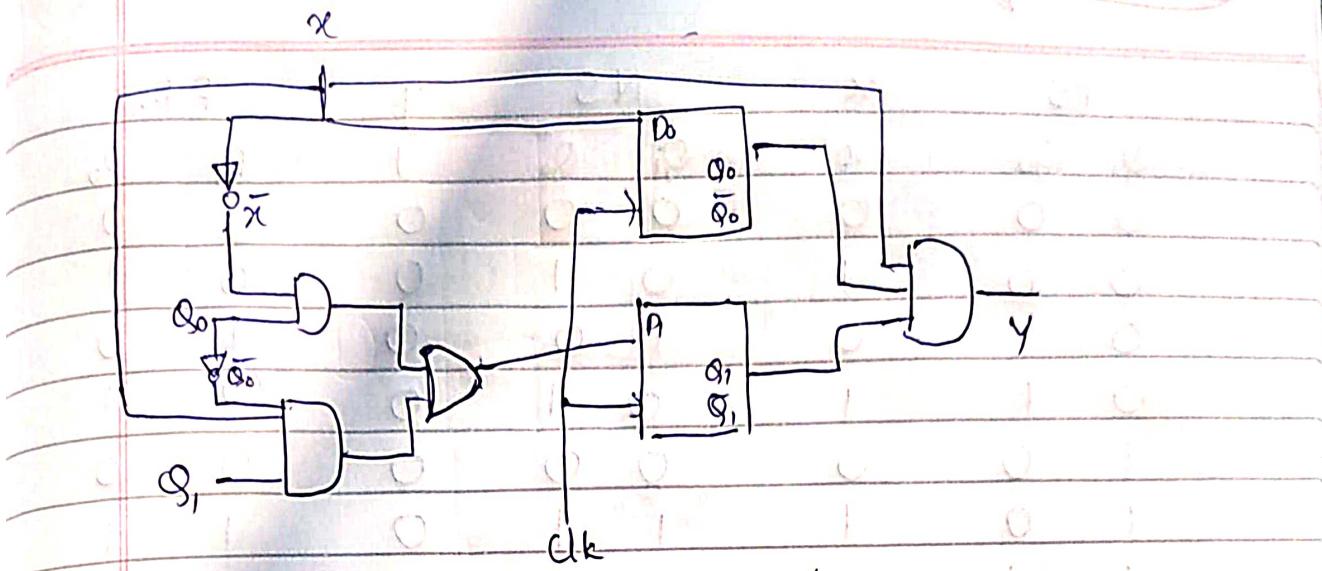

Q. 1010

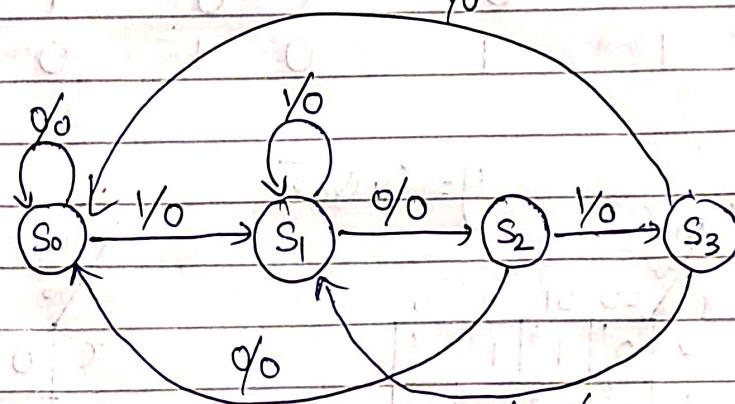

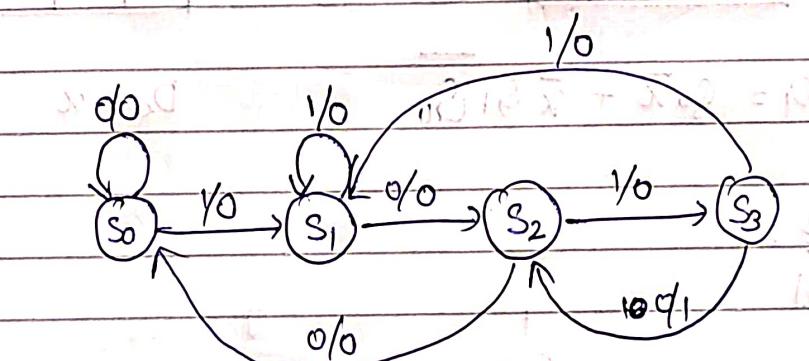$S_0 \rightarrow 0$
 $1 \rightarrow 0$
 $1 \rightarrow 1$
 $11 \xrightarrow{S_1 \rightarrow 10} 10$
 $10 \rightarrow 1$
 100
 $+ S_2 \rightarrow 101$
 $10 \rightarrow 0$
 $1 \rightarrow 1$
 1010
 $10x1$
 101
 $1 \rightarrow 0$
 $1 \rightarrow 1$
 $S_1 \rightarrow 10$
 $S_1 10 \rightarrow 1$
 $x00$
 $S_2 \rightarrow 101$
 $101 \rightarrow 0$
 $x010$



$S_0 \rightarrow 00$
 $S_1 \rightarrow 01$
 $S_2 \rightarrow 10$
 $S_3 \rightarrow 0011$

Legend: 0 = 0, 1 = 1, x = 0 or 1

PS	x	NS	y	F.F.
Q ₁	Q ₀	Q ₁ Q ₀	Q ₁	D ₁
0	0	0	0	D ₀
0	0	1	0	0
0	1	0	1	1
0	1	1	0	0
1	0	0	0	0
1	0	1	1	0
1	1	0	1	1
1	1	1	0	1

$$y = Q_1 Q_0 \bar{x}$$

x	00	01	11	10
0	0 ¹	1 ³	1 ⁷	0 ⁵
1	0 ²	0 ⁴	0 ⁸	1 ⁶


x	0	0	0	0
1	1	1	1	1

$$D_1 = Q_0 \bar{x} + \bar{x} Q_1 Q_0$$

$$D_0 = x$$

* Moore


101

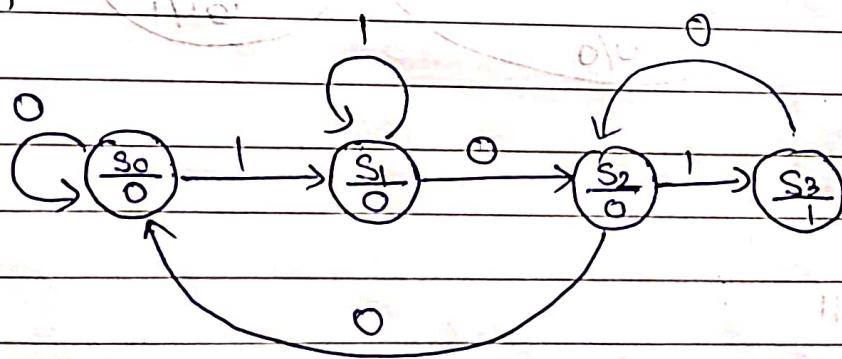

* Logic Gate using CMOS:

↓
Combination
of P & N.

NOT
gate

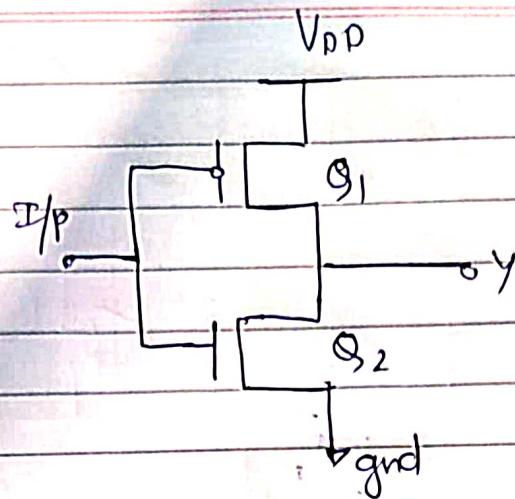


I/P	y
0	1
1	0

NAND

P-parallel

N-series

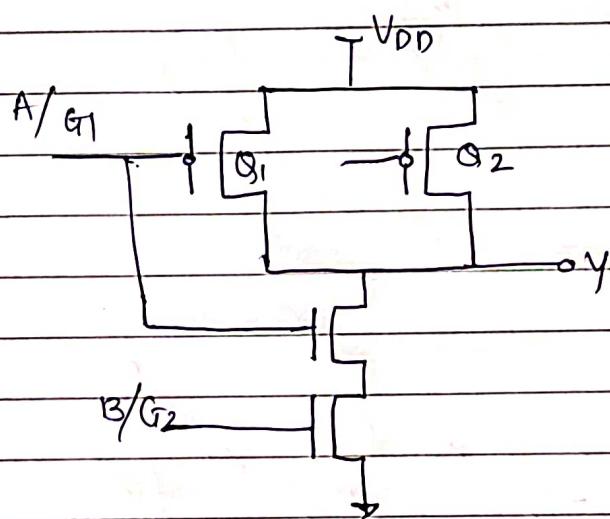


A	B	y
0	0	1
0	1	1
1	0	1
1	1	0

NOR

P-series

N-parallel.

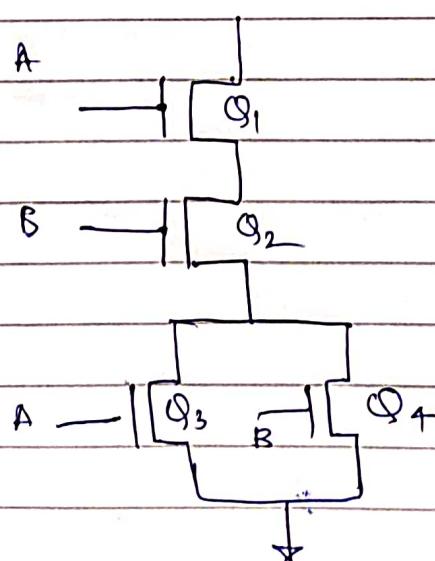

A	B	y
0	0	1
0	1	0
1	0	0
1	1	0