

Unit - 1

Circuit Simplification Techniques.

PAGE No.	/ / /
DATE	



* Networks -

- (1) Active / Passive ~~n/w~~ n/w
- (2) Linear / Non-linear n/w
- (3) Unilateral / Bi-lateral n/w


Sources -

voltage


current

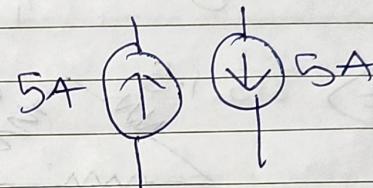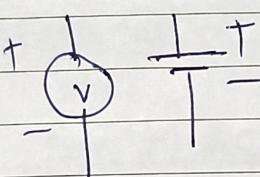

Star -

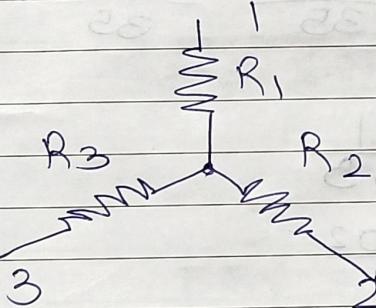

Delta

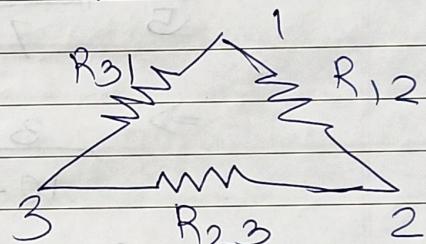

S to D

$$R_{12} = \frac{R_1 + R_2 + R_1 R_2}{R_3}$$

$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$


$$R_{31} = R_3 + R_1 + \frac{R_3 R_1}{R_2}$$

D to S


$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$R_2 = \frac{R_{12} R_{23}}{R_{12} + R_{23} + R_{31}}$$
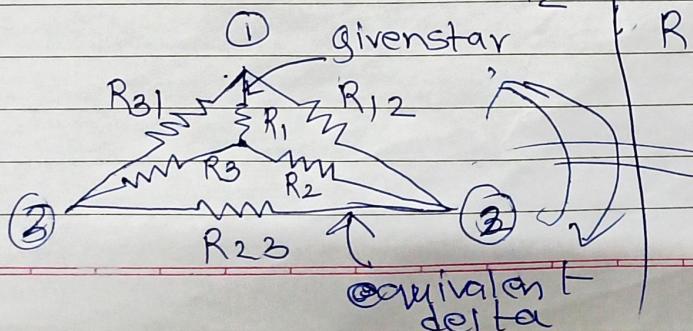
$$R_3 = \frac{R_{23} R_{31}}{R_{12} + R_{23} + R_{31}}$$



Q) Star to delta

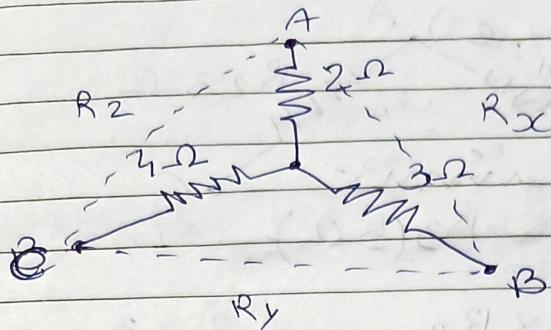

using formula.

$$R_x = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$= 2 + 4 + \frac{2 \times 4}{3}$$


$$R_x = 6.5$$

$$\text{simly} - R_y = 3 + 4 + \frac{3 \times 4}{2}$$


$$R_y = 13$$

$$\text{simly} - R_2 = 2 + 4 + \frac{2 \times 4}{3}$$

$$R_2 = 8.6$$

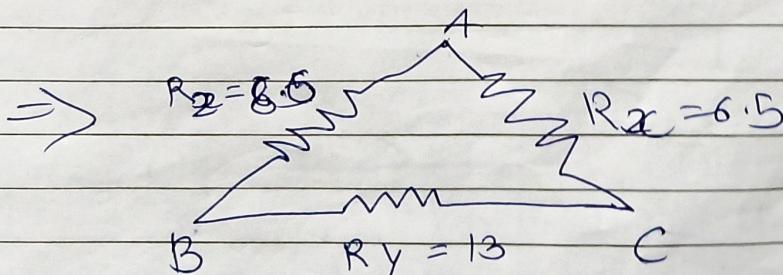


Q) Delta to Star

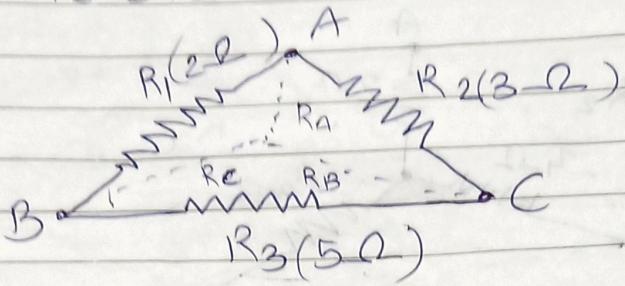

$$\therefore R_A = \frac{R_1 \times R_2}{R_1 + R_2 + R_3} = \frac{2 \times 3}{2+3+5} = 0.6\Omega$$

$$R_B = \frac{R_2 \times R_3}{R_1 + R_2 + R_3} = \frac{3 \times 5}{2+3+5} = 1.5\Omega$$

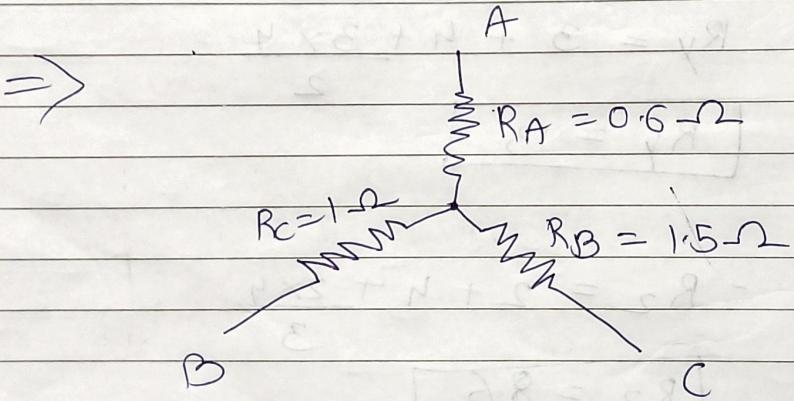
$$R_C = \frac{R_1 \times R_3}{R_1 + R_2 + R_3} = \frac{2 \times 5}{2+3+5} = 1\Omega$$




Series +
Parallel
Delta = $a^{-1} + b^{-1} = ans^{-1}$

PAGE No.	/ / /
DATE	/ / /

(Q)

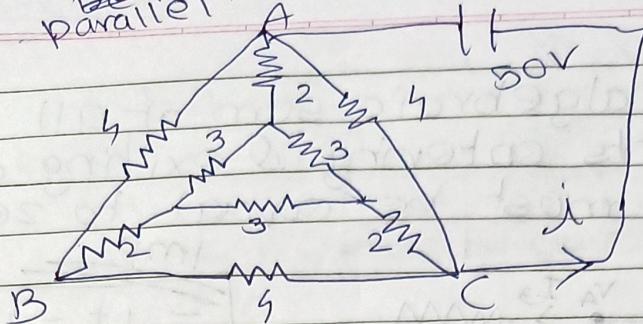


Delta to star.

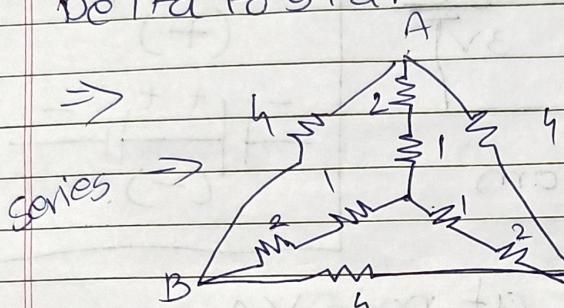

$$R_1 = \frac{3 \times 3}{3+3+3} \rightarrow R_2 = \frac{3 \times 3}{3+3+3}$$


$$R_3 = \frac{3 \times 3}{3+3+3}$$

series $\rightarrow a+b$

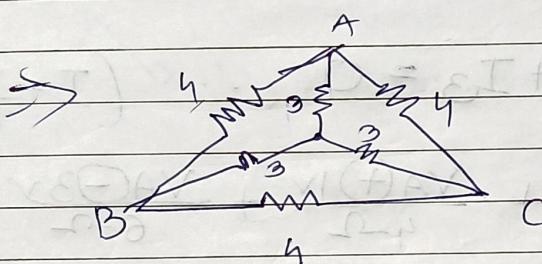



$$\text{Parallel} \rightarrow a^{-1} + b^{-1} = Ans^{-1}$$

Star to Delta.

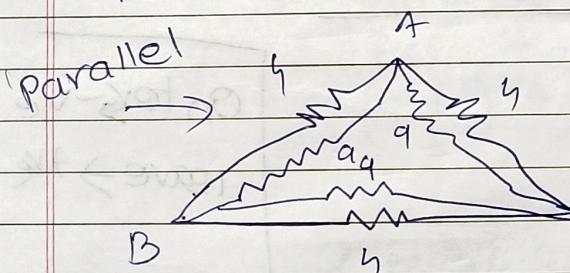


$$R_{\Delta} = \frac{R_1 + R_2 + R_1 R_2}{R_3} = 9$$
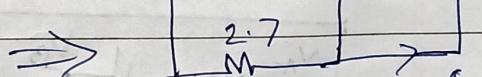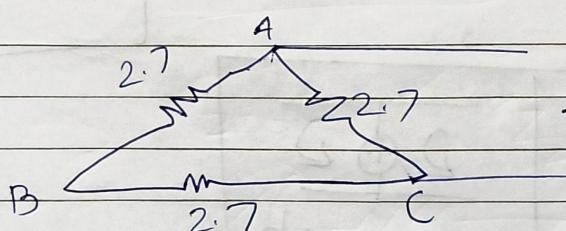
$$R_B = 3 + 3 + \frac{3 \times 3}{3} = 9$$



$$I = \frac{V}{R} = \frac{50}{1.8}$$


$$I = \underline{27.77 \text{ Amp}}$$

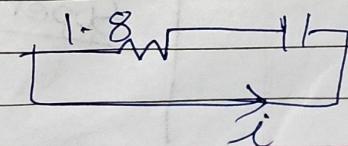


KCL

PAGE No.	/ / /
DATE	/ / /

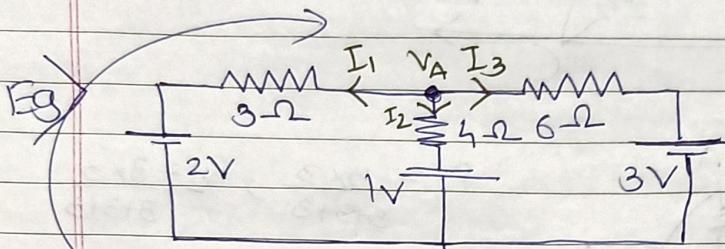KCL - The algebraic sum of all currents entering & exiting a node must be equal to zero



assume away from sun.

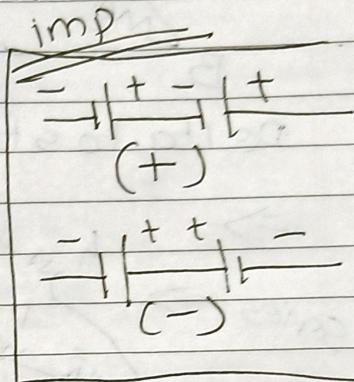



Applying KCL at node V_A

assume V_A at higher potential $\therefore I_1 + I_2 + I_3 = 0 \dots \dots (I = \frac{V}{R})$


$$\frac{V_A - 2V}{3\Omega} + \frac{V_A + 1V}{4\Omega} + \frac{V_A - 3V}{6\Omega} = 0$$

$$\therefore V_A = \underline{\hspace{2cm}}$$

on to \rightarrow leave \rightarrow the

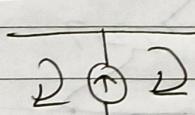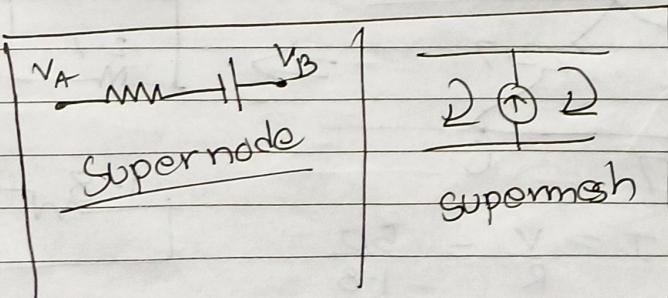

supermesh

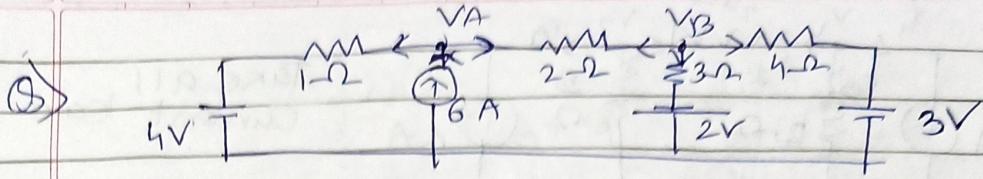

Apply KCL at node VA

$$\frac{VA - 4}{1} + \frac{VA - VB}{2} = 6$$

Apply KCL at node VB

$$\frac{VB - VA}{2} + \frac{VB + 2}{3} + \frac{VB - 3}{4} = 0$$

$$VA - 4 + \frac{VA}{2} - \frac{VB}{2} = 6$$

$$(1 - \frac{1}{2})VA - (\frac{1}{2})VB = 6 + 4 \quad \text{---(I)}$$

$$\frac{VB - VA}{2} + \frac{VB + 2}{3} + \frac{VB - 3}{4} = 0$$

$$(-\frac{1}{2})VA + (\frac{1}{2} + \frac{1}{3} + \frac{1}{4})VB = -\frac{2}{3} + \frac{3}{4} \quad \text{---(II)}$$


$$x = 37.28 \quad y = 17.28$$

$$\text{i.e. } VA = 37.28V, VB = 17.28$$

entry $\rightarrow -V_e$
leave $\rightarrow +V_e$

PAGE No.	/ /
DATE	/ /

(8)

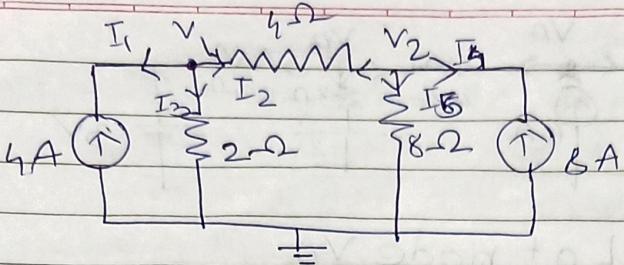

Take all current leave

Applying KCL at node V_1

$$I_1 + I_2 + I_3 \\ -\frac{4}{4} + \frac{V_1 - V_2}{4} + \frac{V_1 - 0}{2} = 0$$

$$-\frac{4}{4} + \frac{V_1 - V_2}{4} + \frac{V_1 - 0}{2} = 0$$

$$\left(\frac{1}{4} + \frac{1}{2}\right)V_1 - \left(\frac{1}{4}\right)V_2 = 4 \quad \text{---(1)}$$

Applying KCL at node V_2

$$I_2 + I_4 + I_5 \\ \frac{V_2 - V_1}{4} + \frac{V_2 - 0}{8} - \frac{8}{8} = 0$$

$$\frac{V_2 - V_1}{4} + \frac{V_2}{8} = 8 \quad \text{---(2)}$$


$$\left(\frac{1}{4} + \frac{1}{8}\right)V_2 - \left(\frac{1}{4}\right)V_1 = 8 \quad \text{---(1)}$$

Solving (1) & (2)

$$\underline{x = 16}, \underline{y = 32}$$

$$\therefore V_1 = 16V, V_2 = 32V$$

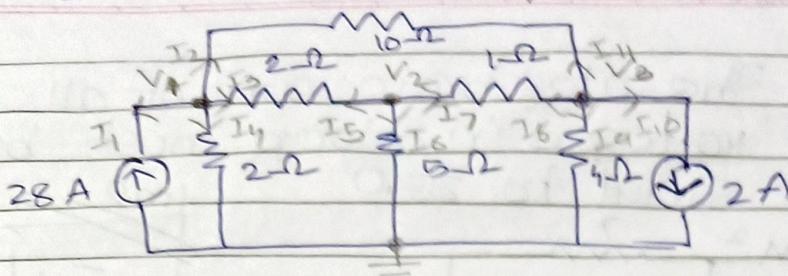(8) For the circuit shown below find the current flowing through 5 ohm resistance by nodal analysis.



Apply KCL at node 1

$$I_1 + I_2 + I_3 + I_4 = 0$$

$$\frac{-28 + V_1 - V_3}{10} + \frac{V_1 - V_2}{2} + \frac{V_1 - 0}{2} = 0$$

$$\frac{V_1}{10} - \frac{V_3}{10} + \frac{V_1}{2} - \frac{V_2}{2} + \frac{V_1}{2} = 28$$

$$\left(\frac{1}{10} + \frac{1}{2} + \frac{1}{2}\right)v_1 - \left(\frac{1}{2}\right)v_2 - \left(\frac{1}{10}\right)v_3 = 28 \quad \text{--- (1)}$$

Apply KCL at node 2

$$I_5 + I_6 + I_7 = 0$$

$$\frac{v_2 - v_1}{2} + \frac{v_2 - 0}{5} + \frac{v_2 - v_3}{1} = 0$$

$$\frac{v_2 - v_1}{2} + \frac{2v_3}{5} + v_2 - v_3 = 0$$

$$\left(-\frac{1}{2}\right)v_1 + \left(\frac{1+1}{2} + \frac{1}{5}\right)v_2 - (1)v_3 = 0 \quad (11)$$

Apply KCL at node ③

$$I_8 + I_9 + I_{10} + I_{11} = 0$$

$$\frac{v_3 - v_2}{1} + \frac{v_3 - 0}{4} - 2 + \frac{v_3 - v_1}{10} = 0$$

$$\frac{v_3 - v_2 + \frac{v_3}{5}}{1} - 2 + \frac{v_3}{10} - \frac{v_1}{10} = 0$$

$$\left(\frac{-1}{10}\right)v_1 - v_2 + \left(1 + \frac{1}{4} + \frac{1}{10}\right)v_3 = 2 \quad (III)$$

Solving (i), (ii), (iv), (v)

$$x = 38.76, y = 25.74, z = 22.68$$

$$\therefore \text{Current through } B\text{-}\Omega = \frac{V_2 - 0}{5} = \frac{24.74 - 0}{5} = 4.948 \text{ A}$$

mesh - smallest loop which cannot be further divided



KVL

mesh analysis \rightarrow KVL

DATE

/ / /

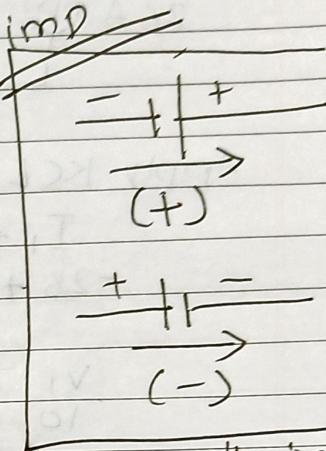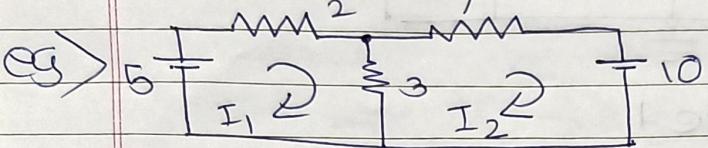KVL - The algebraic sum of all voltages in a loop must be equal to zero



Applying KVL in loop ①

$$5 - 2I_1 - 3(I_1 - I_2) = 0$$

$$5 - 2I_1 - 3I_1 - 3I_2 = 0$$

$$5 - 5I_1 + 3I_2 = 0$$

$$\underline{5I_1 + 3I_2 = 5} \quad \text{---} \textcircled{1}$$

whenever there is resistance
there is voltage drop (-)

Applying KVL in loop ②

$$-3(I_2 - I_1) - 7I_2 - 10 = 0$$

$$-3I_2 + 3I_1 - 7I_2 - 10 = 0$$

$$\underline{10I_2 - 3I_1 = -10} \quad \text{---} \textcircled{2}$$

Solving ① & ② simultaneously (by Crammer's rule).

$$x = \frac{-1/3}{-1/3} \quad y = \frac{20/1}{-1/3}$$

$$= -0.33 \quad = 2.22$$

Shortcut

add R

loop 1


$$3 + 2 = 5$$

$$5I_1 + 3I_2 = 5$$

loop 2

$$7 + 3 = 10$$

$$10I_2 - 3I_1 = -10$$

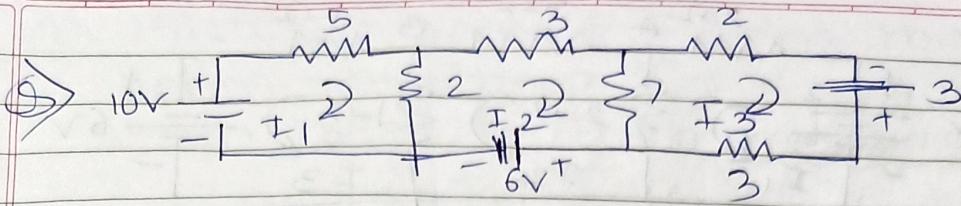

Applying KVL in loop 1

$$7I_1 - 2I_2 = 10V \quad \text{--- (1)}$$

Applying KVL in loop 2

$$12I_2 - 2I_1 - 7I_3 = -6V \quad \text{--- (2)}$$

Applying KVL in loop 3

$$12I_3 - 7I_2 = 3V \quad \text{--- (3)}$$

Solving simultaneously,


$$x = \frac{848}{617} = 1.37 \quad \therefore I_1 = 1.37$$

$$y = \frac{117}{617} = 0.189 \quad \therefore I_2 = 0.189$$

$$z = \frac{86}{617} = 0.139 \quad \therefore I_3 = 0.139$$

or drawing three A-B
Find current in AB & power across 3 resistors

PAGE NO.
DATE

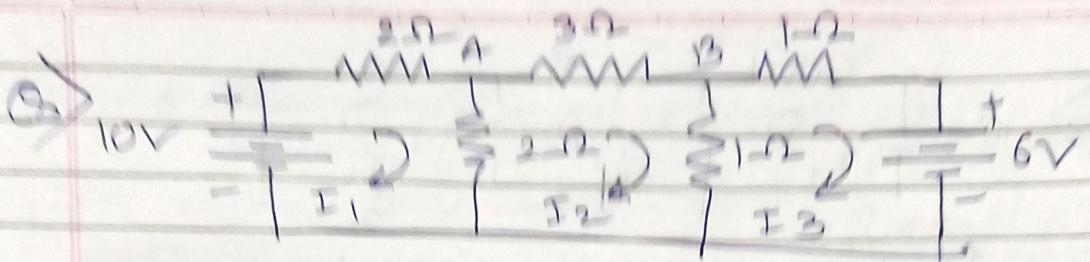

Applying KVL in loop ①

$$-10 + 2I_1 + 2(I_1 - I_2) = 0$$
$$-10 + 2I_1 + 2I_1 - 2I_2 = 0$$

$$\underline{4I_1 - 2I_2 = 10} \quad \text{--- ①}$$

loop ②

$$3I_2 + 1(I_2 - I_3) + 2(I_2 - I_1) = 0$$
$$3I_2 + I_2 - I_3 + 2I_2 - 2I_1 = 0$$

$$\underline{6I_2 - 2I_1 - I_3 = 0} \quad \text{--- ②}$$

loop ③

$$6 + 1(I_3 - I) + I_3 = 0$$
$$6 + I_3 - I_2 + I_3 = 0$$

$$\underline{2I_3 - I_2 = -6} \quad \text{--- ③}$$

Solving simultaneously.


$$x = \frac{49}{18} = 2.72, y = \frac{1}{9} = 0.44, z = -\frac{25}{9} = -2.77$$

i.e. $I_1 = 2.72$, $I_2 = 0.44$, $I_3 = -2.77$

$$\boxed{I_2 = 0.44 \text{ A}}$$

$$P = I^2 R = (0.44)^2 \times 3$$
$$P = 0.591 \text{ W}$$

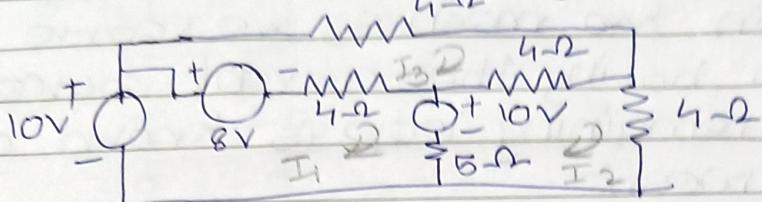(Q) Find the current flowing through 5 ohm resistance for the network shown below by using mesh analysis.



Applying KVL in loop ①

$$\begin{aligned} 9I_1 - 4I_3 - 5I_2 &= 10 + -8 - 10 \\ 9I_1 - 5I_2 - 4I_3 &= -8 \quad \text{---} \end{aligned}$$

Applying KVL in loop ②

$$\begin{aligned} 13I_2 - 5I_1 - 4I_3 &= 10 \\ -5I_1 + 13I_2 - 4I_3 &= 10 \quad \text{---} \end{aligned}$$

Applying KVL in loop ③

$$\begin{aligned} 12I_3 - 4I_1 - 4I_2 &= +8 \\ -4I_1 - 4I_2 + 12I_3 &= 8 \quad \text{---} \end{aligned}$$

Solving ①, ②, ③ simultaneously.

$$x = 0.36, y = 1.28, z = 1.21$$

$$\therefore I_1 = 0.36A, I_2 = 1.28A, I_3 = 1.21A$$

\therefore The current flowing through 5Ω i.e.

$$\begin{aligned} \text{Total current } I_{5\Omega} &= I_2 - I_1 \\ &= 1.28 - 0.36 \\ I_{5\Omega} &= 0.92A \end{aligned}$$


Mesh Analysis

PAGE No.

DATE / /

* Supermesh -

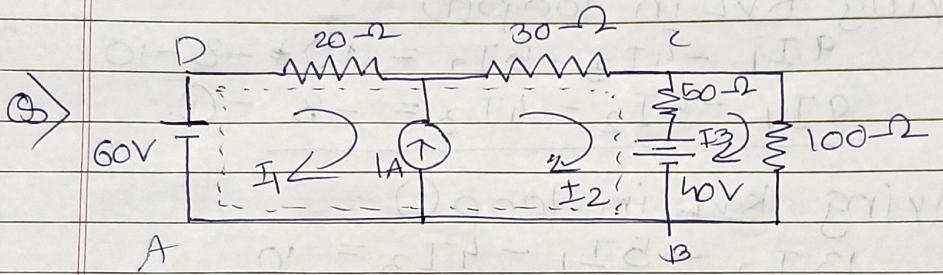When a current source is present between two meshes, we remove the branch having the current source and then remaining loop is known as Supermesh.



Apply KVL in loop 3

$$0I_1 - 50I_2 + 150I_3 = 60V \quad \text{--- (3)}$$

Apply supermesh.

$$I_2 - I_1 = 1 \quad \text{--- (2)}$$

Applying K.V.L to complete loop of supermesh.


$$20I_1 + 50I_2 - 50I_3 = 60 - 60$$

$$20I_1 + 80I_2 - 50I_3 = 20 \quad \text{--- (1)}$$

Solving (1), (2), (3) sum

$$I_1 = \underline{\hspace{2cm}}, \quad I_2 = \underline{\hspace{2cm}}, \quad I_3 = \underline{\hspace{2cm}}$$


(b)

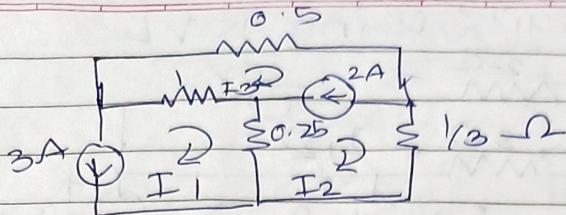

$$I_1 = -3 \text{ A} \quad \text{--- (1)}$$

$$I_3 - I_2 = 2 \text{ A} \quad \text{--- (2)}$$

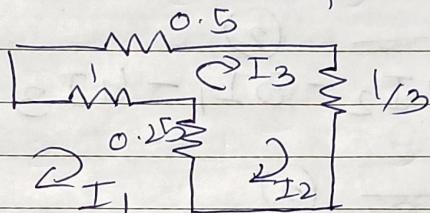For earn (2) remove 2A current source
& write earn for supermesh.



$$-0.5I_3 - 0.33I_2 - 0.25(I_2 - I_1) - (I_3 - I_1) = 0$$


$$-0.5I_3 - 0.33I_2 - 0.25(I_2 + 3) - (I_3 + 3) = 0$$

$$-0.58I_2 - 1.5I_3 = 3.75$$

$$\text{put } I_3 = I_2 + 2$$

$$\therefore \boxed{\begin{aligned} I_2 &= -3.24 \text{ A} \\ I_1 &= -1.24 \text{ A} \end{aligned}}$$

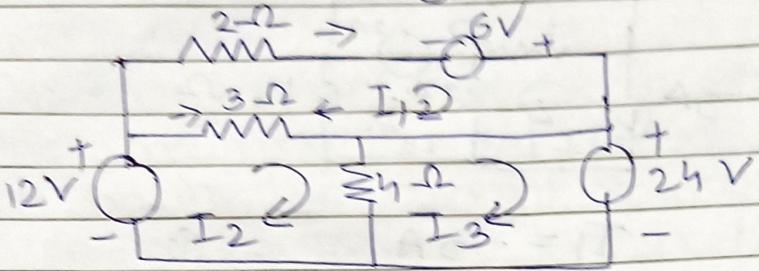b) Find I_1 , I_2 & I_3 for given circuit using KVL



App KVL in loop ①

$$5I_1 - 3I_2 = 6V \quad \text{---} \textcircled{1}$$

$$7I_2 - 3I_1 - 4I_3 = 12V \quad \text{---} \textcircled{2}$$

$$4I_3 - 4I_2 = -24 \quad \text{---} \textcircled{3}$$

$$x = -3A \quad y = -7A \quad z = -13A$$


i.e. $I_1 = -3A$

$$I_2 = -7A$$

$$I_3 = -13A$$

Q3) For the network shown in fig determine the values of I_1 , I_2 & I_3

PAGE NO.	/ /
DATE	

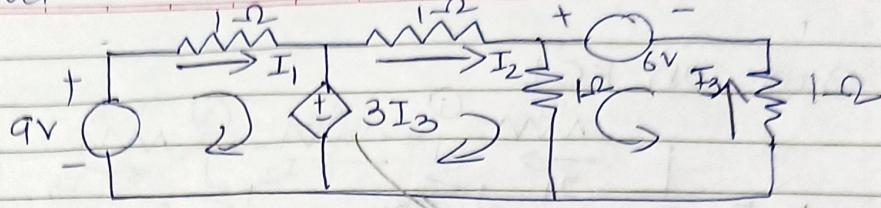

Current dependent MT source

applying KVL in loop ①

$$I_1 + 3I_3 = 9 \quad \text{---} \textcircled{1}$$

Applying KVL in loop ②

$$2I_2 - 3I_3 + I_3 = 0$$

$$2I_2 - 3I_3 \\ 2I_2 - 2I_3 = 0 \quad \text{---} \textcircled{2}$$



Applying KVL in loop ③

$$2I_3 + I_2 = 6V$$

$$I_2 + 2I_3 = 6V \quad \text{---} \textcircled{3}$$

$$x = 3, y = 2, z = 3.$$


$$\text{i.e. } I_1 = 3A, I_2 = 2A, I_3 = 2A$$

Nodal Analysis

PAGE No.

DATE

Based on KCL

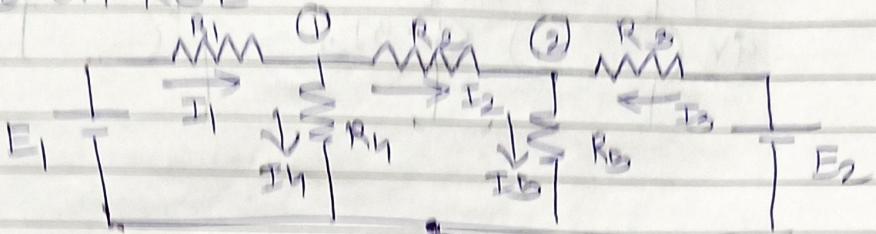

Junction where three or more branches meet is called as node

One of these is assumed as reference/datum/zero potential node

If n no. of total nodes are there
no. of equations will be $(n-1)$

Node ③ in reference node

at node ①

$$I_1 = I_2 + I_4 \quad \text{--- (A)}$$

$$I_1 R_1 = E_1 - V_A$$

$$\therefore I_1 = \frac{E_1 - V_A}{R_1} \quad \text{--- (1)}$$

$$I_4 = \frac{V_A}{R_4}$$

$$I_2 R_2 = V_A - V_B$$

$$\therefore I_2 = \frac{V_A - V_B}{R_2}$$

put I_2 & I_4 in eqn (A)

$$V_A \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} \right) - \frac{V_B}{R_2} - \frac{E_1}{R_1} = 0$$

At node ②

$$I_5 = I_2 + I_3 \quad - (B)$$

$$I_5 = \frac{V_B}{R_S}$$

$$I_2 = \frac{\sqrt{A} - V_B}{R_2} \quad \text{--- already written}$$


$$I_3 = \frac{E_2 - V_B}{R_3}$$

put these values in eqn (B)

$$V_B \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_S} \right) - \frac{\sqrt{A}}{R_2} - \frac{E_2}{R_3} = 0$$

In short -

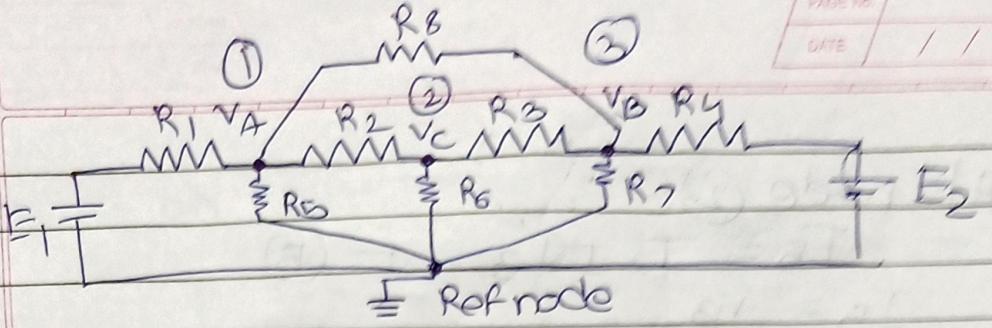- ① Product of node potential V_A & $(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_S})$
i.e., sum of the reciprocals of the branch resistances connected to this node
- ② Minus the ratio of adjacent potential V_B & the interconnecting resistance R_2
- ③ Minus ratio of adjacent battery voltage E_1 & interconnecting resistance R_3 .
- ④ All above equal to zero.




$$VA \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_5} + \frac{1}{R_8} \right) - \frac{V_C}{R_2} - \frac{V_B}{R_5} - \frac{E_1}{R_1} = 0$$

$$VB \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_7} + \frac{1}{R_8} \right) - \frac{VA}{R_8} - \frac{V_C}{R_3} - \frac{E_2}{R_4} = 0$$

$$VC \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_6} \right) - \frac{VA}{R_2} - \frac{VB}{R_3} = 0$$

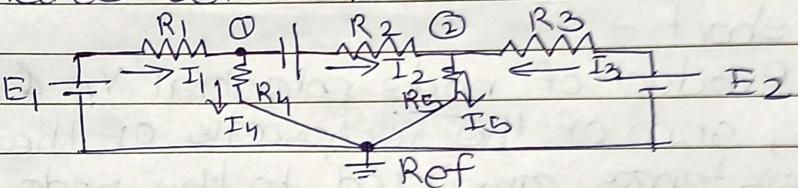Case 2: when a third battery of emf E_3 is connected between node (1) & (2)



E_3 is connected between node (1) & (2). As we travel from (1) to (2), we go from -ve terminal of E_2 to +ve terminal. Hence acc to sign convention it must be taken +ve & vice versa for when we travel from (2) i.e. $-E_3$ at node (1).

$$I_1 = I_2 + I_4 \quad I_2 = \frac{V_A + E_3 - V_B}{R_2} \quad I_4 = \frac{V_A}{R_1}$$

$$I_1 = \frac{E_1 - V_A}{R_1}$$

$$VA \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} \right) - \frac{E_1}{R_1} - \frac{V_B}{R_2} + \frac{E_3}{R_2} = 0$$

at node (2),


$$I_2 + I_3 = I_5$$

$$I_2 = \frac{V_A + E_3 - V_B}{R_2} \quad I_3 = \frac{E_2 - V_B}{R_3} \quad I_5 = \frac{V_B}{R_5}$$

$$VB \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_5} \right) - \frac{E_2}{R_2} - \frac{VA}{R_2} - \frac{E_3}{R_2} = 0$$

Super node - v/t source between two nodes

PAGE NO. / / / /
DATE / / / /

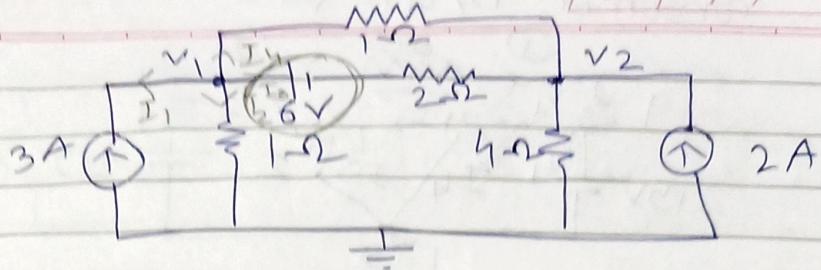

App K.C.L at node V_1

$$-3 + \frac{V_1 - V_2}{1} + \frac{V_1 - 6 - V_2}{2} = 0$$

$$5V_1 - 3V_2 = 12 \quad \text{---(1)}$$

App K.C.L at node V_2

$$\frac{V_2 - V_1}{1} + \frac{V_2 - 0}{4} + \frac{V_2 + 6 - V_1}{2} = 2$$


$$-6V_1 + 7V_2 = -4 \quad \text{---(2)}$$

Solving (1) & (2)

$$V_1 = 4.23V, \quad V_2 = 3.05V$$

Calculate total power consumed by all passive elements

DATE / / /

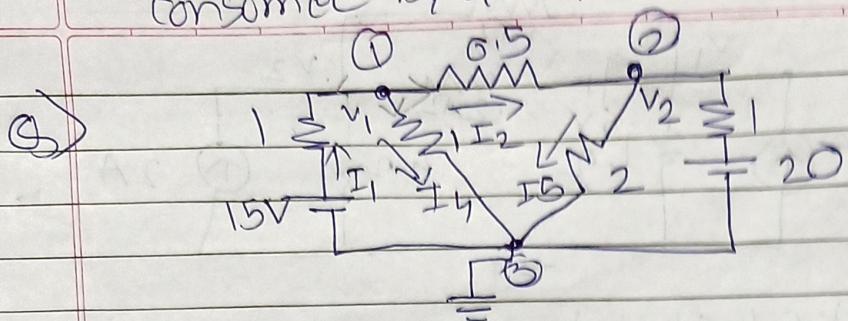

Applying ^{KCL} at node 1

$$\frac{V_1 - 15}{1} + \frac{V_1 - V_2}{0.5} + \frac{V_1 - 0}{1} = 0$$

$$\frac{V_1 - 15}{1} + \frac{V_1 - V_2}{0.5} + \frac{V_1 - 0}{1} = 0$$

~~$$+ 4\left(\frac{2+1}{0.5}\right)V_1 - \left(\frac{1}{0.5}\right)V_2 = 15$$~~

Applying ^{KCL} at node 2

$$I_1 = \frac{5.13 - 15}{1}$$

$$\frac{V_2 - V_1}{0.5} + \frac{V_2 - 0}{2} + \frac{V_2 - 20}{1} = 0$$

$$I_2 = \frac{5.13 - 2.77}{0.5}$$

$$\frac{V_2 - V_1}{0.5} + \frac{V_2 - 0}{2} + \frac{V_2 - 20}{1} = 0$$

$$\left(\frac{1}{0.5}\right)V_1 + \left(1 + \frac{1}{2} + \frac{1}{0.5}\right)V_2 = 20$$

$$I_3 = \frac{5.13 - 0}{1}$$

$$x = \frac{18.5}{36} \rightarrow y = \frac{25}{9}$$

$$I_4 = \frac{2.77 - 0}{2}$$

$$-5.13 \quad y = 2.77$$

$$V_1 = 5.13 \quad V_2 = 2.77$$


$$I_5 = \frac{2.77 - 20}{1}$$

~~$$= \frac{V_1}{R} = \frac{5.13}{0.5}$$~~

$$\text{Total } P = I_1^2 R + I_2^2 R + I_3^2 R + I_4^2 R + I_5^2 R$$

I_{ab}, I_{bc}, I_{cd} = ?

PAGE No.	/ / /
DATE	

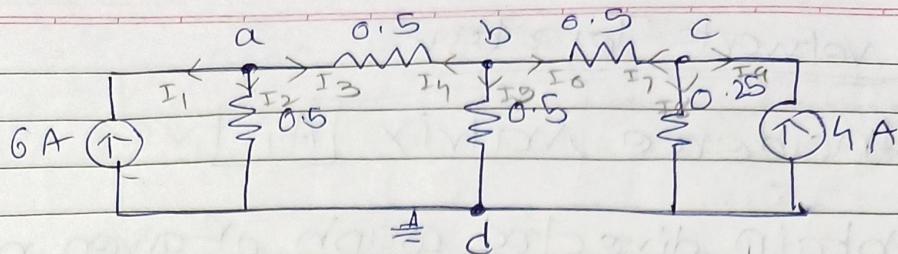

Applying KCL at node a

$$I_1 + I_2 + I_3 = 0$$

$$-6 + \frac{V_a - 0}{0.5} + \frac{V_a - V_b}{0.5} = 0$$

$$\frac{V_a}{0.5} + \frac{V_a}{0.5} + \frac{V_b}{0.5} = 6$$

$$\left(\frac{1}{0.5} + \frac{1}{0.5}\right)V_a + \left(\frac{1}{0.5}\right)V_b = 6 \quad (1)$$

Applying KCL at node b

$$I_4 + I_5 + I_6 = 0$$

$$\frac{V_b - V_a}{0.5} + \frac{V_b - V_a}{0.5} + \frac{V_b - V_c}{0.5} = 0$$

$$\left(-\frac{1}{0.5}\right)V_a + \left(\frac{1}{0.5} + \frac{1}{0.5} + \frac{1}{0.5}\right)V_b - \left(\frac{1}{0.5}\right)V_c = 0 \quad (2)$$

Applying KCL at node c

$$I_7 + I_8 + I_9 = 0$$

$$\frac{V_c - V_b}{0.5} + \frac{V_c - 0}{0.25} + -4 = 0$$

$$\left(-\frac{1}{0.5}\right)V_b + \left(\frac{1}{0.5} + \frac{1}{0.25}\right)V_c = 4 \quad (3)$$

~~$$V_a = x = \frac{I_3}{12} = 1.08$$~~

$$\frac{V_a - V_b}{0.5} = \frac{1.08 - 0.83}{0.5}$$

~~$$V_b = y = \frac{5}{6} = 0.83$$~~


~~$$V_c = z = \frac{17}{12} = 1.41$$~~

* Network Topology


* Incidence Matrix $[A_i]$

- ① obtain directed graph of given n/w
- ② Assign '+1' in the matrix if the arrow of a branch is oriented away from that node.
- ③ Assign (-1) ... oriented towards that node
- ④ Assign '0' in the matrix if the branch is not connected to a node

(Q1)

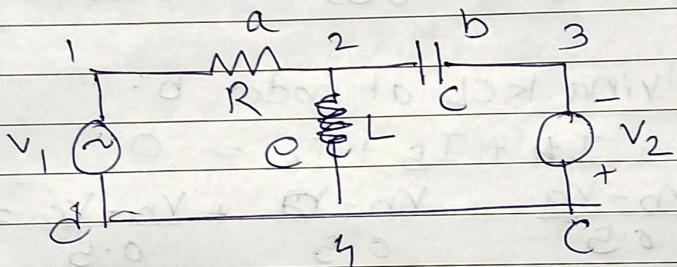


Directed path

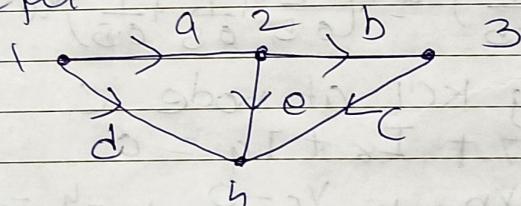


branches \rightarrow

nodes	a	b	c	d	e
1	1	0	0	1	0
2	-1	1	0	0	1
3	0	-1	1	0	0
4	0	0	-1	-1	-1

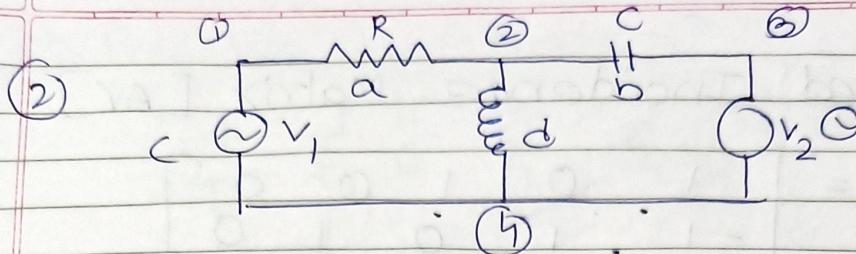

Directed cut

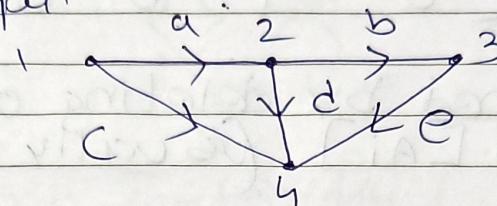

incidence matrix $[A_i]$

branches \rightarrow	a	b	c	d	e
nodes	1	2	3	4	5
1	1	0	0	1	0
2	-1	1	0	1	0
3	0	-1	0	0	1
4	0	0	-1	0	-1

check (1) sum of columns is zero

(2) Det 1 is zero

* Reduced Incidence Matrix $[A_R]$

$$\text{Q) } [A_R] = \begin{bmatrix} 1 & 0 & 1 & 0 & 0 \\ -1 & 1 & 0 & 1 & 0 \\ 0 & -1 & 0 & 0 & 1 \end{bmatrix} \quad 3 \times 5$$

obtained by deleting one row from $[A_i]$ (usually last row)

$$\text{No. of possible trees} = \det \{ [A_R] [A_R]^T \}$$

$$\therefore [A_R] = \begin{bmatrix} 1 & 0 & 1 & 0 & 0 \\ -1 & 0 & 0 & 1 & 0 \\ 0 & -1 & 0 & 0 & 1 \end{bmatrix} \quad 3 \times 5$$

$$[A_R] = \begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & -1 \\ 1 & 0 & 0 \\ 0 & 0 & 1 \\ 0 & 0 & 0 \end{bmatrix} \quad 5 \times 3$$


$$\det \{ [A_R] \cdot [A_R]^T \}$$

$$[A_R]^T = \begin{bmatrix} 2 & -1 & 0 \\ -1 & 3 & -1 \\ 0 & -1 & 2 \end{bmatrix}$$

$$D = 8$$

$$\therefore \text{No. of trees} = 8$$

Q) Possible no. of trees = ?

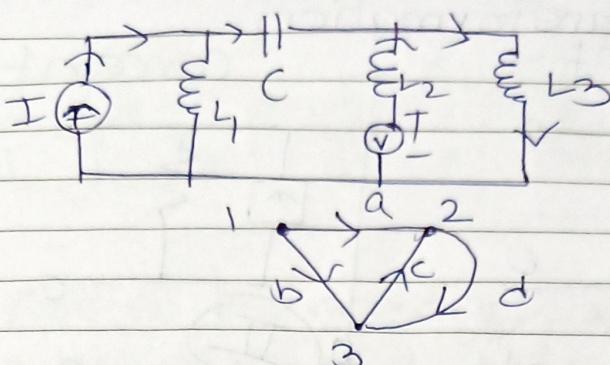

incidence matrix $[A_i]$

$$\begin{matrix} \text{br} \rightarrow & a & b & c & d \\ \downarrow & 1 & 1 & 1 & 0 \ 0 \\ & 2 & -1 & 0 & -1 \ 1 \\ & 3 & 0 & -1 & 1 \ -1 \end{matrix}$$

$$Ar = \begin{bmatrix} 1 & 1 & 0 & 0 \\ -1 & 0 & -1 & 1 \end{bmatrix} \quad [Ar]^T = \begin{bmatrix} 1 & -1 \\ 1 & 0 \\ 0 & -1 \\ 0 & 1 \end{bmatrix}$$

$$[Ar] [Ar]^T = \begin{bmatrix} 1 & 1 & 0 & 0 \\ -1 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} 1 & -1 \\ 1 & 0 \\ 0 & -1 \\ 0 & 1 \end{bmatrix}$$

$$X^{-1} = \begin{bmatrix} 2 & -1 \\ -1 & 3 \end{bmatrix}$$


$$\text{Det} \Rightarrow \begin{bmatrix} 2 & -1 \\ -1 & 3 \end{bmatrix}$$

$$= 5$$








* Source Transformation


Volt

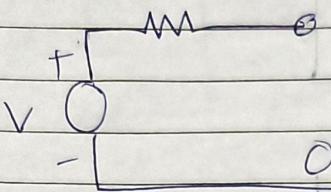

Current

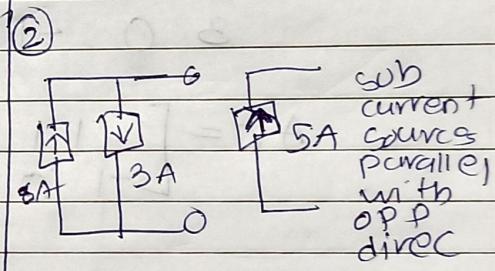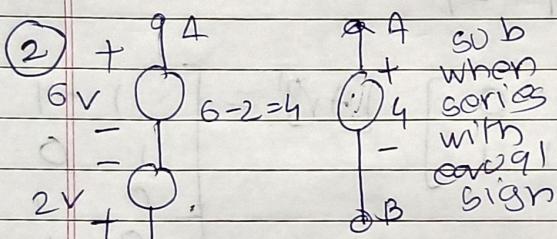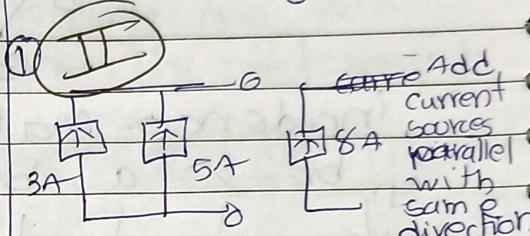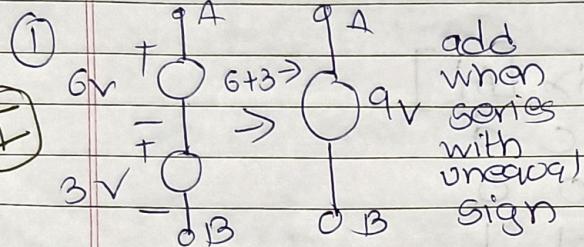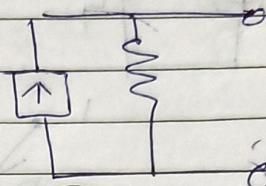

Transformation.

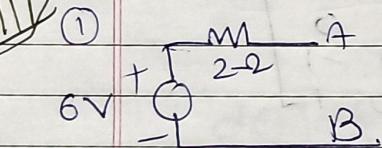




$$V = 6$$

$$R = 2$$

$$I = V/R$$

$$I = 6/2 = 3$$

(5) In series

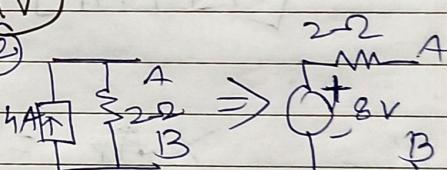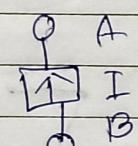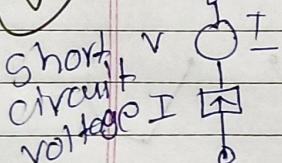

$$I = 4A$$


$$R = 2$$

$$V = I R$$

$$= 4 \times 2$$

$$V = 8$$

(6) In parallel

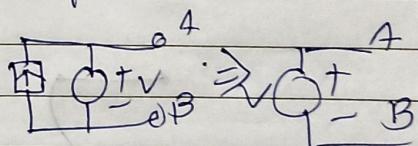


open circuit voltage.

Voltage source always in series
current source always in parallel

PRACTICE
DATE


VII

① Volt & R in parallel
dummy element

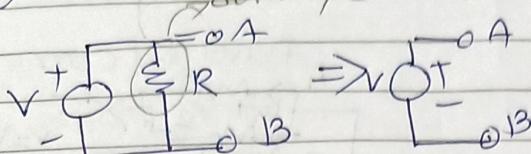


VIII

② I & R in series

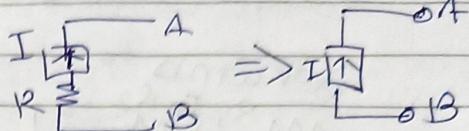

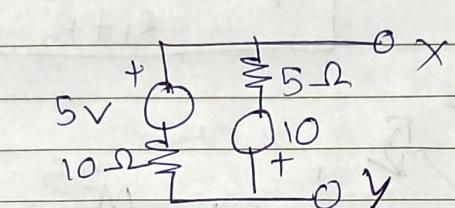
eg → Reduce the network shown in figure to a single voltage source in series with single element.





$$V = 5V$$

$$R = 10 \Omega$$

$$I = V/R = 5/10 = 0.5A$$

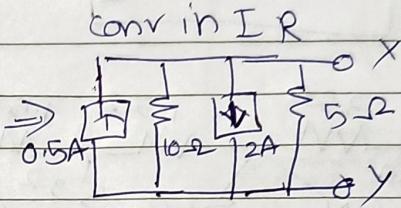

conv in I R

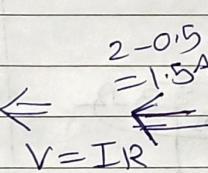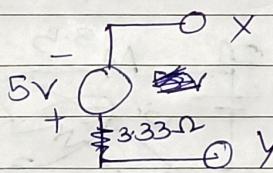

$$2 - 0.5 = 1.5A$$

$$= 1.5A$$

$$V = 10$$

$$R = 5$$

$$I = 2A$$

$$= 2A$$

↓ sub current so




$$\frac{R_1 R_2}{R_1 + R_2} = \frac{10 \times 5}{10 + 5} = 3.33 \Omega$$

$$V = IR$$

$$= 1.5A \times 3.33 \Omega$$


$$= 4.99 \approx 5V$$

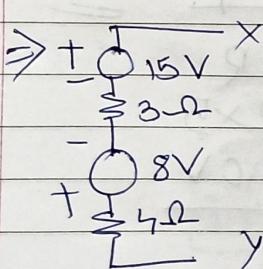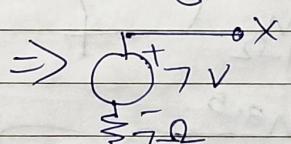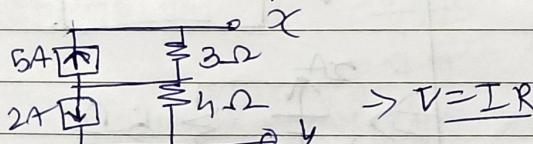Q) Convert given combination into a single current source in parallel with a single element





$$15 - 8 = 7V$$

$$I = \frac{V}{R} = \frac{7}{7} = 1A$$

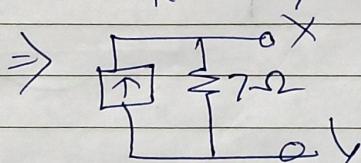






* Series Parallel combination

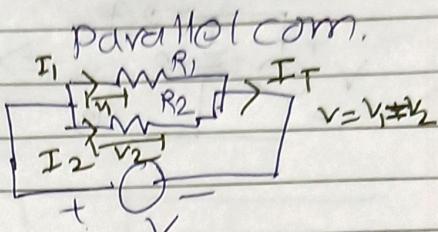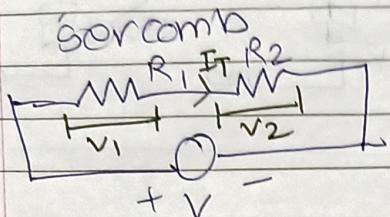

$$R_T = R_1 + R_2 + \dots + R_n$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \cdots + \frac{1}{R_n}$$

$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

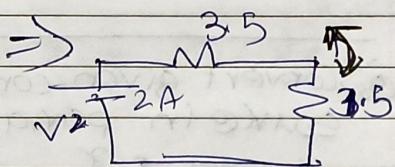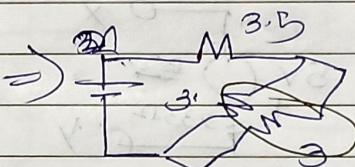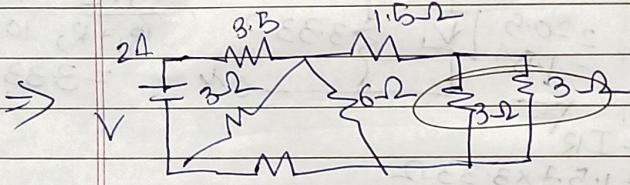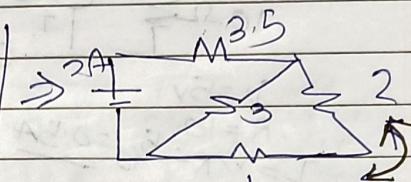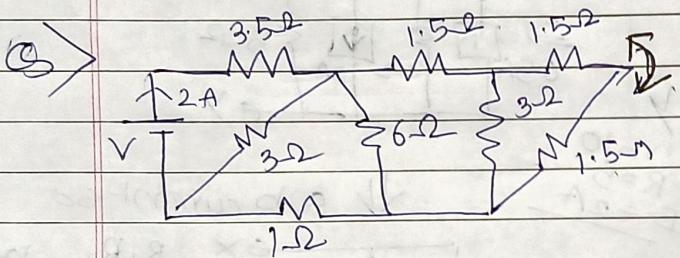


$$V = IR$$

$$\sqrt{ } = 2 \times 5$$

$$\underline{V = 10V}$$

* Current division formula -

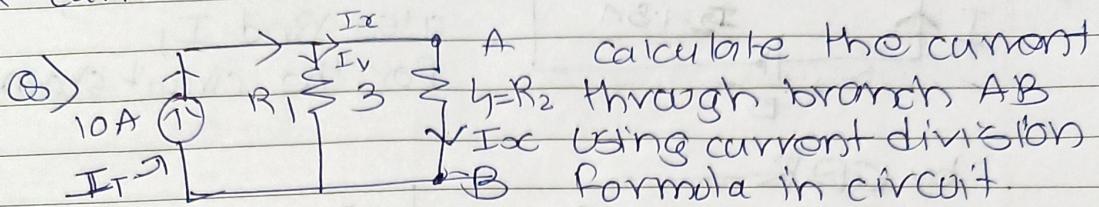

① First find total current $[I_T]$

by current division formula

$$I_x = I_T \times \frac{R_1}{R_1 + R_2}$$

$$= 10 \times \frac{3}{3+4}$$

$$= 10 \times \frac{3}{7}$$


i.e. $I_{AB} = 4.28A$

$$I_x = 4.28A$$

current division formula

$$I_x = I_T \times \frac{\text{Res of opp branch}}{\left(\frac{\text{Res of opp branch}}{\text{Res of current branch}} + 1 \right)}$$

imp

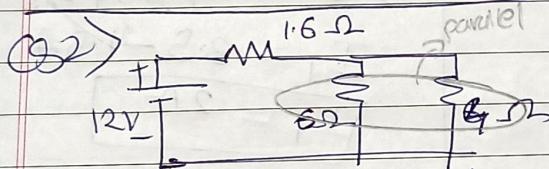


Find the current through 4 ohm resistor for the circuit shown.

① Find total current

$$I_T = \frac{12V}{1.6\Omega + 2.4\Omega}$$

$$= \frac{12}{4} = 3A$$
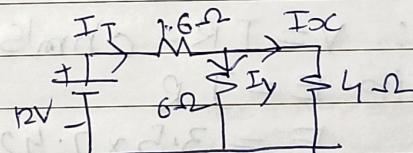
$$\therefore \text{Total } R_T = 1.6 + 2.4 = 4\Omega$$



by current div formula.

$$I_x = I_T \times \frac{4}{4+6}$$

$$I_T = \frac{12V}{4\Omega}$$

$$= 3A$$


$$\boxed{I_T = 3A}$$

$$= 3 \times \frac{4}{10}$$

$$I_{SC} = 1.8A$$

i.e. current flowing

through the 4 ohm resistor is 1.8A

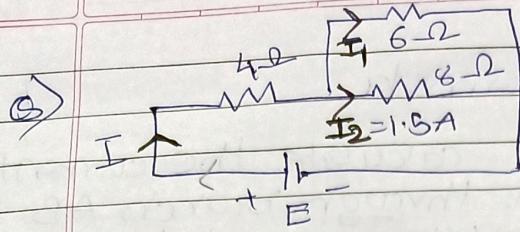

Find the value of
battery voltage,
also find I_1
for the circuit shown

by CDR

$$I_2 = I \times \frac{6}{6+8}$$

$$1.5 = I \times \frac{6}{6+8}$$

$$\frac{1.5 \times 14}{6} = I$$

$$I = 3.5A$$

By CDR

$$I_1 = I \times \frac{8}{8+6}$$

$$= 3.5 \times \frac{8}{14}$$

$$I_1 = 2A$$

OR

Total Resistance R_T

$$R_T = 5 + \frac{6 \times 8}{6+8}$$

$$R_T = 7.428 \Omega$$

$$I = I_1 + I_2$$

$$3.5 = I_1 + 1.5A$$

$$I_1 = 3.5 - 1.5A$$

$$I_1 = 2A$$

$\therefore V = IR$ - Ohm's law

$$\text{i.e. } E = IR$$

$$E = 3.5 \times 7.428$$

$$E = 25.998V$$

$$E \approx 26V$$

$$E = 26V$$

$$I_1 = 2A$$

2

PAGE No.	
DATE	/ /


Unit II

Network Theorems

PAGE No.	/ /
DATE	



* Superposition Theorem.

In any multi source linear, bilateral network, voltage across or current through any given element is algebraic sum of individual voltage or current considering one source at a time and replacing all remaining sources (only independent) by their internal resistances if any.

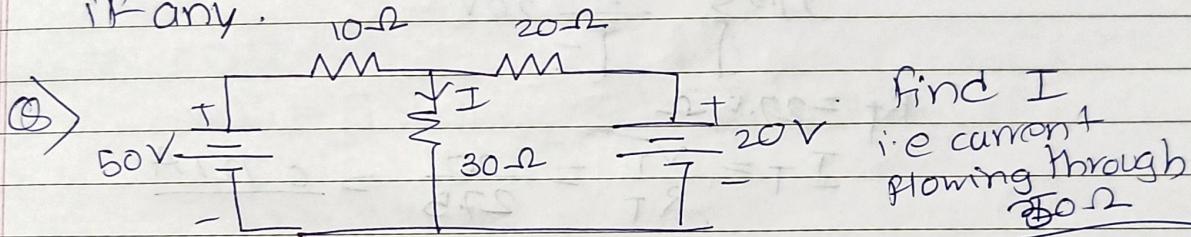

Find I
i.e. current flowing through 30Ω

Step 1) Consider 50V volt source.

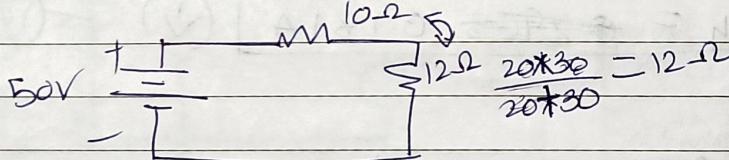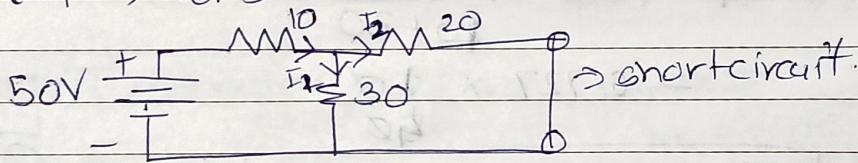

$$50V \frac{+}{-} \left\{ \begin{array}{l} 10\Omega \\ 30\Omega \end{array} \right\} 20\Omega \rightarrow \text{short circuit.}$$

$$I_T = \frac{V_T}{R_T} = \frac{50}{22} = 2.272A$$

$$\boxed{I_T = 2.272A}$$

by CDR


~~$$I_1 = \frac{2.272 \times 20}{20 + 30}$$~~

$$\boxed{I_1 = 0.908A \quad (\downarrow) \quad \textcircled{1}}$$

voltage source \rightarrow short circuit
 current source \rightarrow open circuit

PAGE No.	/ / /
DATE	

Step II) Consider 20V volt source.

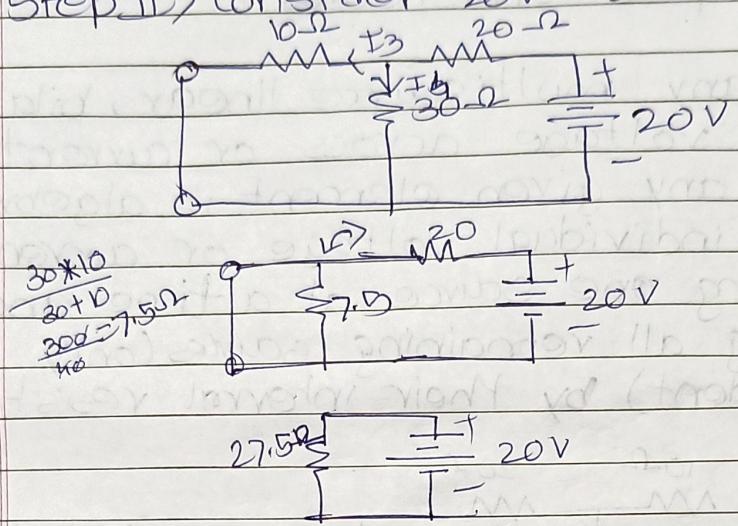

$$R_T = 27.5 \Omega$$

$$I_T = \frac{V_T}{R_T} = \frac{20}{27.5} = 0.727 A$$

by CDR

$$I_y = I_T \times \frac{10}{10 + 30}$$

$$= 0.727 \times \frac{10}{40}$$


$$I_y = 0.181 A \quad (V) \quad (1)$$

Step III) Final current I


$$I = I_1 + I_y \quad \dots \text{from } (1) \text{ & (1)}$$

$$I = 0.908 + 0.181$$

$$I = 1.089 A \quad \checkmark$$

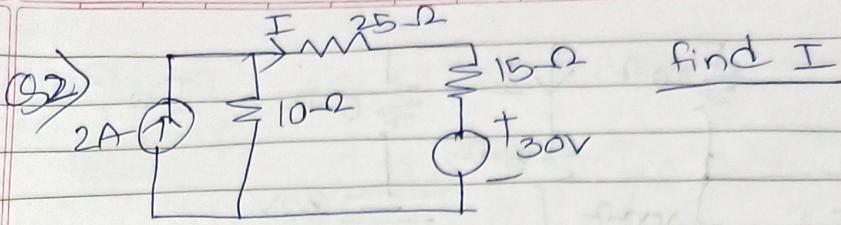

Step I) Consider 2A current source.

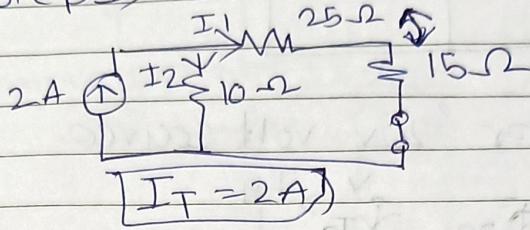



by CDR

$$I_1 = \frac{I \times 10}{10 + 40} \rightarrow \text{current branch} = \frac{25 + 15}{25 + 15 + 10} = 40$$

$$I_1 = 2 \times \frac{10}{10 + 40}$$

$[I_1 = 0.4A] \rightarrow$

Step II) Consider 30V volt source.

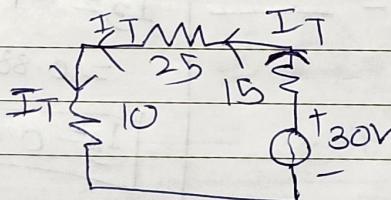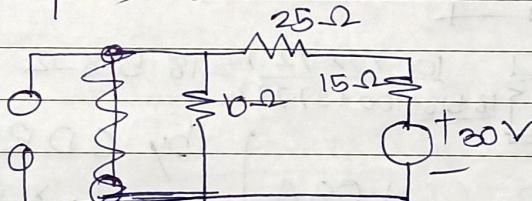

$$R_T = 25 + 15 + 10 = 50 \Omega$$

$$V = 30V$$

$$IT = \frac{30}{50} = 0.6A$$

$I_2 = IT$ $[IT = 0.6A] \leftarrow$

by CDR

No CDR because no current is divided.

Step 3) I?


$$\therefore I = I_2 - I_1$$

$$\frac{25}{25+15} = 0.6 - 0.4$$



$$I_{2B} = 0.2A \quad (\leftarrow)$$

Dummy branch addition

(Q3)

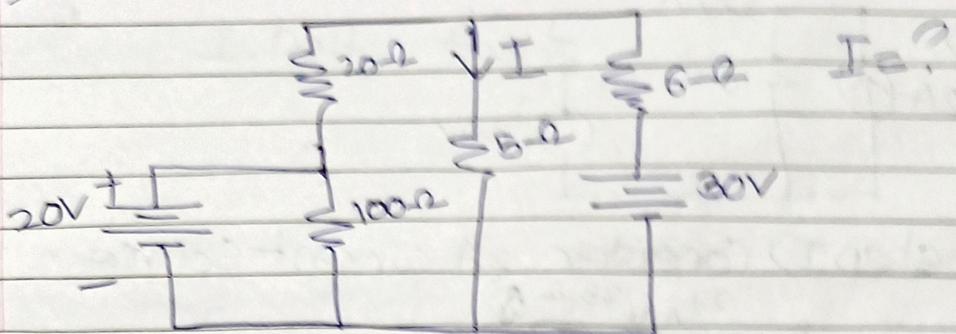

Step I > consider '20v' volt source.

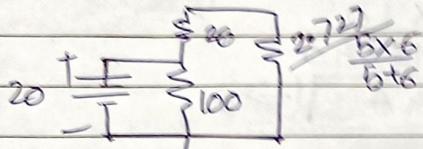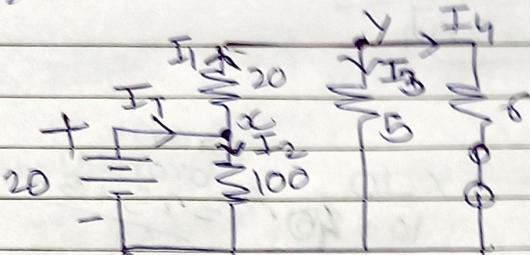

$$20 \text{ } \frac{+}{-} \text{ } 100 \text{ } \frac{+}{-} \text{ } 22.727$$

$$20 \text{ } \frac{+}{-} \text{ } \frac{100 \times 22.727}{18.518 + 22.727} = 18.518 - 2$$

$$R_T = 18.518$$

$$V = 20 \quad I = \frac{V}{R_T} = \frac{20}{18.518} = 1.08A$$

by CDR at x

$$I_1 = I_T \times \frac{100}{100 + 22.727}$$

~~$$= \frac{100}{100 + 22.727} = 0.88A$$~~

~~$$I_1 = 0.88A$$~~


by CDR at y

$$I_3 = I_T \times \frac{6}{6 + 15}$$


$$= 0.88 \times \frac{6}{21} = 0.48$$

$$\boxed{I_3 = 0.48} \checkmark$$

Step II) consider 30 V volt source.

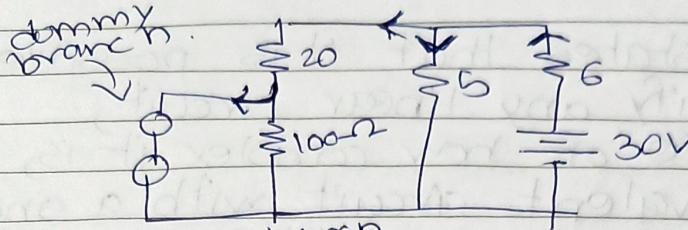

remove dummy branch I_3

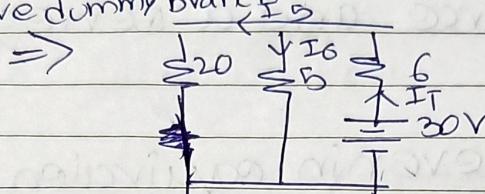


$$\frac{20 \times 5}{20 + 5} = 10$$

$$R_T = 6 + 20 = 10$$

$$V = 30V$$

$$I_T = \frac{30}{10} = 3A$$

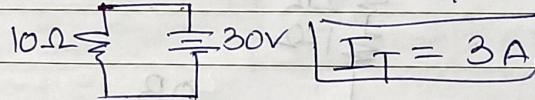

by CDR

$$I_6 = I_T \times \left(\frac{20}{20+5} \right)$$

$$= 3 \times \frac{20}{20+5}$$

$$I_6 = 2.4 A$$

Step III) Total current (I) \rightarrow

$$\therefore I = I_3 + I_6$$


$$= 0.48 + 2.4$$

$$I = 2.88A$$


* Thevenin's Theorem

It states that it is possible to simplify any linear circuit, irrespective of how complex it is, to an equivalent circuit with a single voltage source and a series resistance.

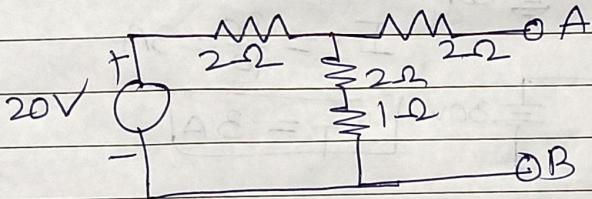(Q1) Find the Thevenin equivalent circuit between the terminals A & B for the circuit shown below.



Step I) Calculation of V_{Th}

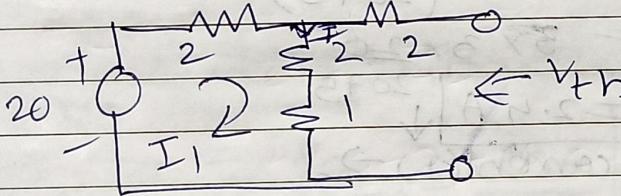

apply KVL in loop ①

$$5I_1 = 20$$

$$I_1 = 20/5$$

$$I_1 = 4A$$

$$\begin{aligned} &\text{Step II} \\ &\text{calc of } R_{Th} \\ & \frac{M^2}{M^2} \leftarrow R_{Th} \\ & \frac{1}{2} \leftarrow R_{Th} \\ & \text{(short } B\text{)} \\ & (2||3) + 2 \end{aligned}$$

$$\therefore R_{Th} = \frac{2 \times 3}{2+3} + 2$$

$$R_{Th} = 3.2 \Omega$$

by deactivating
all sources

$$\therefore V_{Th} = I_1 \times (2+1)$$

$$= 4 \times 3$$

$$V_{Th} = 12V$$

Thevenin \Rightarrow



- ① V_{Th}
- ② Z_{Th}
- ③ Circuit

PAGE NO.


DATE

Refer

Thevenin's equivalent circuit

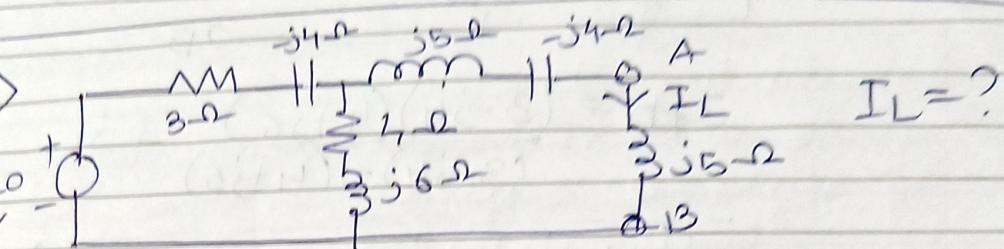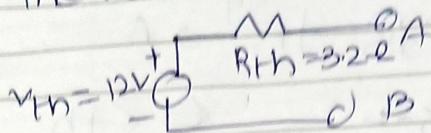

Step I) Calculation of V_{Th}

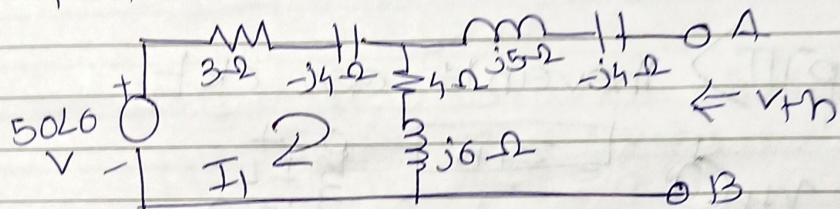

by applying KVL in loop ①


$$\begin{aligned}
 -50\angle 0^\circ + 3I_1 - j4I_1 + 4I_1 + j6I_1 &= 0 \\
 (7 + j2)I_1 &= 50\angle 0^\circ \\
 I_1 &= \frac{50\angle 0^\circ}{7 + j2}
 \end{aligned}$$

$$I_1 = 6.868 \angle -15.945^\circ$$

$$\begin{aligned}
 V_{Th} &= I_1 \times (4 + j6) \\
 &= (6.868 \angle -15.945^\circ) \times (4 + j6)
 \end{aligned}$$

$$V_{Th} = 49.525 \angle 40.364^\circ$$

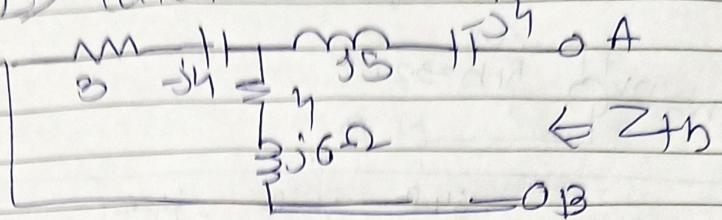
Step II \rightarrow calculation of Z_{th} .



$$Z_{th} = \frac{(3 - j4)(4 + j6)}{(3 - j4) + (4 + j6)} + j1$$

$$Z_{th} = 4.831 \angle -1.118^\circ$$

Step III \rightarrow Therein's law ckt

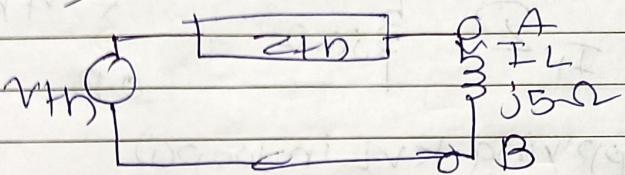


$$I_L = \frac{V_{th}}{Z_{th} + Z_L}$$

Load current


$$= \frac{3.9.525 \angle 40.36^\circ}{(3.831 \angle -1.118) + j5}$$

$$I_L = 7.193 \angle -5.081^\circ$$

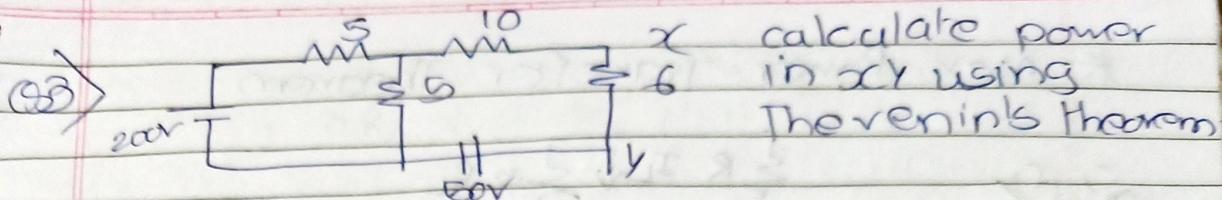

calculate power
in V using
Thevenin's theorem

Step I) Calculation of V_{TH} .

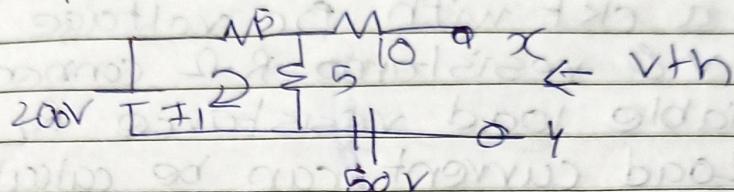

apply KVL.

$$I_1 = \frac{200}{5+5} = \frac{200}{10} = 20A$$

$$V_{TH} = I_1 \times R = 20 \times 5 = 100V$$

$$\boxed{V_{TH} = -50V}$$

Step II) Calculate R_{TH} .

$$\begin{aligned} R_{TH} &= (5||5) + 10 \\ &= \frac{5 \times 5}{5+5} + 10 \\ &= \frac{25}{10} + 10 \\ &= 2.5 + 10 = 12.5\Omega \end{aligned}$$

$$\boxed{R_{TH} = 12.5\Omega}$$


Step 3) $I_L = \frac{-50V}{12.5+6} = \frac{-50}{18.5} = -2.702$

$$\text{Power} = I^2 R$$

$$= (-2.702)^2 \times 6$$

$$= 43.74$$

* Max Power Transfer Theorem

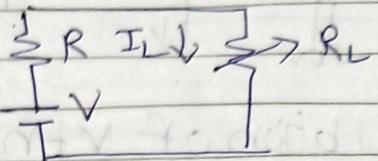

Consider a ckt with DC voltage source V & resistance R -Ω connected to variable load resistance R_L

Load current can be calculated here as

$$I_L = \frac{V}{R + R_L}$$

The power consumed by the load resistance R_L is,

$$\begin{aligned} P &= I_L^2 R_L \\ &= \left(\frac{V}{R + R_L} \right)^2 R_L \end{aligned}$$

If R_L is changed, I_L will also change and at a particular value of R_L the power transferred to the load will be maximum. Hence the power depends on the value of R_L . To get the value of R_L at which power will be max; let's differentiate above eqn of power w.r.t R_L & equate to zero

$$\therefore \frac{dP}{dR_L} = 0$$

$$d \times^2 (SOP-5) =$$

$$N.C.E.N. =$$

$$\therefore \frac{d}{dR_L} \left[\frac{V}{R+R_L} \right]^2 - R_L = 0$$

$$V^2 \frac{d}{dR_L} \left[\frac{R_L}{(R+R_L)^2} \right] = 0$$


after solving this we get,

$$R + R_L - 2R_L = 0$$

$$\therefore [R_L = R]$$

Thus when load resistance is equal to rest of the ckt; max power transfer takes place.

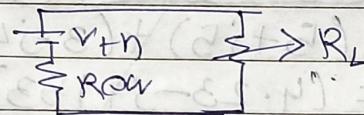we represent the complex network with Thevenin's ckt



If we compare this ckt with above ckt diagram we get,

$$[R_L = R_{th}] \quad \dots \text{for max power transfer}$$

And max power will be calculated as:-


$$P_m = \left[\frac{V_{th}}{R_{th} + R_L} \right]^2 \cdot R_L$$

$$\text{with } R_L = R_{th}$$

$$P_m = \left[\frac{V_{th}}{2R_{th}} \right]^2 \cdot R_{th}$$


$$P_m = \frac{V_{th}^2}{4R_{th}} \text{ watts.}$$

(Q1)

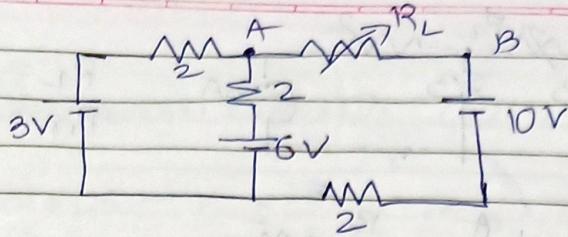


calculate R_L so
the max power
is transformed

→

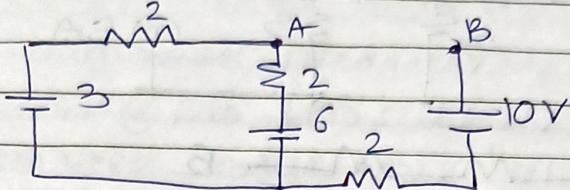


$$I_1 = \frac{6-3}{2} = \frac{3}{2} A$$

$$I_2 = \frac{10}{2} = 5A$$

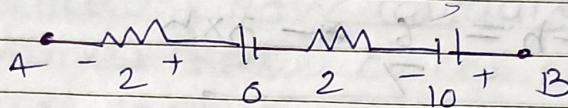


$$V_{th} = 2 \times \frac{3}{2} + 10 - 6$$

$$\boxed{V_{th} = 5.5V}$$

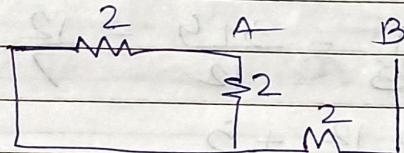


$$R_{eq} = 3\Omega$$


$$\therefore R_L = 3\Omega$$

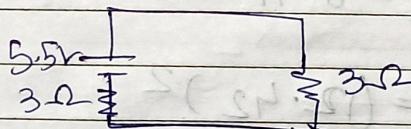
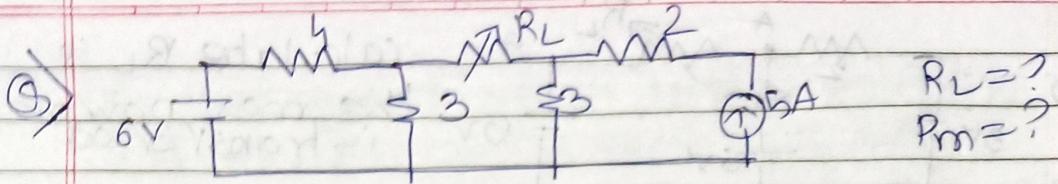
$$P = \frac{(5.5)^2}{4 \times 3\Omega} = \frac{30.25}{12} = 2.52W$$




Soln:

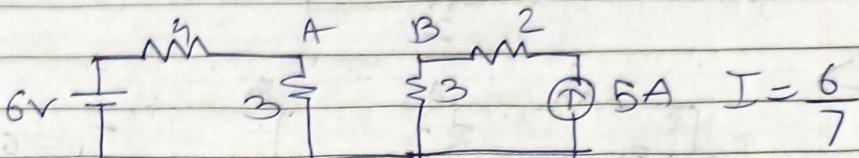

$$A \xrightarrow{+} \frac{M}{3} - \frac{M}{3} B$$

$$V_{th} = \frac{6}{7} - 3 \times 5$$

$$\boxed{V_{th} = -12.42 V}$$

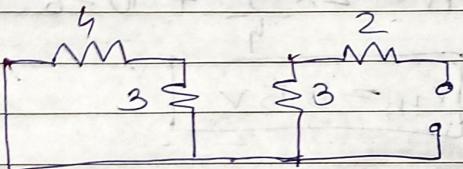

$$\frac{1}{4} + \frac{1}{3} = \frac{3+4}{12} = \frac{12}{7}$$

$$R_{eq} = \frac{12}{7} + 5$$

$$= 6.71 \Omega$$

$$R_L = 6.71 \Omega$$

$$P_m = \frac{(12.42)^2}{4 \times 6.71}$$

$$= \frac{164.25}{26.84}$$

$$= 5.74 W$$

* Thevenin's Rule.

Steps -


- ① Remove load resistance & calculate voltage at open circuited terminals
This V_{Th} is V_{Th} .
- ② Remove sources also. Replace V_{Th} source by S-C & current source by open circuit. Now calculate equivalent resistance (R_{eq}) of the ckt as if you are looking into the ckt from open circuited terminals.
- ③ Draw Thevenin's eqv ckt
- ④ Connect R_L to eqv ckt
- ⑤ calculate load current by using

$$I_L = \frac{V_{Th}}{R_{eq} + R_L}$$

* Norton's Theorem

Any two terminal active network containing voltage source and resistances, when viewed from its output terminals, is equivalent to the constant current source and a parallel resistance. The constant current source is equal to the current which would flow in a short circuit placed across the terminals; and the parallel resistance is the resistance of the network when viewed from those open circuited terminals after all voltage & current sources have been removed and replaced by their internal resistance."

Norton's equivalent circuit is -

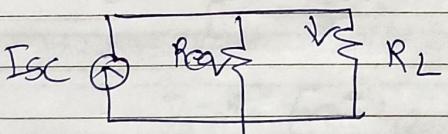

$$\therefore I_L = \frac{I_{SC} \times R_{eq}}{R_{eq} + R_L}$$





* Steps -


- ① Remove R_L and short circuit the terminals.
- ② Calculate current through short circuit (I_{SC})
- ③ Remove S.C, replace sources and calculate r_{eq} as done in Thevenin's theorem.
- ④ Draw the Norton's equivalent circuit with I_{SC} & r_{eq} parallel with each other
- ⑤ Connect R_L in parallel with the curr ckt
- ⑥ Calculate I_L using formula,

$$I_L = I_{SC} \times \frac{r_{eq}}{r_{eq} + R_L}$$

Dual of Thvenins: Norton's eqn ckt

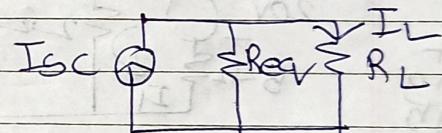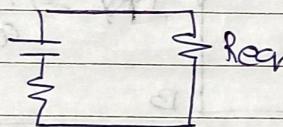


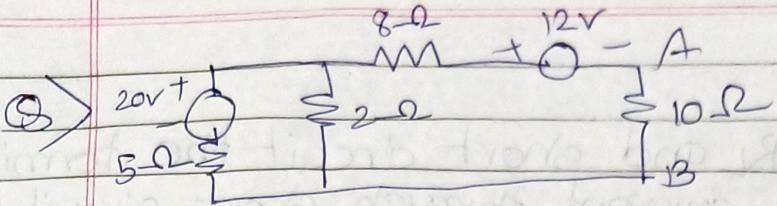⇒ Any linear circuit containing several energy sources and resistances can be replaced by a single constant current generator in parallel with a single Resistor.??



Step I) Calculation of R_{th}

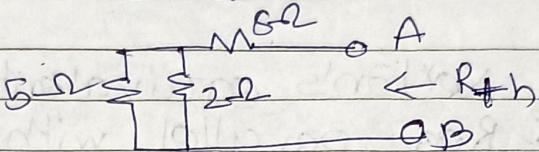'calculate
 R_{th} at A-B
by replacing
all voltage
& current
sources.'




$$R_{th} = \frac{5 \times 2}{5+2} + 8 =$$

$$\boxed{R_{th} = 9.4285}$$

Step II) Calculation of I_N

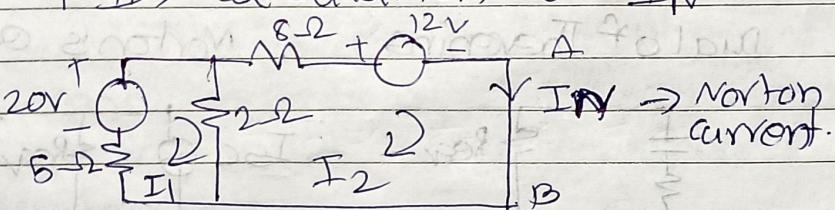Remove
load
& short
AB &
current
flowing
through
it is I_N



Apply KVL in loop ①

$$7I_1 - 2I_2 = 20V - 0$$


apply KVL in loop ②

$$10I_2 - 2I_1 = -12 - ①$$

$$\therefore \underline{I_1 = 2.66} \quad \underline{I_2 = -0.66}$$

$$\therefore \boxed{I_N = I_2 = -0.66 A}$$

Step III) Norton equivalent circuit

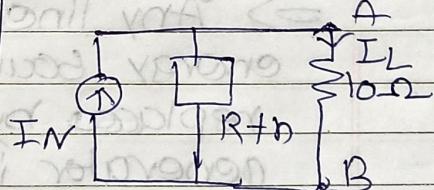



\therefore by CDR

$$I_L = \frac{I_N \times R_{th}}{R_{th} + 10}$$


$$= -0.66 \times \frac{9.428}{9.428 + 10}$$

$$\boxed{I_L = -0.320 A}$$

$$\boxed{I_L = 0.320 A}$$

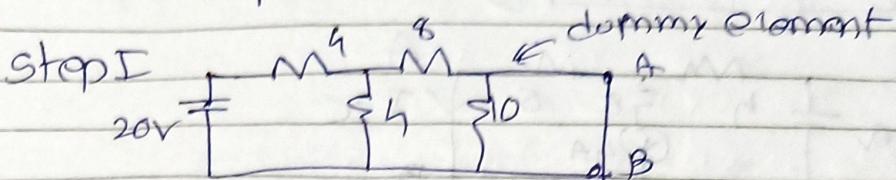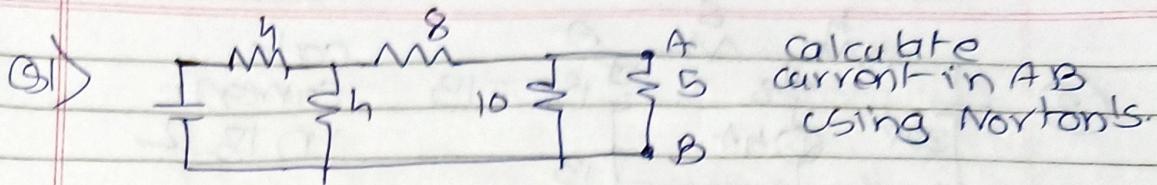

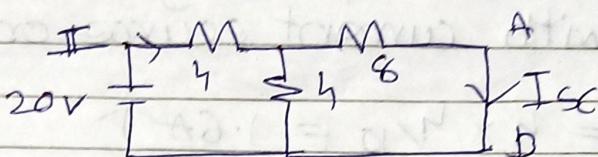Now 10Ω has become redundant.
 \therefore CKT will be -




$$(8||4) + \frac{4}{12} = \frac{32}{12} + 4 = 6.667\Omega$$

$$\therefore I = \frac{V}{R} = \frac{20}{6.667} = 3A$$

by CPR

$$I_{SC} = I \times \frac{4}{4+8} = 3 \times \frac{4}{12} = 1A$$

Step II) calculate Req

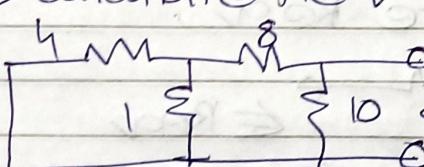


$$(4||4) = 2$$

$$2 + 8 = 10$$


$$(10||10) = 5 = Req$$

Step III) equivalent circuit is -

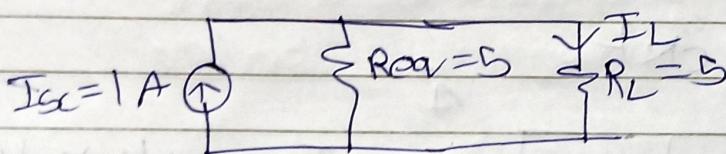


$$\therefore I_L = 1 \times \frac{5}{5+5}$$

$$I_L = 0.5A$$

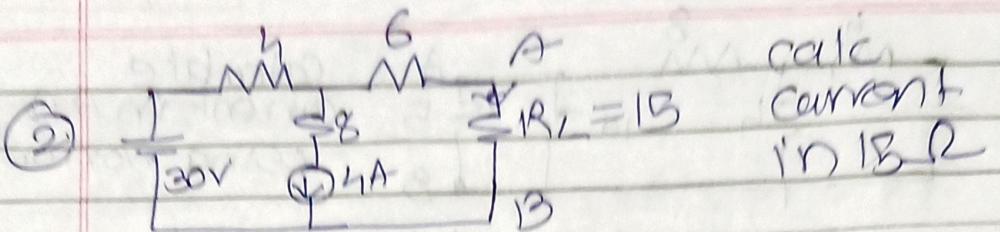

calc.
current
in R2

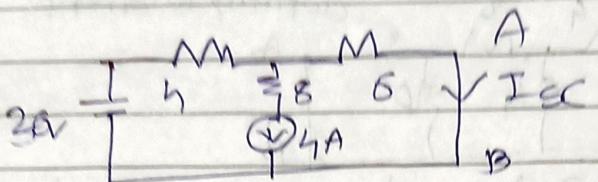

Step I) calculate I_{SC} by using superposition

- I_{SC}^1 with current source only.


$$I_{SC}^1 = 4 \times \frac{4}{10} = 1.6 A \uparrow$$

- I_{SC}^{II} with voltage source only

$$I_{SC}^{II} = 30/10 = 3 A \downarrow$$


$$\therefore I_{SC} = I_{SC}^{II} - I_{SC}^1 = 3 - 1.6 = 1.4 A$$

Step II) To calculate R_{eq}

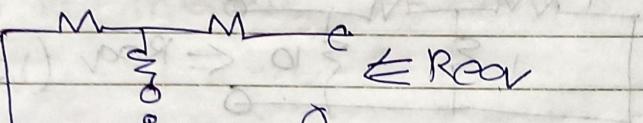

$$\therefore R_{eq} = 4 + 6 = 10 \Omega$$

Step III) ear crf

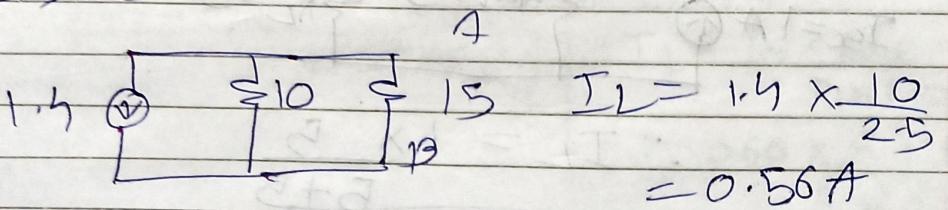


$$I_L = 1.4 \times \frac{10}{25} = 0.56 A$$

* Millman's Theorem.

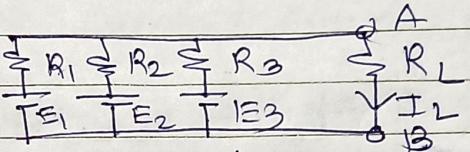a) As applicable to voltage source.

This theorem is a combination of Thevenin's & Norton's theorem.

It is used for finding common voltage across any n/w which contains a no. of parallel voltage sources \rightarrow



The common voltage V_{AB} which appears across the o/p terminals A & B is affected by the voltage sources $E_1, E_2 \& E_3$. The value of the voltage is given by:

$$V_{AB} = \frac{E_1/R_1 + E_2/R_2 + E_3/R_3}{1/R_1 + 1/R_2 + 1/R_3} = \frac{I_1 + I_2 + I_3}{G_1 + G_2 + G_3} = \frac{\Sigma I}{\Sigma G}$$

The voltage V_{AB} represents the Thevenin's voltage V_{Th} .

The resistance R_{Th} or R_{eq} can be calculated as usual, by replacing each vltg source by a terminal A & B, this load current is given by

$$I_L = \frac{V_{Th}}{R_{eq} + R_L}$$



b) As applicable to current sources.

This theorem is applicable to a mixture of parallel voltage & current sources that are reduced to a single final equivalent source which is either a constant current or a constant voltage source. The theorem can be stated as -

"Any no. of constant current sources which are directly connected in parallel can be converted into a single current source whose value is algebraic sum of the individual source currents and whose total internal resistance equals the combined individual source resistances in parallel".



$$\boxed{V_{AB} = \left[\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} \right] = \sum \frac{v}{R}}$$

$$\boxed{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \sum \frac{1}{R}}$$

$$\boxed{I_L = \frac{V_{Th}}{R_{eq} + R_L}}$$
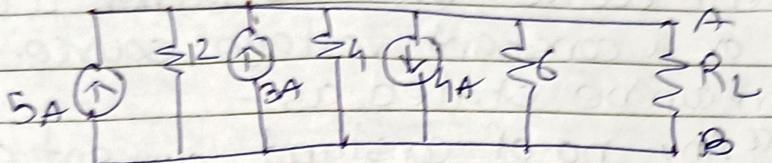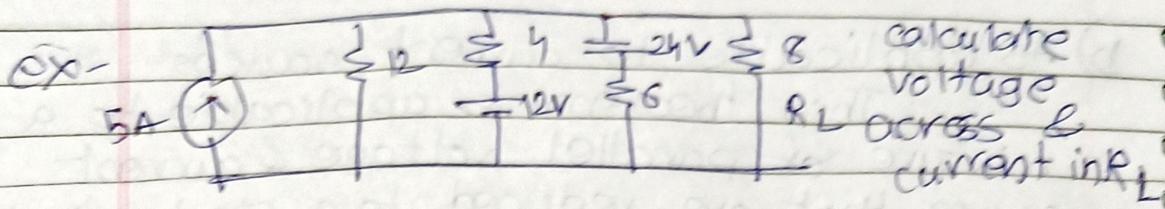
$$R_{eq} = R_{Th} = \frac{1}{R_1} + \frac{1}{R_2} \dots$$






$$\therefore \text{Net current} = 6 + 3 - 4 = 5 \text{ A}$$

$$\text{combined res} = \frac{12}{11} \parallel \frac{16}{11} = 2 \Omega$$


\therefore simplified circuit is,

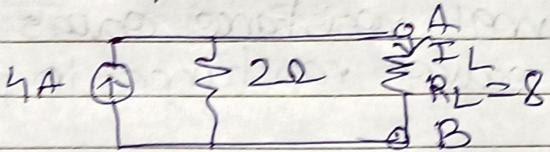


$$\therefore I_L = 4 \times \frac{2}{2+8} = 0.8 \text{ A}$$

$$V_L = 8 \times 0.8 = 6.4 \text{ V}$$

OR convert it into voltage source.

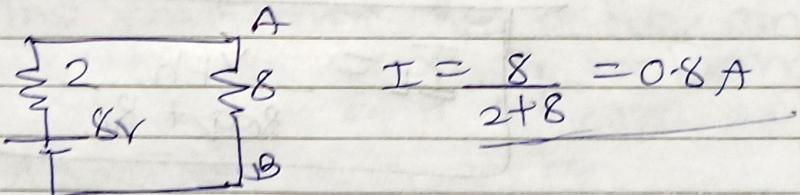

* Generalized form of Millman's Th.

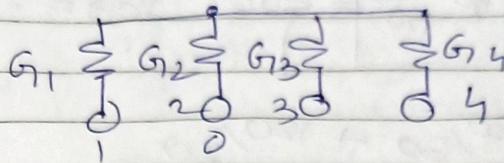


Consider no. of admittances $G_1, G_2, G_3, \dots, G_n$ terminate at common point o' . The other ends of admittances are named as $1, 2, 3, \dots, n$.

Let o be any other point in the network.

Acc to this theorem, the vltg. drop from o to o' ($V_{oo'}$) is given by -

$$V_{oo'} = V_{o_1}G_1 + V_{o_2}G_2 + V_{o_3}G_3 + \dots + V_{o_n}G_n$$

$$G_1 + G_2 + G_3 + \dots + G_n$$

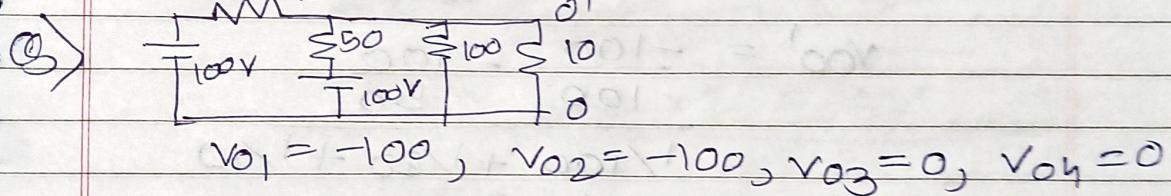


$$V_{o_1} = -100, V_{o_2} = -100, V_{o_3} = 0, V_{o_4} = 0$$

$$\therefore V_{oo'} = (-100/100) + (-100/50) + (0/100) + (0/10)$$

$$= (-1/1) + (-2/1) + 0 + 0$$


$$= -3V$$

Method-II

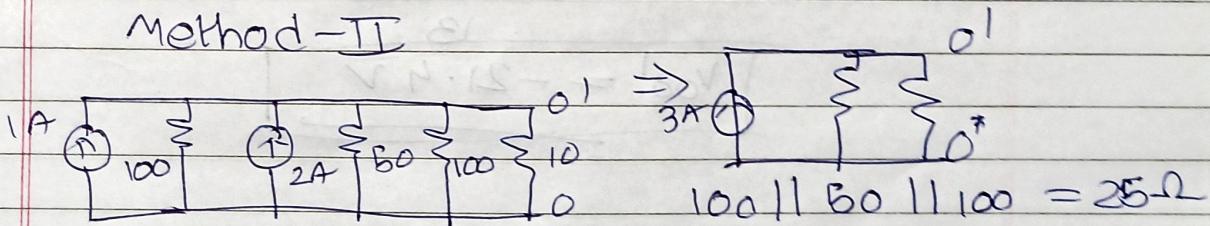

$$I_L = \frac{3 \times 25}{35} = 2.1428 A$$
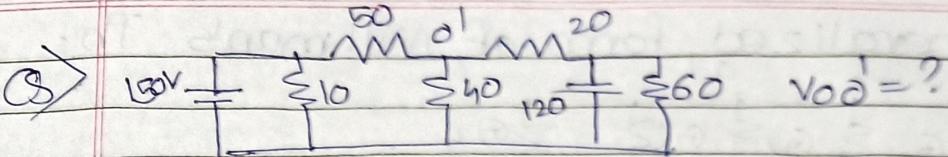
$$\therefore V_{oo'} = 10 \times 2.1428 = 21.4 V$$




$$\Rightarrow \text{v}_{00} = \frac{-150/50 + 120/20}{1/50 + 1/40 + 1/20}$$

$$= \frac{-3 + 6}{0.02 + 0.025 + 0.05}$$

$$= \frac{3}{0.095}$$

$$V_{ool} = 31.5V$$

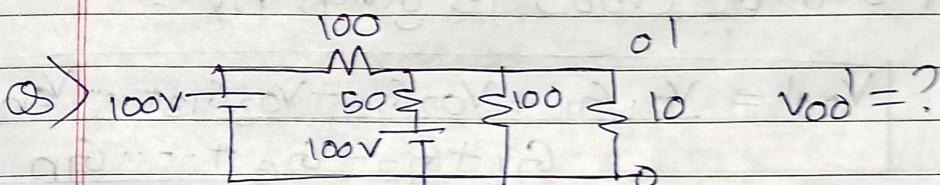


$$v_{00} = \frac{-100}{100} - \frac{100}{50}$$

$$\begin{aligned}
 & \frac{1}{100} + \frac{1}{50} + \frac{1}{10} \\
 &= \frac{-1 - 2}{1 + 2 + 10} \\
 &= \frac{-3}{13} \times 100
 \end{aligned}$$

$$V_{OD} = -21.4 \text{ V}$$

a)

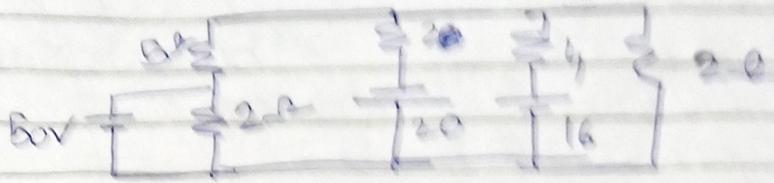

Find volt & current through 2-Ω res.

$$V_E = \frac{50}{6} - \frac{20}{2} + \frac{16}{4}$$
$$= \frac{V_6 + V_{2\Omega} + V_4}{V_6 + V_{2\Omega} + V_4}$$
$$= 26V$$

$$R_{Th} = \frac{1}{V_6 + V_{2\Omega} + V_4} = 2\Omega$$

$$I_{2\Omega} = \frac{26}{2+2} = 6.5A$$

$$V_L = I_{2\Omega} \times 2 = 13V$$

$$21 + 03 = \frac{24}{0} = 00$$

M + O + N

VAS

$$21 + 03 = \frac{24}{0} = 00$$

PV + oPV + PV

$$42.2 - 25 = 17$$

$$V = 8 \times 17 = 4M$$

Unit - 3 Analysis of Transient Response in Circuits.

PAGE NO.	/ /
DATE	

Initial condns.

Time periods $\begin{pmatrix} - \\ + \end{pmatrix}$ 0

- (1) Just before switching ($t = -\infty$ to $t = 0^-$)
- (2) Just after switching ($t = 0^+$)
- (3) After switching ($t > 0$)

1) Initial cond'n for R

$$\Rightarrow V = iR$$

2) Initial cond'n for L

$$\Rightarrow V = L \frac{di}{dt}$$

$$i(t) = \frac{1}{L} \int_0^t V(t) dt + i(0)$$

$i(0)$ is initial current through L

If no current through L at $t = 0^-$

L will act as open circuit

If current I_0 is flowing through L at $t = 0^-$,
L will act as current source of I_0 A.

3) Capacitor

$$\Rightarrow V = \frac{1}{C} \int_0^t i(t) dt + V(0)$$


$V(0)$ is initial voltage across C.

If there is no voltage across capat $t = 0^-$
C will act as short circuit.

If initially the capacitor is charged
to V_0 at $t = 0^-$


C will act as voltage source of V_0

Element with
initial cond'n

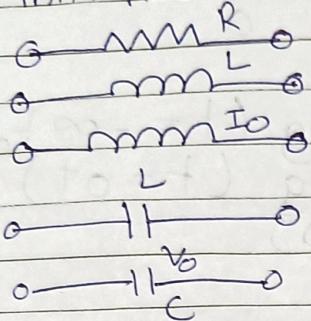


Equi ckt at

$$t=0^+$$

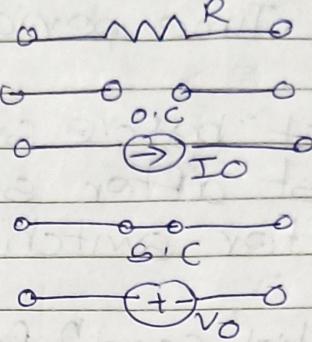

* Procedure for evaluating initial condns.


- ① Draw the equi ckt at $t=0^-$. Before switching take place (i.e. for $t=-\infty$ to $t=0^-$) the n/w is under steady state cond'n. Hence find current flowing through inductors $i_L(0^-)$ & vltg across capacitor $v_C(0^-)$
- ② Draw the equi n/w at $t=0^+$, i.e., immediately after switching. Replace all inductors with O.C. or with current sources $i_L(0^+)$ & replace all capacitors by S.C. or vltg sources $v_C(0^+)$. Keep resistors as it is.
- ③ Initial vltg or currents are determined from the equi n/w at $t=0^+$.
- ④ Initial conditions, i.e. $\frac{di}{dt}(0^+)$, $\frac{dv}{dt}(0^+)$, $\frac{d^2i}{dt^2}(0^+)$, $\frac{d^2v}{dt^2}(0^+)$ are determined by writing into differential eqns for the n/w for $t>0$, i.e. after the switching action by making use of initial cond'n.

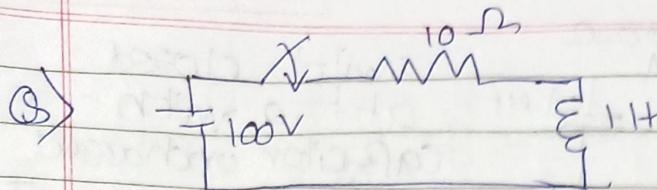

In the given n/w switch is closed at $t=0$ with no current in inductor, find i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t=0^+$

\rightarrow At $t=0^-$, no current flow through L
 $\therefore i(0^-) = 0$


\rightarrow At $t=0^+$ the n/w will be

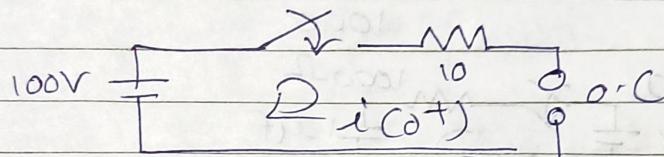

Inductor acts as 0-C

$$\therefore i(0^+) = 0$$

\rightarrow At $t > 0$

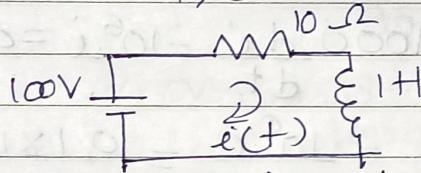

$$100 - 10i - \frac{di}{dt} = 0 \quad \text{(1)}$$

$$\frac{di}{dt} = 100 - 10i - 6$$

\rightarrow At $t=0^+$


$$\frac{di}{dt}(0^+) = 100 - 10i(0^+)$$

$$\boxed{\frac{di}{dt}(0^+) = 100 \text{ A/S}}$$


Difff eqn(2)

$$\frac{d^2i}{dt^2} = -10 \frac{di}{dt}$$

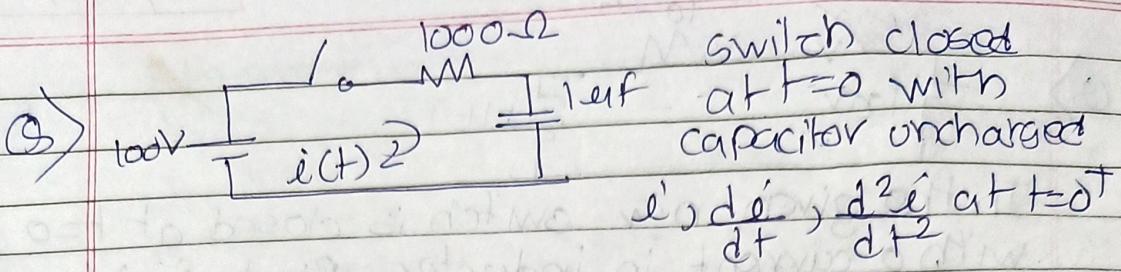
$$\boxed{\frac{d^2i}{dt^2}(0^+) = -10 \frac{di}{dt}(0^+) = -1000 \text{ A/S}^2}$$



Soln: At $t=0^+$, no voltage through C

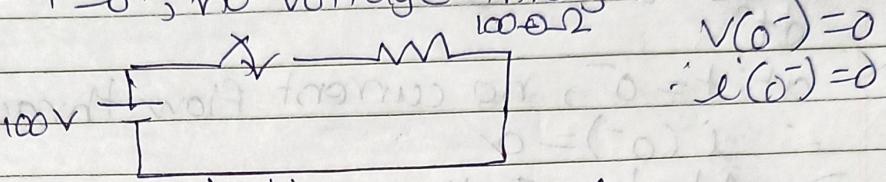
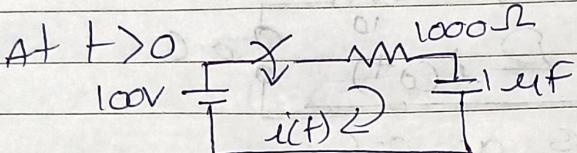
$$i(0^+) = \frac{100}{1000} = 0.1 \text{ A}$$



$$100 - 1000i - 10^6 \int i(t) dt = 0$$

$$\text{At } t=0^+ \quad 0 - 1000 \frac{di}{dt} - 10^6 i = 0$$

$$\frac{di}{dt} = \frac{10^6 i}{1000} = 0.1 \times 10^6$$

$$\frac{di(0^+)}{dt} = -100 \text{ A/s}$$


$$-1000 \frac{d^2i}{dt^2} - 10^6 \frac{di}{dt} = 0$$

$$(t_0) i(0^+) \frac{dt}{dt} = (t_0) \frac{di}{dt}$$


$$-1000 \frac{d^2i}{dt^2} = 10^6 \times (-100)$$

$$\frac{d^2i}{dt^2} = \frac{10^6 \times 100}{1000}$$


$$\frac{d^2i}{dt^2} = 10^5$$

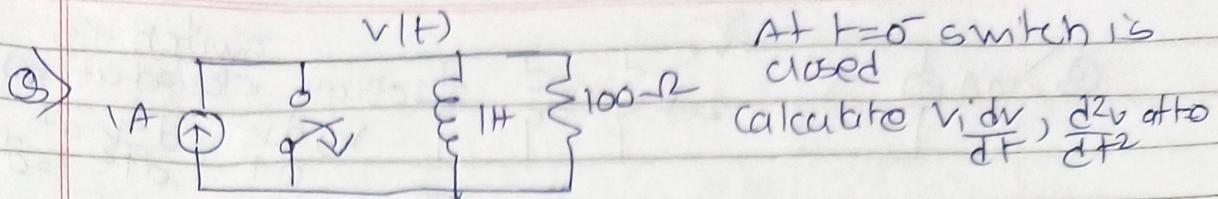

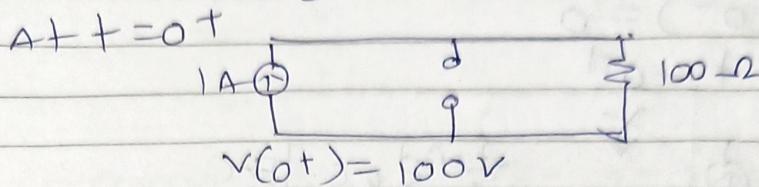\rightarrow At $t=0^-$ $i_L(0^-) = DA$. No current through L



At $t>0$

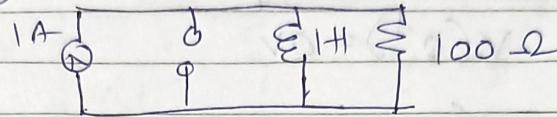

$$I_1 = \frac{1}{L} \int v dt$$

$$I_2 = V/100$$

$$\frac{1}{L} \int v dt + \frac{V}{100} = I$$

$$V_L V + \frac{1}{100} \frac{dv}{dt} = 0$$

$$\frac{dv}{dt} = -\frac{V}{2} \times 100$$

$$\frac{dv}{dt} = -100V$$

At $t=0^+$


$$\frac{dv}{dt}(0^+) = -10^4 V/S$$

$$\frac{d^2v}{dt^2} = -100 \frac{dv}{dt}$$

At $t=0^+$

$$\frac{d^2v}{dt^2}(0^+) = -100 \times (-10^4)$$


$$= 10^6 V/S^2$$

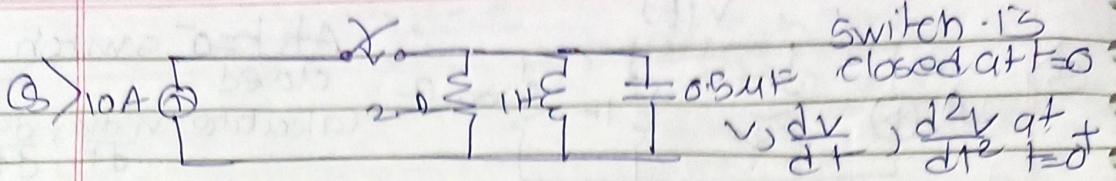

$$\text{Soln} \rightarrow A + t = 0$$


$$v(0^-) = 0$$

$$A + t = 0^+$$

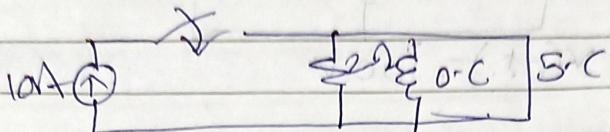

$$v(0^+) = 0V$$

$$A + t > 0$$

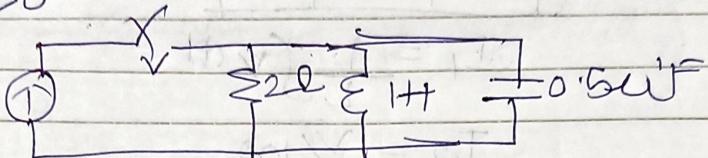

$$V_2 + V_L \int v dt + C \frac{dv}{dt} = 10$$

$$A + t = 0^+$$

$$\frac{v(0^+)}{2} + \frac{1}{L} \int v(0^+) dt + C \frac{dv}{dt} = 10$$

$$\frac{dv}{dt} = \frac{10}{0.5 \times 10^{-6}}$$

$$\frac{dv}{dt} = 2 \times 10^7 \text{ V/S}$$

$$V_2 \frac{dv}{dt} + \frac{1}{L} v + \frac{C dv^2}{dt} = 0$$


$$\frac{1}{2} 2 \times 10^7 + V_L v(0^+) + 0.5 \times 10^{-6} \frac{d^2 v}{dt^2} = 0$$

$$10^7 + 0.5 \times 10^{-6} \frac{d^2 v}{dt^2} = -10^7$$

$$\frac{d^2 v}{dt^2} = -2 \times 10^{13} \text{ V/S}^2$$

* Transient Response.

1) R-L circuit

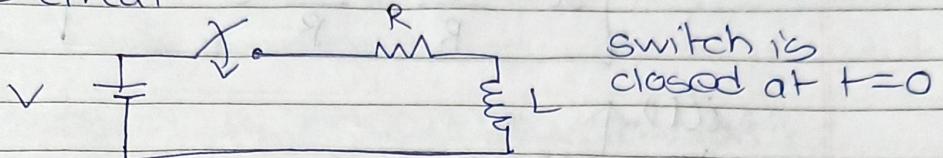

\therefore current in inductor at $t=0^- = 0$.

$$V - \frac{1}{L} \int i(t) dt = R i(t) \quad t > 0$$

KVL earn at $t > 0$

$$V - R i(t) - L \frac{di}{dt} = 0 \quad - \text{Linear D.E. order 1}$$

If variables are separated

$$(V - R i) dt = L di$$

$$\frac{L}{V - R i} di = dt$$

integrating both sides

$$-\frac{L}{R} \ln(V - R i) = t + K - ①$$

To get value of K , at $t=0, i=0$


$$-\frac{L}{R} \ln V = K - ②$$

Put ② in ①

$$-\frac{L}{R} (\ln V - R i) = t - \frac{L}{R} \ln V.$$

$$V - R \cdot i = V_0 e^{-R/L t}$$

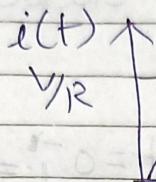
$$\boxed{i = \frac{V}{R} - \frac{V}{R} e^{-R/L t}}$$



Voltage across R

$$V_R = R \cdot i = R \times \frac{V}{R} (1 - e^{-R/L t})$$

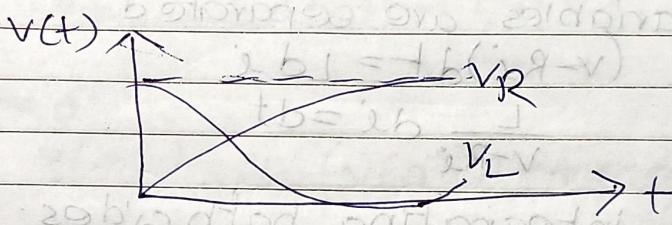
$$V_L = V \cdot e^{-R/L t} \quad \text{for } t > 0$$




$\frac{V_L}{V_R}$ \rightarrow time constant of R-L circuit.

$$V_{out} \cdot \frac{1}{1 + \frac{t}{\tau}} = (i \cdot R - V_{out}) \cdot \frac{1}{R}$$

2) R-C circuit

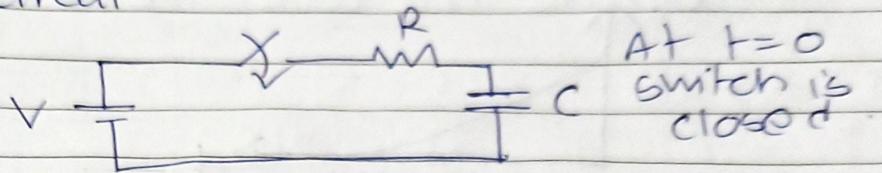

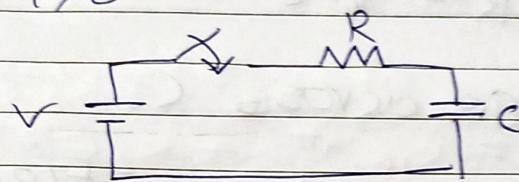\therefore Capacitor is uncharged initially
for $t > 0$



$$V - Ri - \frac{1}{C_0} \int i dt = 0$$

$$0 - Rdi - \frac{i}{C} = 0$$

$$\frac{di}{dt} + \frac{1}{RC} i = 0$$

Int both sides

$$\ln i = -\frac{1}{RC} t + K$$


$$\text{At } t=0 \quad i = V/R$$

$$\therefore \ln \left(\frac{V}{R} \right) = K$$

$$\therefore \ln i = -\frac{t}{RC} + \ln \left(\frac{V}{R} \right)$$
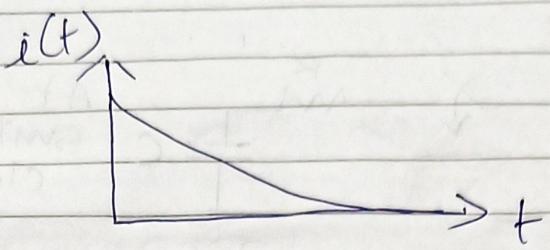
$$i = \frac{V}{R} \cdot e^{-t/RC} \text{ for } t > 0$$






voltage across R
 $v_R = v \cdot e^{-t/RC}$

voltage across C


$$v_C = \frac{1}{C} \int_0^t \frac{v_0}{R} e^{-t/RC} dt$$

$$v_C = -v_0 e^{-t/RC}$$

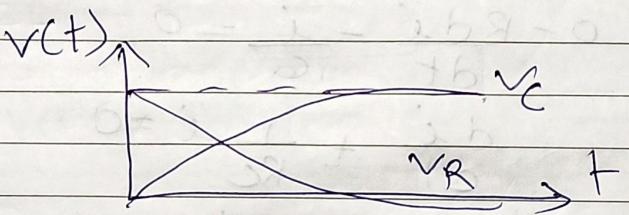

$RC \rightarrow$ Time constant of RC ckt(T)


III) \rightarrow RLC circuit

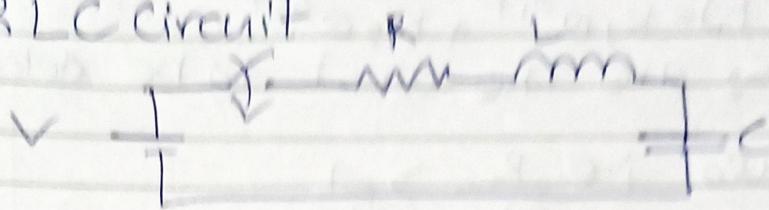

Switch is closed at $t = 0$

Inductor current $i = 0$
capacitor voltage $V = 0$

for $t > 0$

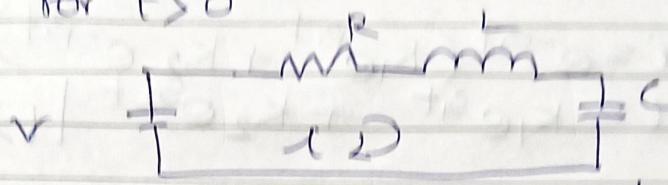

$$V - R\dot{i} - L \frac{d\dot{i}}{dt} - \frac{1}{C} \int i dt = 0$$

diff

$$0 - R\ddot{i} - L \frac{d^2i}{dt^2} - \frac{i}{C} = 0$$

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

2nd order DE

$$s^2 + \frac{Rs}{L} + \frac{1}{LC} = 0$$

$$s_1, s_2 = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$s_1 = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \frac{1}{4\omega^2}} \\ = -\alpha + \beta$$


$$s_2 = -\alpha - \beta$$

$$i(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t}$$

K_1, K_2 are the const to be determined.

I] $\alpha > \omega_0$ i.e. $\frac{R}{2L} > \frac{1}{\sqrt{LC}}$

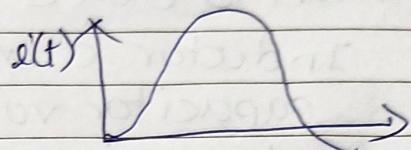Roots are real
& unequal
overdamped condn




Soln is $i = e^{-\alpha t} (K_1 e^{\beta_1 t} + K_2 e^{\beta_2 t})$

or $i = K_1 e^{s_1 t} + K_2 e^{s_2 t} \quad t > 0$

II] $\alpha = \omega_0$

i.e. $\frac{R}{2L} = \frac{1}{\sqrt{LC}}$

Roots are real & equal
critically damped

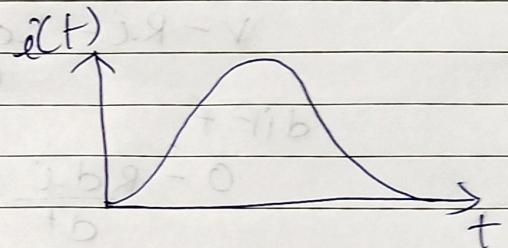


Soln is $i = e^{-\alpha t} (K_1 + K_2 t) \quad t > 0$

III] $\alpha < \omega_0$

i.e. $\frac{R}{2L} < \frac{1}{\sqrt{LC}}$

Roots are complex conjugate.

under damped.

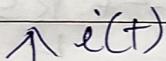

$$i = K_1 e^{s_1 t} + K_2 e^{s_2 t}$$