

ADIC

Assignment-1

Name: Shreerang Mhatre

Rollno: 29

Batch: A2

Sy B.Tech Electrical & Computer

Set 1.3

Q 1) Design an inverting Schmitt trigger to have $V_{UT} = 2.5V$ and $V_{LT} = -2.5V$. If $V_{in} = 10V_{pp}$ and supply voltages $= \pm 15V$. Draw input output waveforms, hysteresis curve with voltages. Assume $R_L = 8.2k\Omega$. Draw neat circuit diagram.

→ Given: $R_L = 8.2k\Omega$
 $V_{UT} = 2.5V$
 $V_{LT} = -2.5V$
 $V_{in} = 10V_{pp}$
Supply $V = \pm 15V$

Soln: $R_L = 8.2k\Omega$


$$V_{sat} = 90\% \text{ of } V_{supply} = 90\% \times 15 = \frac{90 \times 15}{100}$$
$$\therefore V_{sat} = 13.5V$$

$$V_{UT} = \frac{R_2}{R_1 + R_2} (V_{sat}) \Rightarrow 2.5 = \frac{R_2}{R_1 + R_2} (13.5)$$


$$\frac{2.5}{13.5} (R_1 + R_2) = R_2 \Rightarrow R_2 = 1.8k\Omega$$

$$R_{in} = R_1 \parallel R_2 = 1.4k\Omega$$


Circuit Diagram

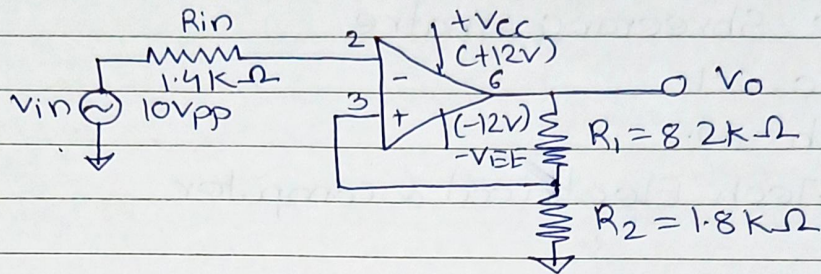

Wave forms

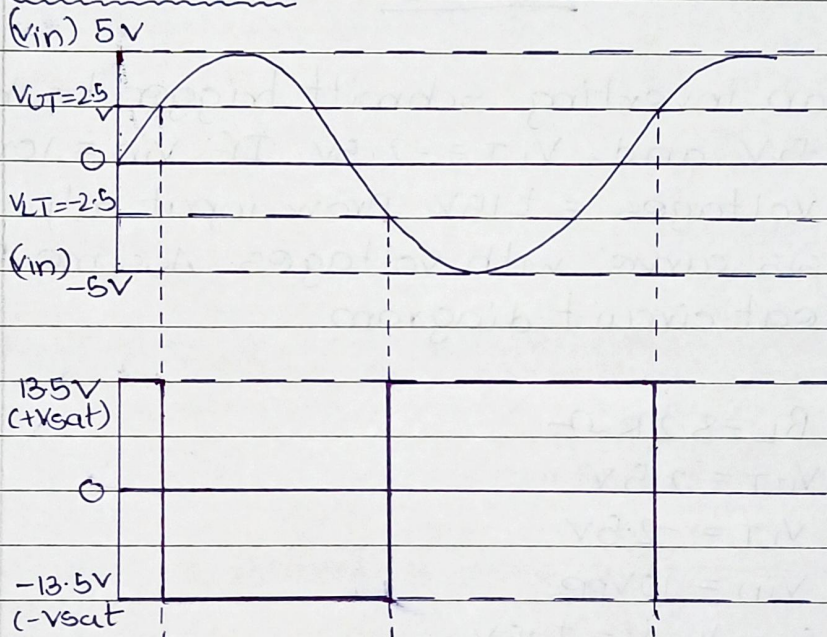

Transfer characteristic (Hysteresis)

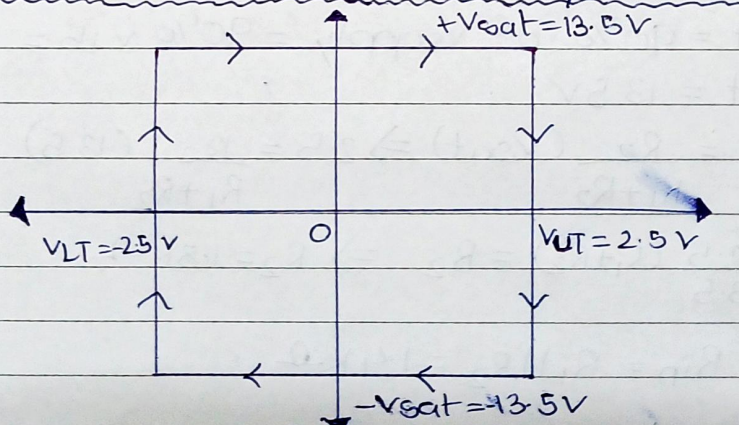

Q 2) Design a square wave and triangular wave generator to operate at frequency of 1.5 KHz. $\beta = 0.5$. Given $R_1 = 10K$, $C = 0.1 \mu F$, $C_F = 0.01 \mu F$. Output has to be $V_{opp} = 5V$. DC gain of integrator is 10. Draw neat circuit diagram indicating all components and wave forms.

→ Given: $F_{sq} = 1.5 KHz$ $R_1 = 10K$ $A = 10$
 $\beta = 0.5$ $C = 0.1 \mu F$
 $C_F = 0.01 \mu F$ $V_{opp} = 5V$

Soln:

$$T = \frac{1}{F_{sq}} = \frac{1}{1500 Hz} = 0.67 ms$$

$$T = 2RC \ln \left(\frac{1+\beta}{1-\beta} \right)$$

$$\frac{1}{1500} = 2R (0.1 \times 10^{-6}) \ln \left(\frac{1+0.5}{1-0.5} \right)$$

$$\therefore R = \frac{1}{3000 (0.1 \times 10^{-6}) \ln \left(\frac{1.5}{0.5} \right)} = 3.0 K\Omega$$

$$\beta = \frac{R_1}{R_1 + R_2} \Rightarrow 0.5 = \frac{10K}{10K + R_2} \Rightarrow R_2 = 10K\Omega$$

$$\therefore R_1 = R_2 = 10K\Omega$$

Now, for integrator,

$$A = \frac{R_F}{R_3} \Rightarrow 10 R_3 = R_F$$

$$V_o = \frac{1}{R_3 C F} \int_0^t v_{in} dt$$

for the first half cycle of square wave generator

$$\text{i.e. } t=0 \text{ to } t = \frac{1}{2(1500)} = \frac{1}{3000} = 0.34 \text{ ms}$$

$$\therefore 2.5 = \frac{1}{-R_3 (0.01 \mu F)} \int_0^{0.34 \text{ ms}} -9 dt$$


$$2.5 = \frac{1}{R_3 (0.01 \times 10^{-6})} (9 (0.34 \times 10^{-3}))$$

$$\therefore R_3 = \frac{9 (0.34 \times 10^{-3})}{25 (0.01 \times 10^{-6})} = 12 \text{ k}\Omega$$

$$\therefore R_F = 10 R_3 = 120 \text{ k}\Omega$$

$\therefore V_{in} = V_o \text{ of sq wave}$
 $\therefore V_{in} = -9 \text{ V}$
 assuming $V_{EE} = -10 \text{ V}$
 $-V_{sat} = 90\% \text{ of } V_{EE}$

Circuit Diagram

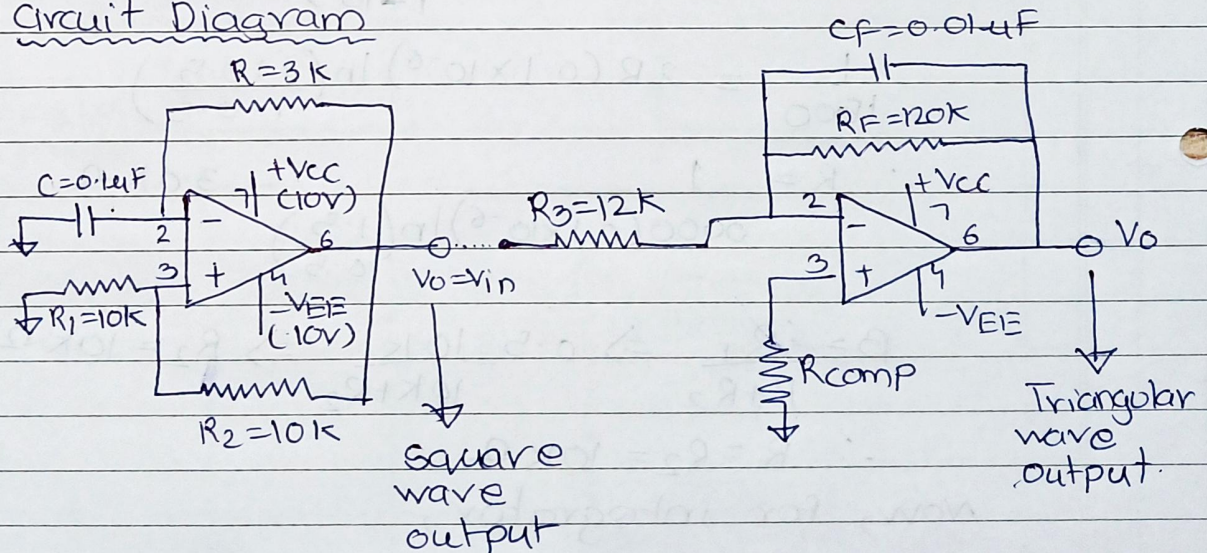

Wave forms

