

Unit 2.

Network Theorems.


Superposition theorem.

KCL, KVL, mesh, nodal analysis give the general methods of n/w analysis. But many of the n/w problems involve only restricted analysis like - finding current in an element for diff. values of resistances, establishing condition for max. power, etc. Although general methods may be used here, but ~~the results~~ it may take time or involve lot of calculations. But using n/w theorems makes the job easy.


Statement - In any multisource linear bilateral n/w voltage across or current through any given element is algebraic sum of individual voltage or current considering one source at a time and replacing all remaining sources (only independent) by their internal resistances if any.

Examples.

1.

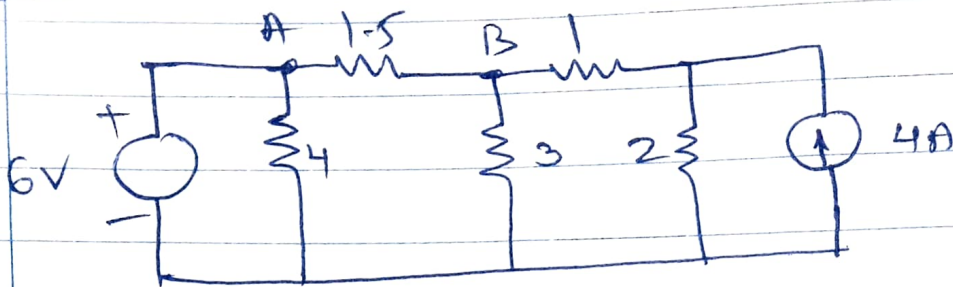

Only 6V acting

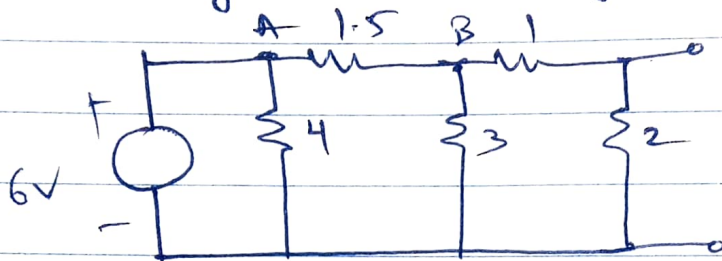


$$3 \parallel 3 = 1.5$$

$$1.5 + 1.5 = 3$$

$$3 \parallel 4 = \frac{12}{7} = 1.714$$

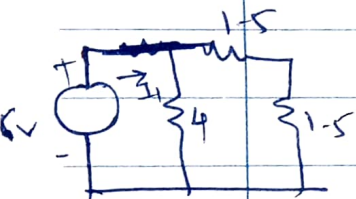
$$\therefore I_1 = 6 / 1.714 = 3.5 \text{ A}$$



$$I_1' = 3.5 \times \frac{4}{4 + 1.5 + 1.5}$$

$$= 2 \text{ A} \rightarrow$$

Only 4A acting

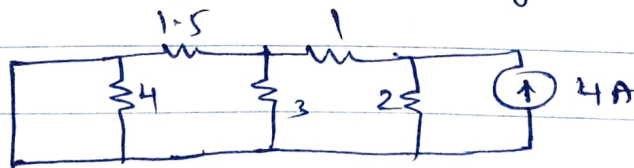

4A becomes redundant

$$1.5 \parallel 3 = 1$$

$$I_2 = 4 \text{ A}$$


$$I_2' = 4 \times \frac{2}{2 + 1 + 1}$$

$$= 2 \text{ A}$$


$$I_2'' = 2 \times \frac{3}{3 + 1.5} = 1.33 \text{ A} \leftarrow$$

$$\begin{aligned}\therefore I_{AB} &= I_1' - I_2'' \\ &= 2 - 1.33 = 0.667 \text{ A} \rightarrow\end{aligned}$$

2. Find V_{AB} using superposition.

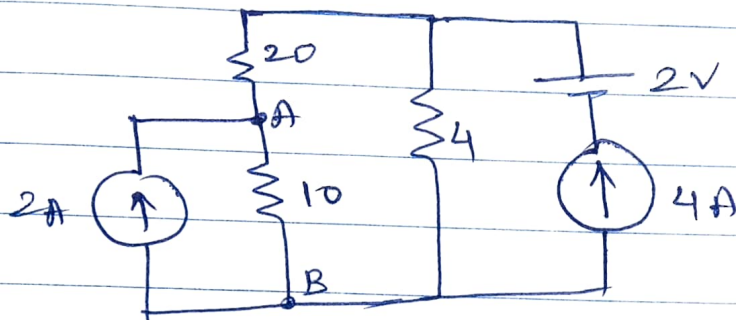

I Only 2A acting

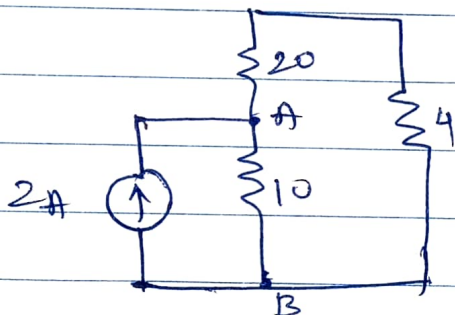


$$\begin{aligned}I_{AB}' &= 2 \times \frac{20}{20+10} \\ &= 1.41 \text{ A} \downarrow\end{aligned}$$

II Only 2V acting;
2A & 4A open ckt

$$\therefore I_{AB}'' = 0$$


III Only 4A acting

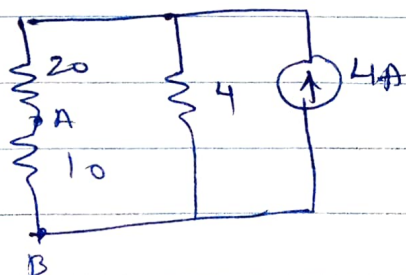

$$\begin{aligned}I_{AB}'' &= 4 \times \frac{4}{4+20+10} \\ &= 0.47 \text{ A} \downarrow\end{aligned}$$

$$\begin{aligned}\therefore I_{AB} &= 1.41 + 0 + 0.47 \\ &= 1.88\end{aligned}$$
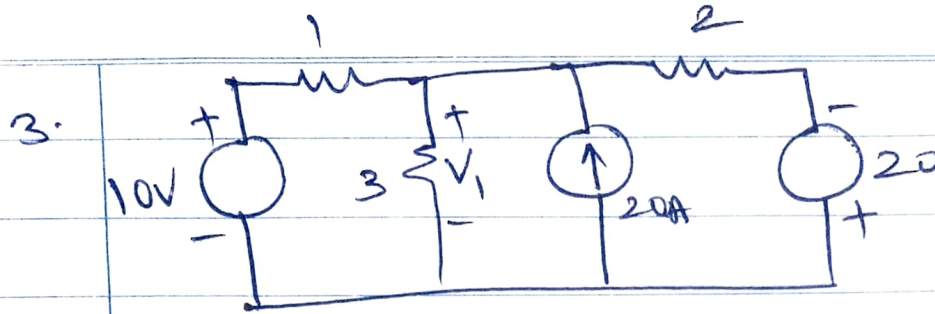
$$\therefore V_{AB} = I_{AB} \times 10 = 18.8 \text{ V.}$$




$$I_1' = 1.81 \text{ A} \downarrow$$

$$I_2' = 3.63 \text{ A} \downarrow$$

$$I_3' = 1.81 \text{ A} \uparrow$$

$$\therefore V_1 = 10.9 \text{ V} \quad \text{Ans.}$$


With dependent sources.

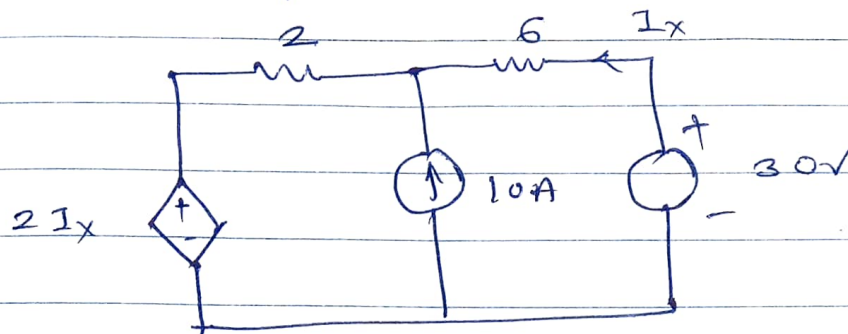

Find I_x

Dependent sources to be kept as it is


Only 10A acting

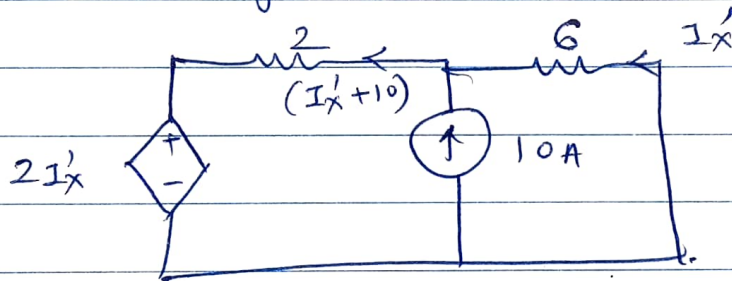

$$= 6I'_x - 2(I'_x + 10) - 2I'_x = 0$$

$$\therefore I'_x = -2$$


Only 30V acting

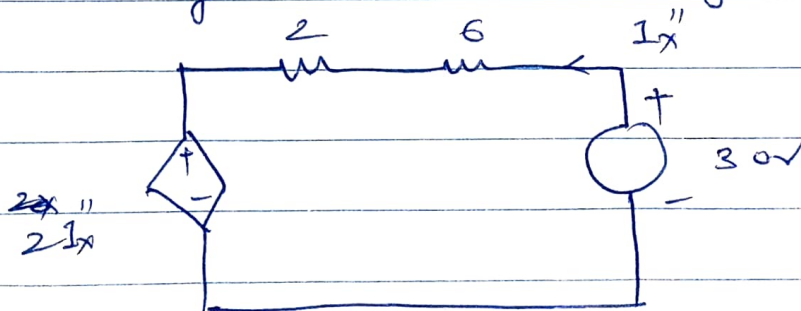

$$-6I''_x - 2I''_x - 2I''_x + 30 = 0$$


$$\therefore I''_x = \cancel{20} 3A$$
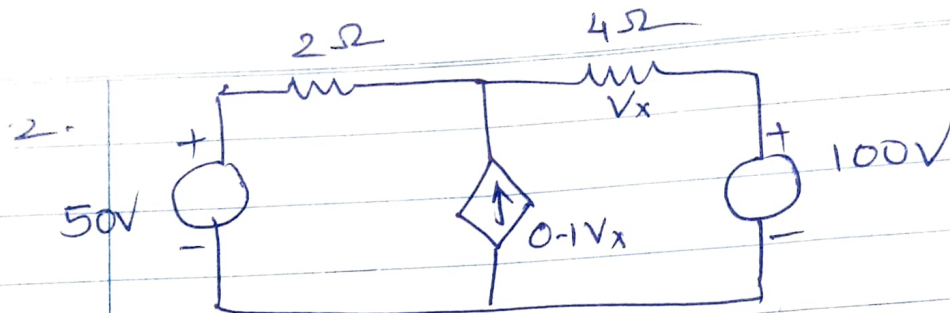
$$\therefore I_x = I'_x + I''_x = -2 + 3 = 1A$$



Use superposition th^m to evaluate V_x .

I. 50V alone

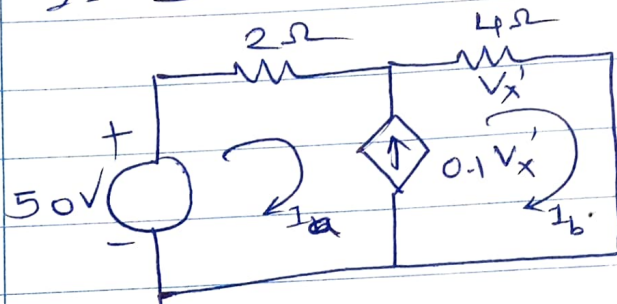

$$I_b - I_a = 0.1V_x' \quad \text{--- (1)}$$

Applying KVL to outer loop.

$$-2I_a - 4I_b + 50 = 0$$

$$I_a + 2I_b = 25 \quad \text{--- (2)}$$

$$\text{and } V_x' = -4I_b \quad \text{--- from KVL} \quad \text{--- (3)}$$

$$\therefore I_b - I_a = 0.1V_x'$$

$$= 0.1(-4I_b)$$


$$-I_a + 1.4I_b = 0 \quad \text{--- (4)}$$

Add 2 & 4

$$I_b = 7.3529 \text{ A}$$

$$\therefore V_x' = -4I_b = -29.4117 \text{ V} \quad \text{--- due to 50V only}$$

II 100V alone

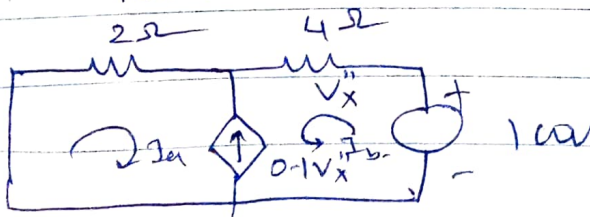

$$I_a + I_b = -0.1 V_x'' \quad \text{--- (5)}$$

Apply KVL to outer loop.

$$-2I_a + 4I_b - 10 = 0$$

$$-I_a + 2I_b = 5 \quad \text{--- (6)}$$

$$\text{also } V_x'' = 4I_b \quad \text{--- (7)}$$

$$\therefore I_a + I_b = -0.1 (4I_b)$$

$$I_a + 1.4I_b = 0 \quad \text{--- (8)}$$

Add (6) & (8);

$$I_b = 14.7058 \text{ A}$$

$$V_x'' = 4I_b$$

$$= 58.8235 \text{ V}$$

$$\therefore V_x = V_x' + V_x''$$



$$= -29.4117 + 58.8235$$

$$= 29.4117 \text{ V}$$

Thevenin's Theorem


Steps.

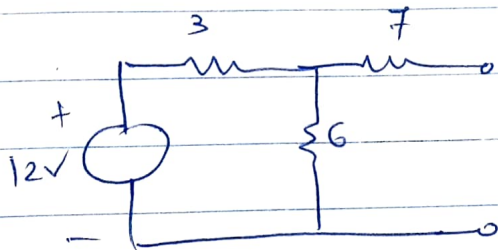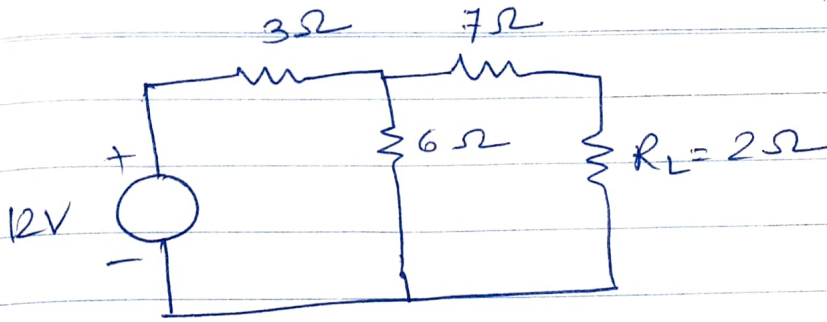1. Remove load resistance and calculate voltage at open circuited terminals. This vltg. is V_{th} .
2. Remove sources also. Replace vltg. source by S.C. & current source by open circuit. Now calculate Equivalent resistance ^(R_{eq}) of the circuit as if you are looking into the ckt. from open circuited terminals.
3. Draw ~~E~~ Thevenin's equi. ckt.
4. Connect R_L to equi. ckt.
5. Calculate load current by using,
$$I_L = \frac{V_{th}}{R_{eq} + R_L}$$




$$I = \frac{12}{9} = 1.33 \text{ A}$$


$$\therefore V_{th} = 6 \times 1.33$$

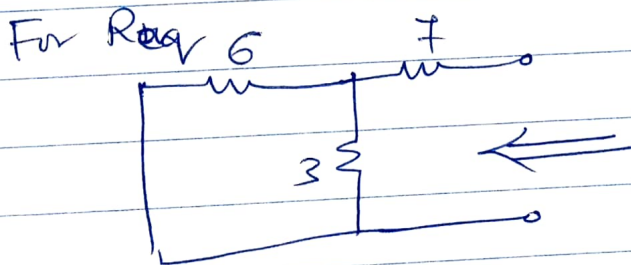

$$(6 \parallel 3) + 7$$

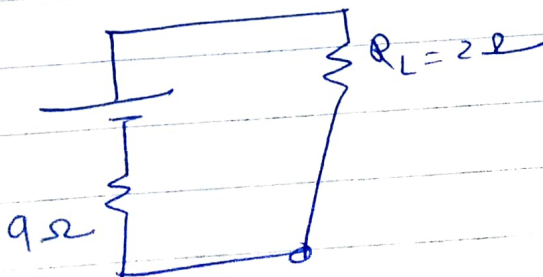
$$R_{eq.} = \frac{18}{9} + 7 = 2 + 7 = 9\Omega$$



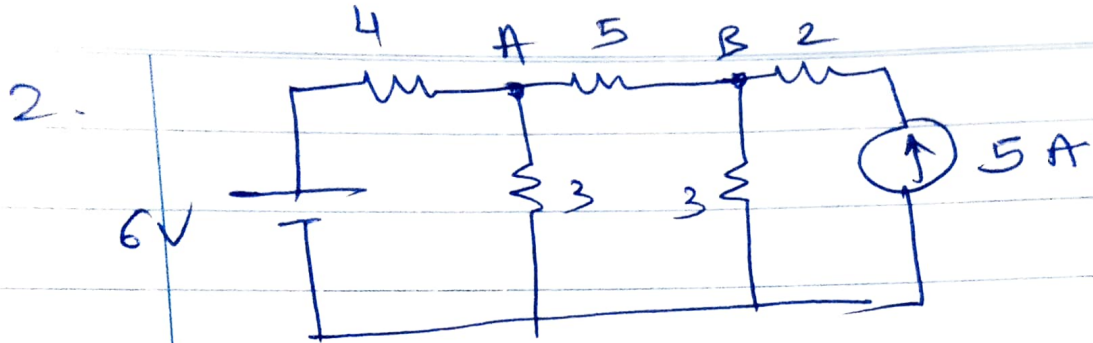

$$I_{AB} = ?$$

Maximum Power Transfer Theorem

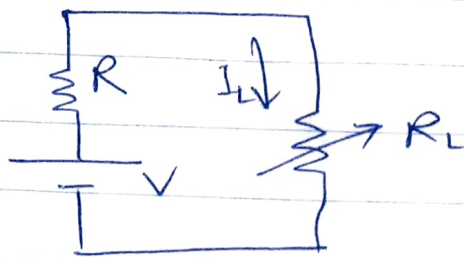

Consider a ckt. with DC vltg source V and resistance R Ω connected to variable load resistance R_L .

Load current ~~can~~ can be calculated here as,

$$I_L = \frac{V}{R + R_L}$$

The power consumed by the load resistance R_L is,

$$\begin{aligned} P &= I_L^2 R_L \\ &= \left(\frac{V}{R + R_L} \right)^2 R_L \end{aligned}$$

If R_L is changed, I_L will also change and at a particular value of R_L , the power transferred to the load will be max. Hence the power depends on the value of R_L . To get the ~~max~~ value of R_L at which power will be max., let's differentiate above eqn of power w.r.t. R_L & equate to zero.

$$\therefore \frac{dP}{dR_L} = 0$$

$$\therefore \frac{d}{dR_L} \left[\frac{V}{R+R_L} \right]^2 \cdot R_L = 0$$

$$V^2 \cdot \frac{d}{dR_L} \left[\frac{R_L}{(R+R_L)^2} \right] = 0$$


after solving this, we get,

$$R + R_L - 2R_L = 0$$

$$\therefore \boxed{R_L = R}$$

Thus when load resistance is equal to ~~internal~~ resis. of the ckt; max. power transfer takes place.

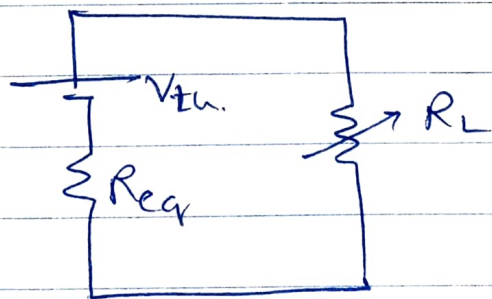we represent the complex n/w with Thevenin's equi. ckt



If we compare ~~to~~ this ckt with above drawn ckt, we get;

2021

$$R_L = R_{eq}$$

for max. power transfer.

And max. power will be calculated as,


$$P_m = \left[\frac{V_{th}}{R_{eq} + R_L} \right]^2 \cdot R_L$$

With $R_L = R_{th}$;

$$P_m = \left[\frac{V_{th}}{2 R_{eq}} \right]^2 \cdot R_{eq}$$

$$P_m = \frac{V_{th}^2}{4 R_{eq}} \text{ watts.}$$

Examples.

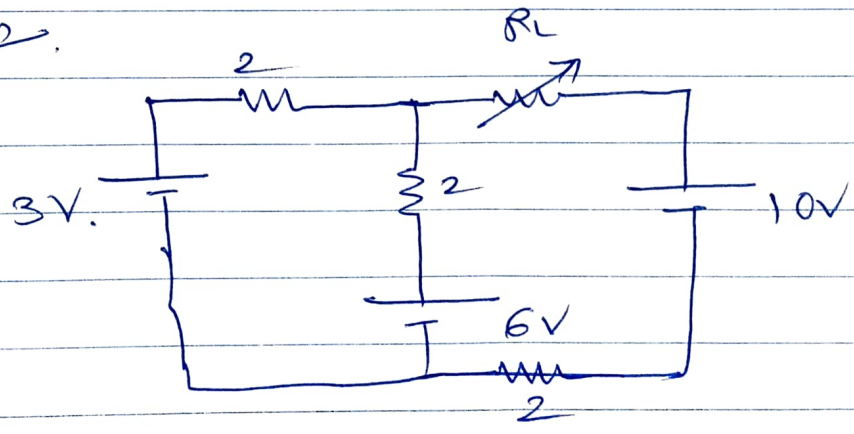

$$V_{th} = 5.5V$$

$$R_{eq} = 3\Omega$$

$$P_m = 2.5208W.$$