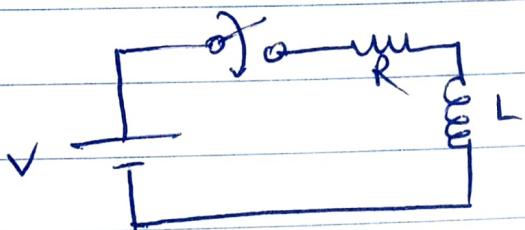


## R-L circuit


Consider a series R-L circuit as shown,



The switch is closed at  $t=0$ .

The inductor in ckt is initially unenergized

Ckt at  $t>0$  will be,

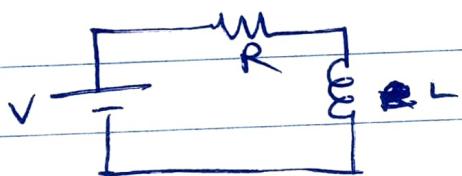

KVL eqn at  $t>0$  will be,

$$V - Ri - L \frac{di}{dt} = 0$$

This is a linear differential eq<sup>n</sup> of first order.

It can be solved if variables can be separated.

$$(V - Ri) dt = L di$$

$$\frac{L di}{V - Ri} = dt$$

Integrating both sides,

$$-\frac{L}{R} \ln(V - Ri) = t + K \quad \text{--- (1)}$$

Where  $\ln$  is log at base e & k is arbitrary constant. Value of k can be evaluated from the initial condition.

In the given ckt. the switch is closed at  $t=0$  ie, before closing the switch, the current in the inductor is zero.

Since the inductor doesn't allow sudden change in current, at  $t=0^+$  the current remains zero.

Setting  $i=0$  at  $t=0$ ,

$$-\frac{L}{R} \ln V = k \quad \text{--- (2)}$$

Putting value of k from eqn(2) in (1),

$$-\frac{L}{R} \ln(V - Ri) = t - \frac{1}{R} \ln V$$

$$-\frac{L}{R} [\ln(V - Ri) - \ln V] = t$$

$$\frac{V - Ri}{V} = e^{-\frac{RL}{R}t}$$

$$V - Ri = V \cdot e^{-\frac{RL}{R}t}$$

$$Ri = V - V \cdot e^{-\frac{RL}{R}t}$$

$$i = \frac{V}{R} - \frac{V}{R} e^{-\frac{RL}{R}t} \quad \text{for } t > 0$$

This response is composed of two parts, the steady state response  $\frac{V}{R}$  and transient response  $\frac{V}{R} e^{-\frac{RL}{R}t}$ .

Or natural response

This transient response is a characteristic of the circuit.



Here the transient period is defined as the time taken for the current to reach its final or steady state value from its initial value.

The term  $L/R$  is called time constant & is denoted by  $T$ :

$$T = L/R$$

- At one time constant, the current reaches 63.2% of its final value  $V/R$ .

- Voltage across the resistor is,


$$V_R = R_i = R \times \frac{V}{R} (1 - e^{-R/Lt})$$

$$= V(1 - e^{-R/Lt}) \text{ for } t \geq 0$$


Similarly, voltage across inductor is,

$$V_L = L \frac{di}{dt} = L \cdot \frac{V}{R} \frac{d}{dt} (1 - e^{-R/Lt})$$
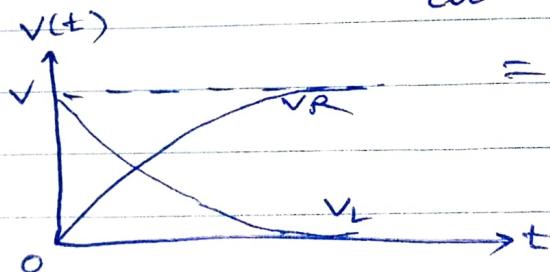
$$= V \cdot e^{-R/Lt} \text{ for } t \geq 0$$



## Resistor-Capacitor Circuit

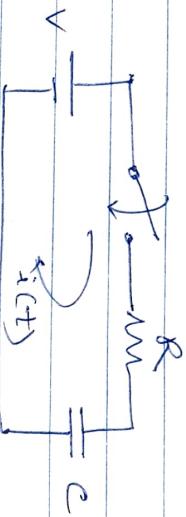

Consider a series  $RC$  circuit.

The switch is closed at  $t = 0$ .

The capacitor is initially uncharged.

Applying KVL to the circuit for  $t > 0$ ,



$$V - Ri - \frac{1}{c} \int i dt = 0$$

Differentiating above eqn,

$$0 - R \frac{di}{dt} - \frac{i}{c} = 0$$

$$\therefore \frac{di}{dt} + \frac{1}{RC} i = 0$$

This is a linear differential eqn of first order. The variables may be separated to solve the eqn.

$$\frac{di}{i} = -\frac{dt}{RC}$$

Integrating both the sides,

$$\ln i = -\frac{1}{RC} t + k$$

The constant  $k$  can be evaluated from initial condition. In the Ckt, the switch is closed at  $t=0$ . Since the capacitor never allows sudden change in voltage, it will act as s.c. at  $t=0^+$ . Hence, current in the circuit at  $t=0^+$  is  $\frac{V}{R}$ .

Setting  $i = \frac{V}{R}$  at  $t=0$

$$\ln\left(\frac{V}{R}\right) = k$$

$$\ln i = -\frac{1}{RC} t + \ln\frac{V}{R}$$


$$\ln i - \ln\frac{V}{R} = -\frac{1}{RC} t$$

$$\ln\left(\frac{i}{(V/R)}\right) = -\frac{1}{RC} t$$

$$\therefore \frac{i}{V/R} = e^{-\frac{1}{RC} t}$$

$$\therefore i = \frac{V}{R} \cdot e^{-\frac{1}{RC} t} \text{ for } t > 0$$

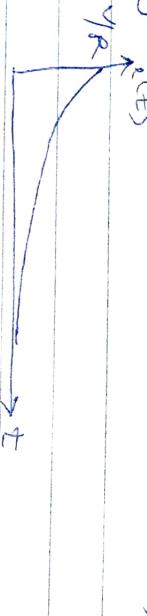When the switch is closed, the response decays with time as shown



The term  $RC$  is called Time constant

& is denoted by  $T$

$$\therefore T = RC$$


Voltage across the resistor is,

$$VR = R_i \\ = R \cdot \frac{V}{R} e^{-\frac{R}{RC} t}$$


$$= V \cdot e^{-\frac{1}{RC} t} \quad \text{for } t > 0$$

Similarly voltage across capacitor is,

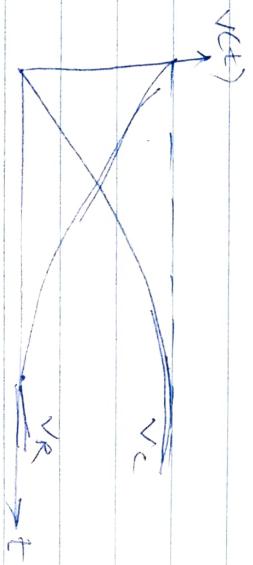
$$VC = \frac{1}{C} \int_0^t i \, dt \\ = \frac{1}{C} \int_0^t \frac{V}{R} e^{-\frac{R}{RC} t} \, dt \\ = -V e^{-\frac{1}{RC} t} + k$$



## R-L-C circuit.

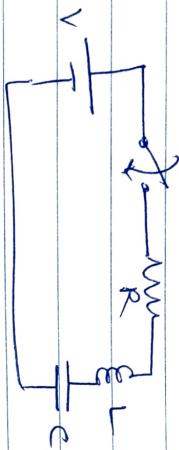

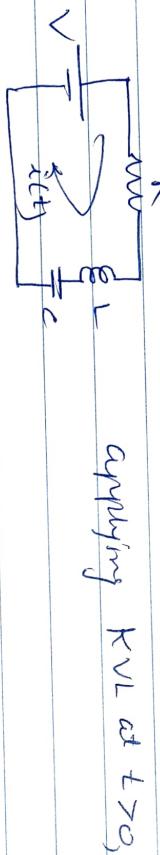- Consider a RLC series ckt. shown above.
- Switch is closed at  $t = 0$
- Capacitor & inductor are initially unchanged.
- at  $t > 0$ , the ckt. will be,



$$V - Ri - L \frac{di}{dt} - \frac{1}{C} \int_0^t i dt = 0$$

Differentiating above eqn,

$$0 - R \frac{di}{dt} - L \frac{d^2i}{dt^2} - \frac{1}{C} i = 0$$

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

This is a second order differential

eqn. The auxiliary or characteristic eqn will be given by,

$$s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$$

Let  $s_1$  &  $s_2$  be the roots of the eqn

$$s_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$= -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$= -\alpha + \beta$$

and

$$s_2 = -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$= -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$= -\alpha - \beta$$

$$\text{where } \alpha = \frac{R}{2L}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\beta = \sqrt{\alpha^2 - \omega_0^2}$$

The solution of above second order differential eqn will be given by

$$i(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t}$$


where  $k_1$  and  $k_2$  are constants to be determined and  $s_1$  and  $s_2$  are the roots of the eqn.

Now depending upon values of  $\alpha$  &  $\omega_0$ ,  
there are 3 cases of response.

I]  $\alpha > \omega_0$  ie,

$$\frac{R}{2L} > \frac{1}{\sqrt{LC}}$$

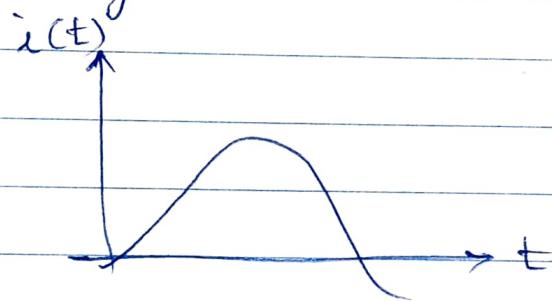The roots are real & unequal and it gives an overdamped response.



In this case soln is given by


$$i = e^{-\alpha t} (k_1 e^{\beta t} + k_2 e^{-\beta t})$$

$$\text{or } i = k_1 e^{st} + k_2 e^{-st} \text{ for } t > 0.$$

II]  $\alpha = \omega_0$  ie,  $\frac{R}{2L} = \frac{1}{\sqrt{LC}}$

Roots are real & equal & it gives critically damped response.

$i(t)$

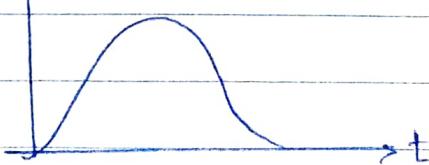

In this case the solution is given by,

~~$i = e^{-\alpha t} (k_1 + k_2 t) \text{ for } t > 0$~~ 


$$i = e^{-\alpha t} (k_1 + k_2 t) \text{ for } t > 0$$

III]  $\alpha < \omega_0$  ie  $\frac{R}{2L} < \frac{1}{\sqrt{LC}}$

The roots are complex conjugate and it gives an underdamped response.


In this case the solution is given by

$$i(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t}$$

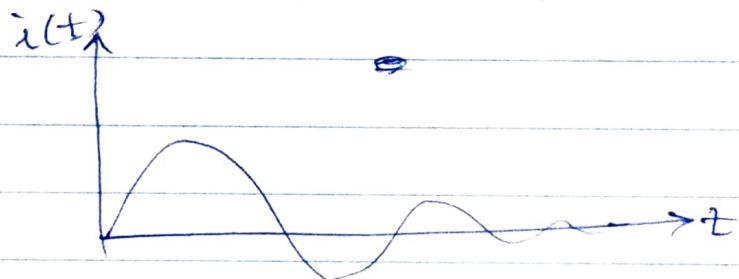

Example:

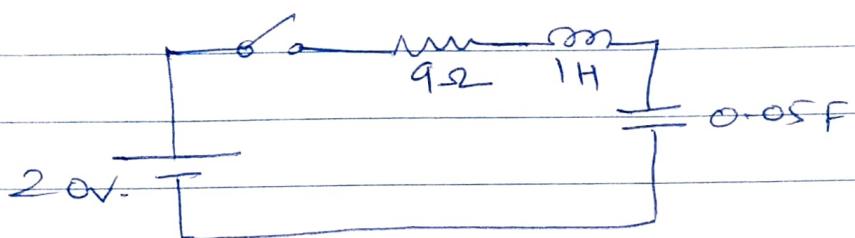1. In the network shown below, the switch is closed at  $t=0$ . Obtain expression for current  $i(t)$  at  $t > 0$



Sol<sup>n</sup>: At  $t = 0^-$  the switch is open

$$\therefore i(0^-) = 0$$


$$v_c(0^-) = 0$$

As the current through inductor & voltage across capacitor cannot change instantaneously,

$$i(0^+) = 0$$

$$v_c(0^+) = 0$$

At  $t \geq 0$ , the circuit is,

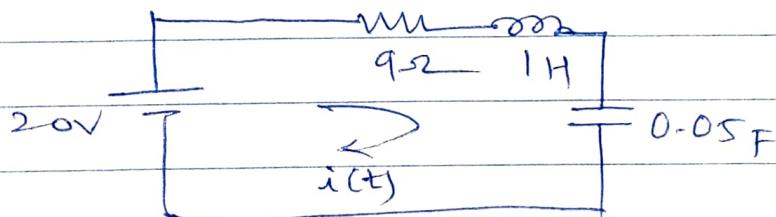

Applying KVL,

$$20 - 9i - i \frac{di}{dt} - \frac{1}{0.05} \int_0^t i dt = 0 \quad \text{--- (1)}$$

Differentiating above eqn,

$$0 - 9 \frac{di}{dt} - \frac{d^2i}{dt^2} - 20i = 0$$

$$\therefore \frac{d^2i}{dt^2} + 9 \frac{di}{dt} + 20i = 0$$

$$D^2 + 9D + 20 = 0$$

$$\therefore D_1 = -4, D_2 = -5$$

The solution for diff. eqn is given by

$$i(t) = k_1 e^{-4t} + k_2 e^{-5t} \quad \text{--- (2)}$$

Differentiating eqn (2),

$$\frac{di}{dt} = -4k_1 e^{-4t} - 5k_2 e^{-5t} \quad \text{--- (3)}$$

$$\text{At } t=0, i(0)=0.$$

$$\therefore 0 = k_1 + k_2 \quad \text{--- (4) From eqn (2)}$$

$$\frac{di}{dt}(0) = -4k_1 - 5k_2 \quad \text{--- (5) From eqn (3)}$$

Putting  $t=0$  in eqn (1),

$$20 - 9i(0^+) - \frac{di}{dt}(0^+) - 0 = 0$$

$$\begin{aligned} \frac{di}{dt}(0^+) &= 20 - 9i(0^+) \\ &= 20 \text{ A.s.} \end{aligned}$$

putting this value in eqn (5),

$$20 = -4k_1 - 5k_2 \quad \text{--- (6)}$$

Solving eqns (4) & (6)

$$k_1 = 20, k_2 = -20$$

$$\therefore \boxed{i(t) = 20e^{-4t} - 20e^{-5t}} \quad \text{for } t > 0.$$

2. A RC circuit has  $R = 20\Omega$  &  $C = 40\mu F$ .  
 What is time constant?

$$T = RC$$

$$= 20 \times 40 \times 10^{-6} = 8ms$$

3. ~~A capacitor in RX circuit with  $R = 25\Omega$  &  $C = 50\mu F$  is being charged with initial zero voltage. What is time taken for the capacitor voltage to reach 70% of its steady state value?~~

~~$R = 25\Omega$~~

~~$C = 50\mu F$~~

~~$\therefore T = RC = 1.25 \times 10^3 s$~~

~~$\therefore \frac{1}{RC} = 800 s^{-1}$~~

4. In a RL ckt with time const of 1.25 sec, inductor current increases from the initial value of zero to the final value of ~~1.2 A~~ 1.2 A  
 a) Calculate inductor current at time 0.4 s, 0.8 s & 2 sec.

b) Find the time at which the inductor current reaches 0.3 A, 0.6 A & 0.9 A

$$L/R = 1.25$$

$$\therefore R/L = 0.8$$

~~$i_L(0) = 0$~~

$$i_L(\infty) = 1.2 A$$

$$i_L = \frac{V}{R} (1 - e^{-\frac{R}{L}t}) \quad A$$

$$= 1.2 (1 - e^{-0.8t}) \quad A$$

a]

$$\text{at } t = 0.4 \text{ s}, i_L = 1.2 (1 - e^{-0.32}) = 0.3286 \text{ A}$$

$$t = 0.8 \text{ sec}, i_L = 0.5672 \text{ A}$$

$$t = 2 \text{ sec} \quad i_L = 0.9577 \text{ A}$$

b]

$$0.3 = 1.2 (1 - e^{-0.8t_1})$$

$$\therefore t_1 = 0.3596 \text{ sec}$$

$$0.5 = 1.2 (1 - e^{-0.8t_2})$$

$$\therefore t_2 = 0.8664 \text{ sec}$$

$$0.9$$

$$t_3 = 1.7329 \text{ sec.}$$

4.

Find expression for the current in a series RLC ckt. fed by dc voltage of 20V with


$R = 4 \Omega$ ,  $L = 1H$  &  $C = \frac{1}{4} F$ . Assume initial condn to be zero

Sol<sup>n</sup>

Assuming zero initial condn,

$$i_L(0^-) = 0 = i_L(0^+) \quad \text{--- (1)}$$
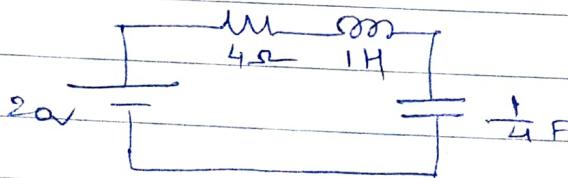
$$V_C(0^-) = 0 = V_C(0^+) \quad \text{--- (2)}$$



KVL eqn

$$20 - 4i - \frac{1}{\frac{1}{4}} \int i dt - 1 \frac{di}{dt}$$

$$4i + 4 \int i dt - \frac{di}{dt} = 20 \quad \text{--- (3)}$$

Differentiating,

$$4 \frac{di}{dt} + \frac{d^2i}{dt^2} + 4i = 0$$

$$\therefore \frac{d^2i}{dt^2} + 4 \frac{di}{dt} + 4i = 0 \quad \text{--- (4)}$$

$$s^2 + 4s + 4 = 0$$

Roots of the eqn are,

$$s_1 = s_2 = -2$$

$\therefore$  Roots are real & equal

Hence sol<sup>n</sup> i,

$$i(t) = k_1 \cdot e^{-2t} + k_2 t \cdot e^{-2t} \quad \text{--- (5)}$$

$$\text{at } t=0, i(0) = 0$$

Putting values,

$$0 = k_1 \cdot e^0 + k_2(0) \cdot e^0$$

$$\therefore k_1 = 0 \quad \text{--- (6)}$$

$$\therefore i(t) = k_2 \cdot t \cdot e^{-2t} \quad \text{--- (7)}$$

Now putting  $t=0$  in eqn (3),

$$4i(0) + \frac{di}{dt}(0) + 4f(0) = 20$$

$$\therefore \frac{di}{dt} = 20 \quad \text{Ans.} \quad \text{--- (8)}$$

Differentiate eqn ⑧ w.r.t. t,

$$\frac{di}{dt} = k_2 \left[ t(-2)e^{-2t} + e^{-2t}(1) \right]$$

$$\therefore \frac{di}{dt} = k_2 (-2t e^{-2t}) + k_2 (e^{-2t}) \quad \text{--- ⑩}$$

At  $t=0$ , eqn ⑩ becomes,

$$\begin{aligned} \frac{di}{dt}(0) &= 20 = k_2 (-2(0)e^{-0}) + k_2 (e^{-0}) \\ &= k_2 (-2(0)e^0) + k_2 \cdot e^0 \end{aligned}$$

$$\therefore k_2 = 20$$

$\therefore$  Expression for current,

$$i(t) = k_2 \cdot t \cdot e^{-2t}$$

$$i(t) = 20t e^{-2t}$$