

F. Y. B. Tech Academic Year 2021-22
ECE101B: Basics of Electrical and Electronics Engineering

Trimester: III

Assignment 2

Date: 18/02/2022

Max. Marks: 25

Submission Date: 25/02/2022

Course Outcomes (COs) Covered:


1. Predict the behavior and characteristics of basic electrical and magnetic circuits. (CLII)
2. Identify components/equipment required for any particular application related to electrical and electronics engineering. (CL-II)

Instructions:

1. Q I is a set of 10 MCQs. Each MCQ carries one mark.
2. Q II, Q III, Q IV each carry 5 marks.
3. Please note that for Q II, Q III, Q IV, the component values are to be selected based on your division and roll number as mentioned in the question.


Q I. Select the answer of the following MCQs-

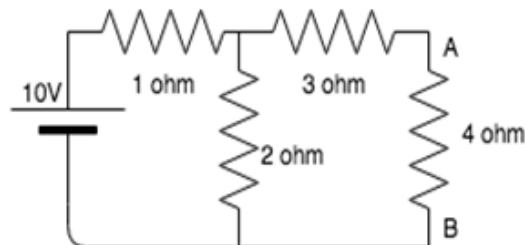1) Calculate the Thevenin resistance across the terminal AB for the following circuit.




- A. 4.34 ohm
- B. 3.67 ohm
- C. 3.43 ohm
- D. 2.32 ohm

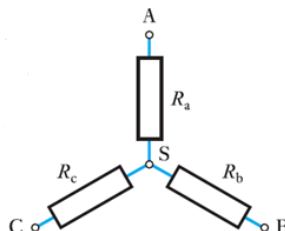2) R_a is resistance at A, R_b is resistance at B, R_c is resistance at C in star connection. After transforming to delta, what is resistance between B and C?



- A. $R_c + R_b + R_c \cdot R_b / R_a$
- B. $R_c + R_b + R_a \cdot R_b / R_c$
- C. $R_a + R_b + R_a \cdot R_c / R_b$
- D. $R_c + R_b + R_c \cdot R_a / R_b$

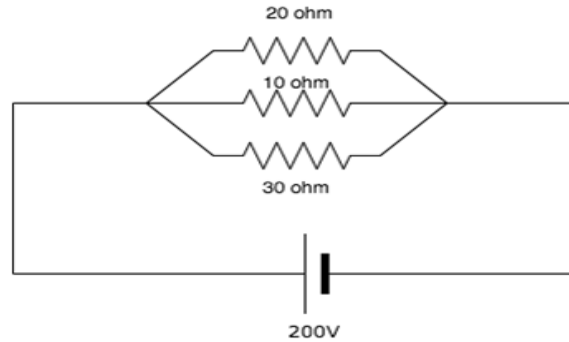3) Calculate the current through 20 ohm resistor.



- A. 10A
- B. 20A
- C. 6.67A
- D. 36.67A

4) KCL is associated with _____

- A. Mesh analysis
- B. Nodal analysis
- C. Both mesh and nodal
- D. Neither mesh nor nodal

5) In superposition theorem, when we consider the effect of one current source, all the other current sources are _____

- A. Shorted
- B. Opened
- C. Removed
- D. Undisturbed

6) A capacitor of 63 micro-F is connected across the voltage source of 230 V, 50 Hz. Current flowing through capacitor is

- A. 4.59 A
- B. 4.55 A
- C. 4.69 A
- D. 4.66 A

7) A voltage source of 230 V, 50 Hz is applied across ideal inductor of 0.11 mH. In this circuit,

- A. Current lags the voltage by 90°
- B. Current leads the voltage by 90°
- C. Voltage leads the current by 45°
- D. Voltage and current are in Phase.

8) A series electric circuit contains resistance of 75 Ohm, capacitor of 5micro-F and inductor of 0.1 mH. At resonance impedance of the circuit is

- A. $75 - j X_C + j X_L$
- B. 75 ohm
- C. $75 + j (X_C - X_L)$
- D. None

9) An alternating voltage has equation , what is value of frequency and RMS voltage

- A. 75Hz, 100v
- B. 70Hz, 110v
- C. 60Hz, 100v
- D. 55Hz, 120v

10) The power factor at resonance in R-L-C parallel circuit is

- A. Zero
- B. 0.08 lagging
- C. 0.8 leading
- D. Unity

Q. II


Assume V_1 = students division number, R_2 = addition of last three digits of student's roll number (R_2 is in Ω), $R_1 = 5\Omega$, $R_3 = 3\Omega$ and $I_1 = 8A$. Using Superposition theorem, find current flowing through R_2 . Comment on result. Refer the circuit shown below.

(For ex. If your Div is XIV then $V_1 = 14 V$ and if Roll No is 114016 then $R_2 = 1+6 = 7 \Omega$)

Q.III

A circuit having following components in series a resistance R = last three digits of Roll No (Ω), an inductance L = your division number (mH) and a capacitance $C = 150 \mu F$, is connected across a 150 V, 50 Hz supply.

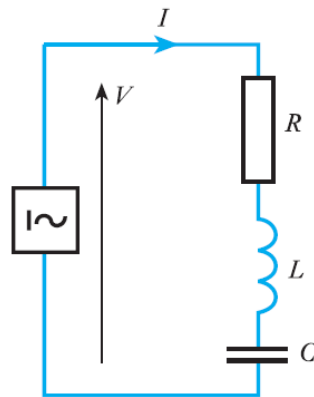(For ex. If your Div is XIV then $L = 14 mH$ and if Roll No is 114016 then $R = 16 \Omega$)



Calculate:

- (a) the impedance
- (b) the current
- (c) the voltages across R, L and C

Q IV

Convert the following star network into its equivalent Delta network by taking the values of R_1 , R_2 & R_3 as follows.

$R_1 = 25\Omega$ (fixed)

R_2 = last three digits of your roll no

R_3 = Your division no.

(For ex. If your Div is XI then $R_3 = 11\Omega$ and if Roll No is 111050 then $R_2 = 050\Omega$)

