

**NAME: SHREERANG MHATRE**  
**ROLLNO: 52**  
**BATCH: A3**

## **IGBT CHARACTERISTICS**

**AIM:** To study the characteristics of IGBT.

**APPARATUS:** 1) Circuit board with IGBT SGH80N60.  
2) 3½ & 4½ digit DMMs, ammeters & voltmeters.  
3) Dual-trace CRO with probes.  
4) 30V power supplies

### **THEORY:**

characteristics of an IGBT are shown in Fig. 3.

### **CIRCUIT DESCRIPTION:**

The section on the board, shown in Fig. 5, is used for obtaining the transfer & output characteristics of the IGBT.

### **PROCEDURE:**

#### **1. Transfer characteristics of IGBT**

- 1.1 Connect a DC ammeter, A3, in 10mA, between X23(+ve) & X24(-ve), in the drain circuit.
- 1.2 Connect a 4½ digit DMM, V1, in 20V range, between X26(+ve) & X27(-ve), in the gate circuit.
- 1.3 Connect a 3½ digit DMM, V2, in 2V range, between X24(+ve) & X22(-ve), in the drain circuit.
- 1.4 Use a table fan to ensure proper cooling of the IGBT mounted on heatsink.
- 1.5 Set potentiometer R11 in the gate circuit to minimum position (maximum anticlockwise).
- 1.6 Connect a DC supply in the gate circuit,  $V_{GG}$ , between X25(+ve) & X22 (-ve). Set supply to 2V.
- 1.7 Connect a DC supply in the drain circuit,  $V_{DD}$ , between X21(+ve) & X22 (-ve). Set supply to 15V.
- 1.8 Slowly increase the gate voltage,  $v_{GS}$ , using  $V_{GG}$  & R11 till the IGBT **just** starts conducting i.e.  $i_D$  is around 50µA. Note value of  $v_{GS}$  which is now the threshold gate-source voltage  $V_{GS(Th)}$ .
- 1.9 Increase the gate voltage further and take five readings of  $i_D$  &  $v_{GS}$  upto  $i_D = 700mA$ . For every reading, ensure that  $v_{DS} = 15V$  by adjusting  $V_{DD}$ .
- 1.10 Reduce  $V_{GG}$  &  $V_{DD}$ .

## 2. Output characteristics of IGBT

2.1 Set  $V_{GS}$  to a value above  $V_{GS(Th)}$ .

2.2 Slowly increase the drain-source voltage,  $v_{DS}$ , by increasing the drain supply voltage,  $V_{DD}$ , and note the corresponding values of drain current  $i_D$ . Initially the IGBT will be in the ohmic region and then, for higher values of  $v_{DS}$ , it will enter the active region. Take three readings in the ohmic region and three readings in the active region, up to  $i_D = 700$  mA.

2.3 Increase  $V_{GS}$  and repeat step 5.2. Readings should be taken for a total three different values of  $V_{GS}$ .

2.4 Switch off all supplies and remove all connections on the chassis.

### OBSERVATIONS:

#### 1. Transfer characteristics of IGBT

1.1:  $V_{GS(Th)} =$  V

1.2:  $i_D$  vs  $v_{GS}$

Sr. No.	$i_D$ mA	$v_{GS}$ V
1.		
2.		
3.		
4.		
5.		

#### 2. Output characteristics of IGBT

2.1:  $v_{GS} =$  V

Sr. No.	Region	$i_D$ mA	$v_{DS}$ V
1.	Ohmic		
2.	Ohmic		
3.	Ohmic		
4.	Active		
5.	Active		
6.	Active		

2.2:  $v_{GS} =$  V

Sr. No.	Region	$i_D$ mA	$v_{DS}$ V
1.	Ohmic		
2.	Ohmic		
3.	Ohmic		
4.	Active		
5.	Active		
6.	Active		

2.3:  $v_{GS} =$  V

Sr. No.	Region	$i_D$ mA	$v_{DS}$ V
1.	Ohmic		
2.	Ohmic		
3.	Ohmic		
4.	Active		
5.	Active		
6.	Active		

### CHARACTERISTICS & GRAPHS:

1. Transfer characteristics of IGBT.
2. Output characteristics of IGBT.

**CALCULATIONS:** Calculate on-state resistance (reciprocal of slope in ohmic region), and output resistance (reciprocal of slope in active region) for each value of  $v_{GS}$ .

### CONCLUSIONS:

### LIST OF FIGURES:

- Fig. 1 IGBT I-V characteristics  
 Fig. 2 Circuit for characteristics of IGBT

## Fig. 3 IGBT I-V Characteristics


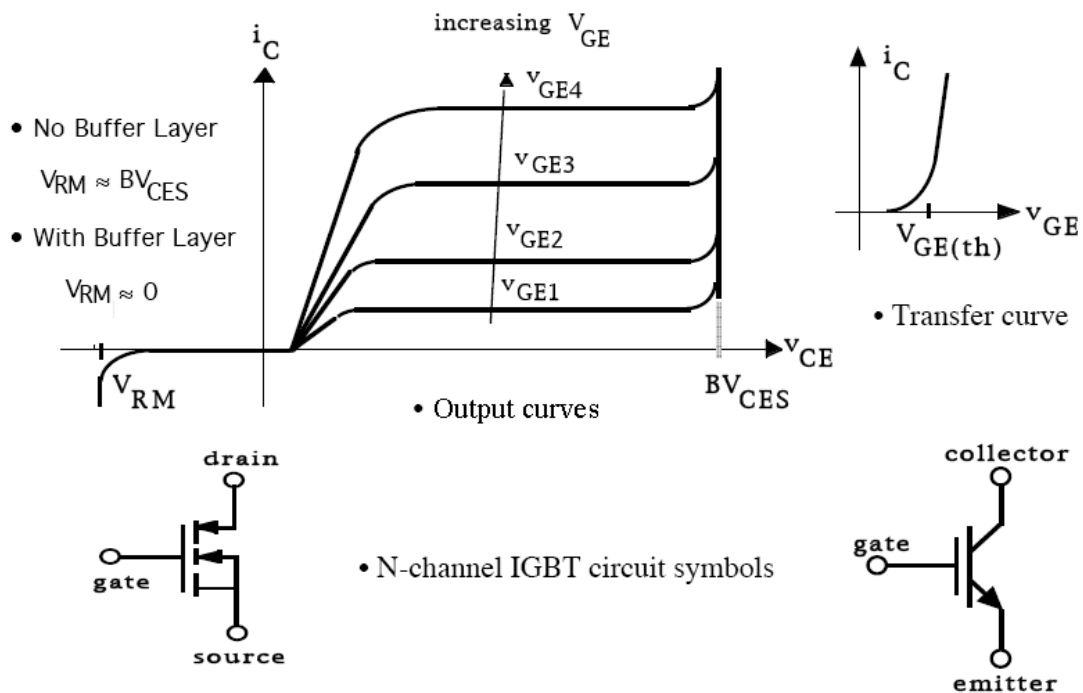


FIG1: V-I CHARACTERISTICS, LATCHING & HOLDING CURRENTS OF SCR & TRIAC

FIG2: TRANSFER \* OUTPUT CHARACTERISTIC OF IGBT

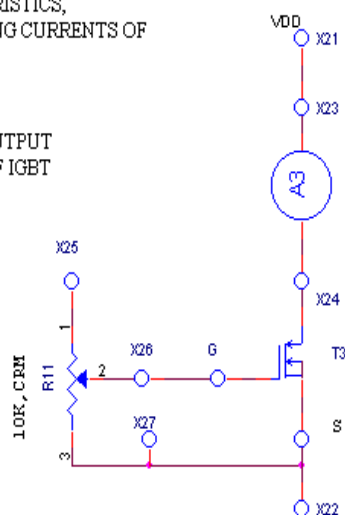

## Exp-2 IGBT



Dr. Vishwanath Karad  
**MIT WORLD PEACE  
UNIVERSITY** | PUNE  
FACULTY OF RESEARCH, SOCIAL INNOVATION & PARTNERSHIPS

Name - Shreeang Mhatre

Rollno - 52

Batch - A3

AIM - To study the characteristics of IGBT.

\* observation -

① Transfer characteristics of IGBT

Sr No	$I_p$ mA	$V_{GS}$ V
1	0.05 mA	3.56
2	0.28 mA	3.84
3	0.70 mA	4.00
4	0.140 mA	4.09
5	0.32 mA	4.51
6	0.67 mA	4.60
7	3.8 mA	4.60
8	6.0 mA	4.66
9	25 mA	4.74
10	67 mA	4.88
11	26 mA	5.10
12	62 mA	5.25

## ② Output characteristics of IGBT

i)  $V_{GS} = 4.0V$

SrNo	Region	$i_D$ mA	$V_{DS}$ V
1	ohmic	30 $\mu$ A	0.3V
2	ohmic	65 $\mu$ A	0.5V
3	ohmic	65 $\mu$ A	1V
4	Active	5 $\mu$ A	0.1V
5	Active	12 $\mu$ A	0.2V

ii)  $V_{GS} = 4.5V$

SrNo	Region	$i_D$ mA	$V_{DS}$ V
1	ohmic	2 $\mu$ A	0.1V
2	ohmic	8 $\mu$ A	0.2V
3	ohmic	31 $\mu$ A	0.3V
4	Active	55 $\mu$ A	0.4V
5	Active	110 $\mu$ A	0.5V

iii)  $V_{GS} = 5V$

SrNo	Region	$i_D$ mA	$V_{DS}$ V
1	ohmic	1mA	0.5
2	ohmic	4.4mA	0.7
3	ohmic	2.2mA	0.6
4	Active	30mA	0.8
5	Active	48mA	0.9



\* calculations -

For  $V_{GS} = 4.0V$

Onstate resistance

$$R_{ON} = \frac{(0.2 - 1)}{(12 - 65)10^{-3}} = 1.509 \text{ k}\Omega$$


For  $V_{GS} = 4.5V$

$$R_{ON} = \frac{(0.5 - 0.3)}{(110 - 31)10^{-3}} = 2.816 \Omega$$




For  $V_{GS} = 5V$
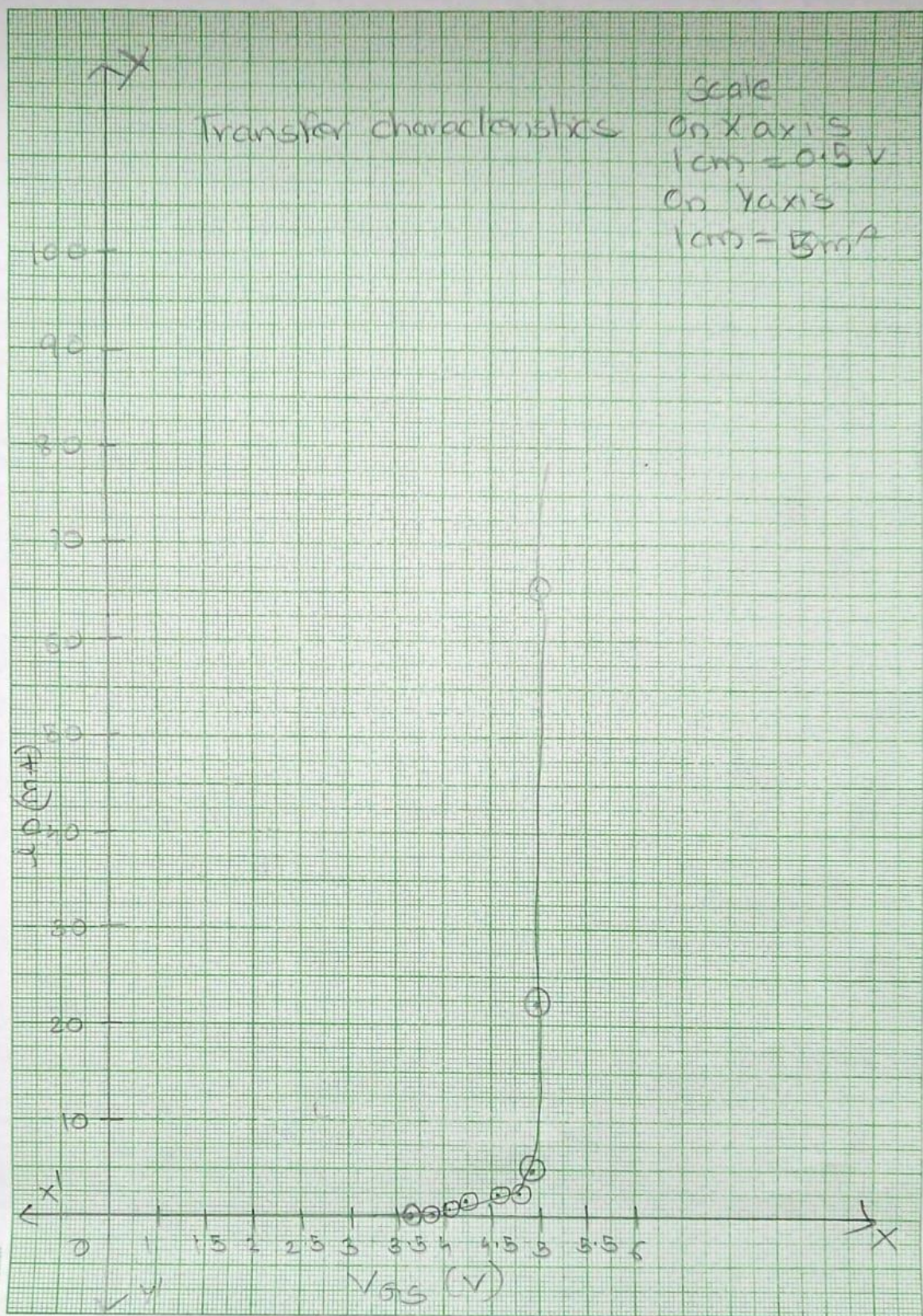
$$R_{ON} = \frac{(0.9 - 0.6)}{(48 - 2.2)10^{-3}} = 6.637 \Omega$$







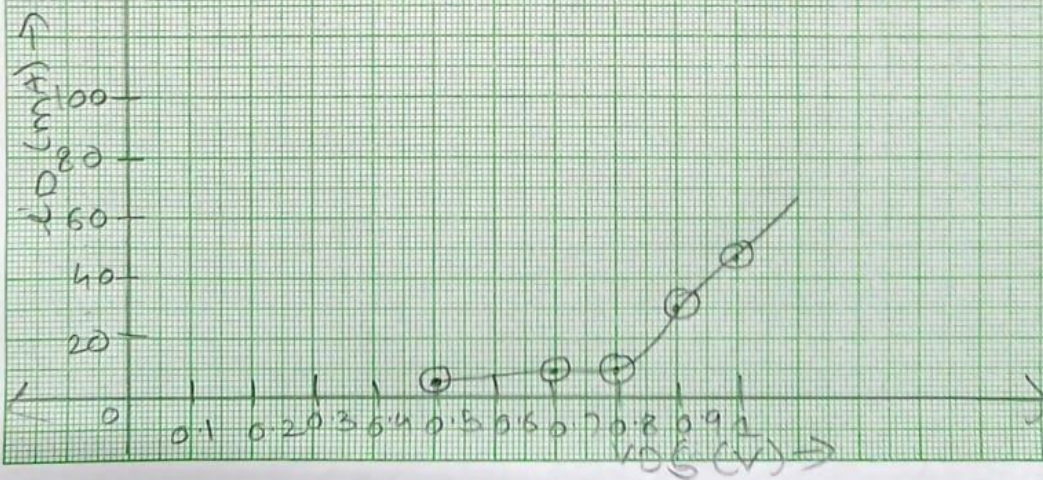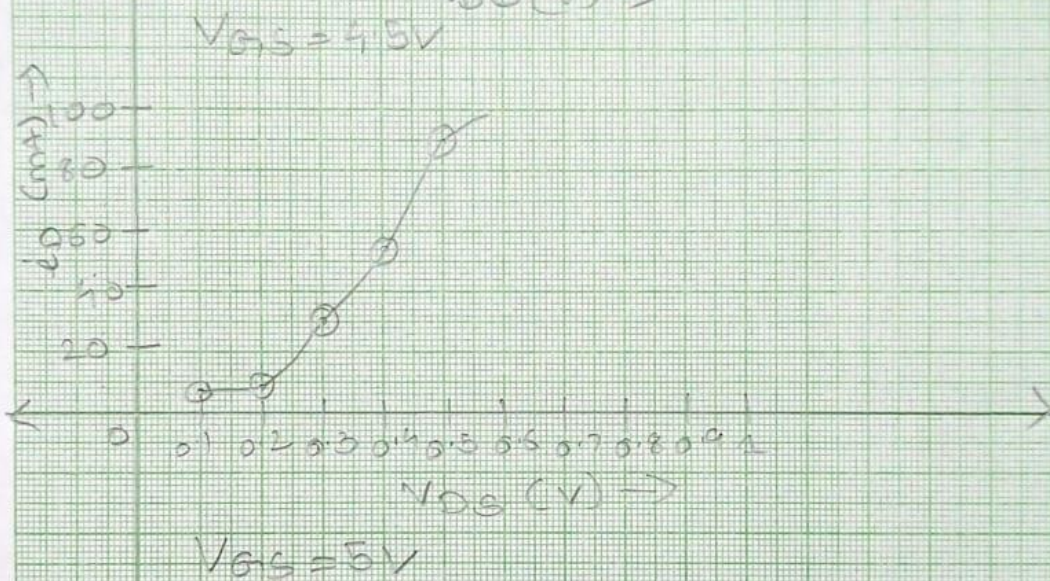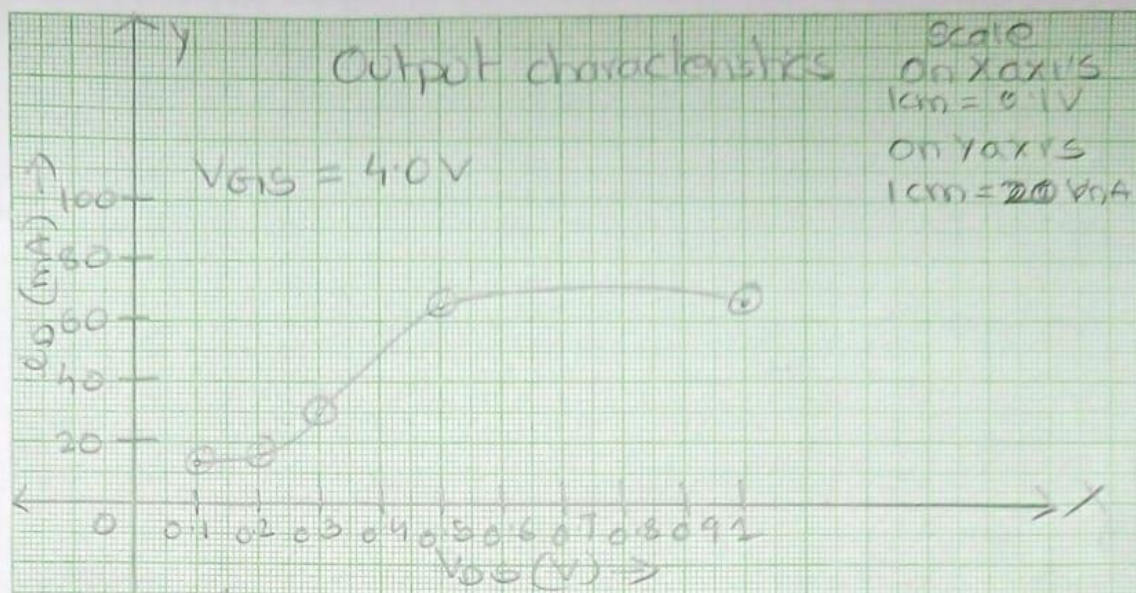



# IGBT I-V Characteristics

