

ECA Assignment

classmate

Date: 24/11/22

Page:

Name: Shreeveng Mhatre


Rollno: 29

Batch: A2

Sy-B.Tech Electrical & Computer Eng

SUB: ECA Assignment.

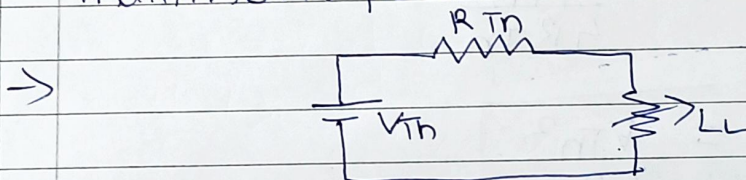- Q 1) Derive a proof of maximum power transfer theorem and hence derive formula for maximum power



$$P_L = I^2 R_L$$

$$\therefore I = \frac{V_{Th}}{R_{Th} + R_L} \quad (\text{by ohm's law})$$

$$\therefore P_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 \cdot R_L$$

$$\therefore P_L = V_{Th}^2 \left[\frac{R_L}{(R_{Th} + R_L)^2} \right] \quad \text{--- (1)}$$

diff wrt

$$\therefore \frac{dP_L}{dR_L} = V_{Th}^2 \left[\frac{(R_{Th} + R_L)^2 \times [-R_L \times 2(R_{Th} + R_L)]}{(R_{Th} + R_L)^4} \right] = 0$$

$$\Rightarrow (R_{Th} + R_L)^2 - 2R_L(R_{Th} + R_L) = 0$$

$$\Rightarrow (R_{Th} + R_L)(R_{Th} + R_L - 2R_L) = 0$$

$$\Rightarrow R_{Th} = R_L$$

→

∴ For max power

$$\boxed{R_L = R_{Th}}$$

Now. for formula.


$$P_{Lmax} = V_{Th}^2 \left\{ \frac{R_{Th}}{(R_{Th} + R_{Th})^2} \right\}$$

$$\Rightarrow P_{Lmax} = V_{Th}^2 \left[\frac{R_{Th}}{4 R_{Th}^2} \right]$$

$$\Rightarrow P_{Lmax} = \frac{V_{Th}^2}{4 R_{Th}}$$


$$\boxed{P_{Lmax} = \frac{V_{Th}^2}{4 R_L}}$$

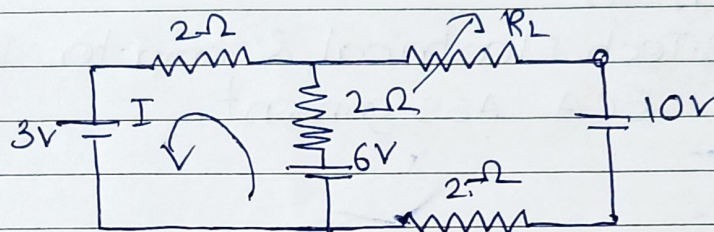- Q 2) Calculate value of R_L to transfer maximum power to it also calculate value of maximum power.




$$I = \frac{6-3}{4} = 0.75 A$$

by Thevenin's theorem

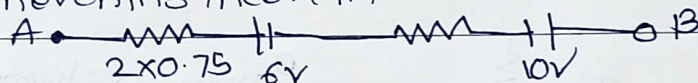
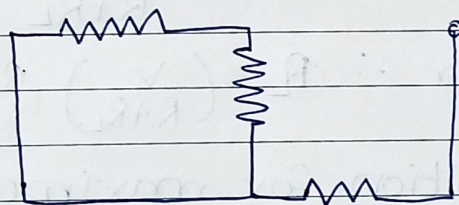
$$V_{Th} = (2 \times 0.75) + 10 - 6 = 5.5V$$



$$R_{eq} = (2/12) + 2 = 3\Omega$$


For maximum power $R_L = R_{eq}$

$$= \left[\frac{V_{Th}}{2R_{eq}} \right]^2 R_{eq} = \frac{5.5^2}{4 \times 3} = 2.52 W$$

$$\boxed{R_L = 3\Omega}$$

$$\boxed{P_{Lmax} = 2.52 W}$$

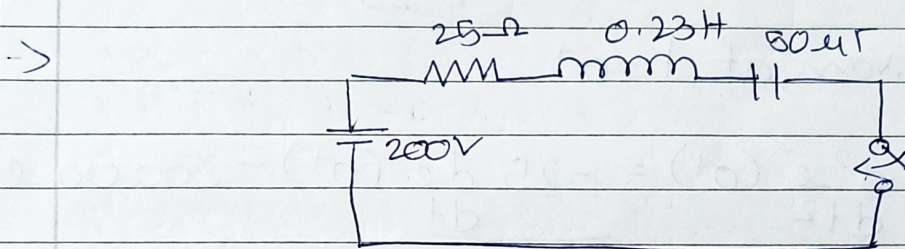- Q 3) In a circuit containing $R = 250 \Omega$, $L = 0.23 \text{ H}$ and $C = 50 \mu\text{F}$ in series with the voltage of 200 V , the switch is closed at $t = 0$. Calculate i' , di'/dt & d^2i'/dt^2 at $t = 0^+$.



At $t = 0^-$ no current flows through circuit

$$\therefore \boxed{i(0^+) = 0}$$

at $t > 0$: by KVL

$$\Rightarrow 200 - iR - L \frac{di}{dt} - \frac{1}{C} \int_0^t i(t) dt = 0$$

$$\Rightarrow 200 - 25i - 0.23 \frac{di}{dt} - \frac{10^6}{50} \int_0^t i(t) dt = 0$$

$$\Rightarrow 200 - 25i - 0.23 \frac{di}{dt} - 20000 \int_0^t i(t) dt = 0$$

$$\Rightarrow \frac{di}{dt} = \frac{200 - 25i - 20000 \int_0^t i(t) dt}{0.23} \quad \text{--- (1)}$$

Now,

$$\frac{di}{dt}(0^+) = \frac{200}{0.23} = 869.56 \text{ A/s}$$

$$\therefore \boxed{\frac{di}{dt}(0^+) = 869.56 \text{ A/s}}$$

→

~~Now~~ diff. eqn (1)

$$\frac{d^2 i'}{dt^2} = \frac{-25 \frac{di'}{dt} - 20000 i'}{0.23}$$

Now, at $t=0^+$

$$\frac{d^2 i'}{dt^2}(0^+) = \frac{-25 \frac{di'}{dt}(0^+) - 20000 i'(0^+)}{0.23}$$

$$= \frac{-25(869.56) - 20000(0)}{0.23}$$

$$\therefore \frac{d^2 i'}{dt^2} = \frac{-25(869.56)}{0.23}$$

$$\boxed{\frac{d^2 i'}{dt^2} = 94517 \text{ A/s}^2}$$