

F. Y. B. Tech Academic Year 2021-22

Trimester:II

Subject: Basics of Electrical and Electronics Engineering

Name -----

Division -----

Roll No -----

Batch -----

Experiment No: 8

Name of the Experiment: Finding Resonant Frequency of series R-L-C circuit

Performed on: -----

Submitted on: -----

Aim : Finding Resonant Frequency of series R-L-C circuit

Objective

To understand the resonance in series R-L-C circuit and to find out resonant frequency of given R-L-C circuit

Components and equipment required

Components	Specifications
Signal Generator	Audio frequency range
AC Ammeter	0-1 A
R-L-C circuit board	

Theory

In the series R-L-C circuit, when inductive reactance equals the capacitive reactance circuit is called as series resonance circuit. Circuit behaves like a resistive circuit and the resulting current is in phase with the applied voltage. Circuit power factor is unity. At resonance, the equivalent impedance of the circuit consists of only resistive components due to cancelling out the reactive components. At this condition circuit draws the maximum current shown in Fig.4 due to minimum impedance of the circuit as shown in Fig.3. As X_L is directly proportional to frequency and X_C is inversely proportional to frequency, we can obtain the resonance of any R-L-C circuit by varying its frequency.

The frequency, at which this condition occurs, is known as resonance frequency of that circuit. The magnitude of the resonating frequency can be calculated using eq.(1)

(1)

During series resonance, voltage magnification is observed. Voltage across the capacitor or inductor is multiple times the supply voltage. This can be observed using the term Q factor or Quality factor of the circuit which is given by eq. (2)

(2)

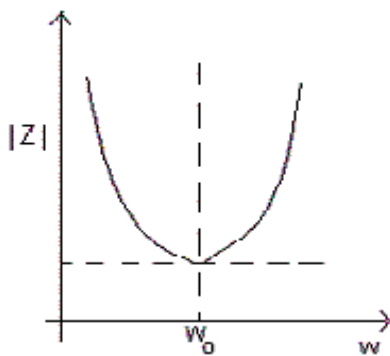


Fig.2: Impedance vs frequency

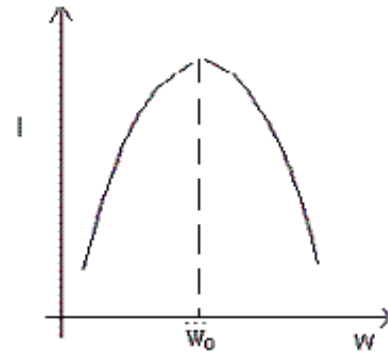


Fig.3: Current vs frequency

Procedure

- 1) Connect the circuit as shown in Fig.1
- 2) Give 10V peak to peak sinusoidal input at 100 Hz from the signal generator.
- 3) Change the frequency from 100 Hz To 1800 Hz and obtain the maximum current in the circuit. Note down this reading as resonant frequency.
- 4) Adjust frequencies for five equally spaced readings above and below the resonant frequency and note down corresponding current values.

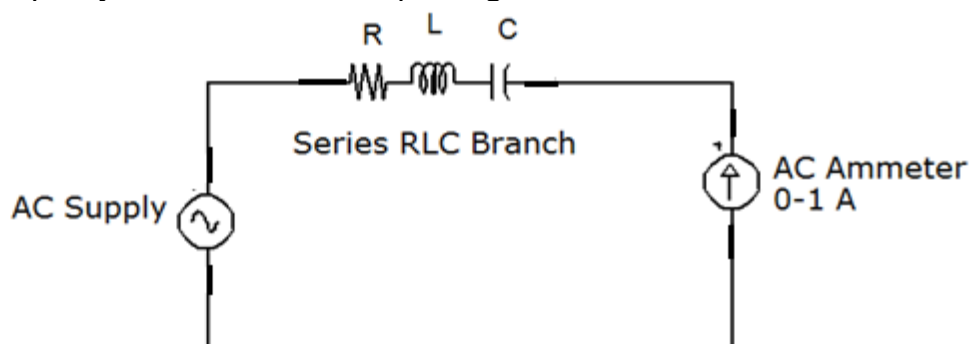


Fig. 4: Series R-L-C Circuit

Observations

1) Components used in the series circuit:

- i) 15 mH ii) 2 μ F iii) 30 Ω -----O4 Batch
ii) 10 mH ii) 1 μ F iii) 30 Ω -----O3 Batch

2) Observation Table : Resistance = 30 Ω

Sr. No	Frequency (Hz)	Voltage (V) across R (CRO Readings)	Current (mA) = Voltage V / 30 Ω
1	100 Hz		
2	200 Hz		
3	400 Hz		
4	600 Hz		
5	800 Hz		
6	900Hz		
7	950Hz		
8	1000 Hz		
9	1200 Hz		
10	1400 Hz		
9	1600 Hz		
10	1800 Hz		

Graph and Calculations

- 1) Plot graph of Current vs. Frequency
- 2) Mark resonant frequency from the graph.
- 3) Calculate resonant frequency using eq.(1).

Result

	Resonance Frequency (Hz)
Practical Value	
Theoretical Value	

Conclusion

Post-Lab Questions

- 1) Derive the expression for resonance frequency.
- 2) Explain the reactance curves (X_L vs ω and X_C vs ω) for series circuit.
- 3) Give applications of resonant circuits.

Note: Students are instructed to do all necessary calculations and answer the questions on separate sheets and attach them.

Applications of the Resonant RLC Circuits

- Oscillator **circuit**, radio receivers, and television sets are used for the tuning purpose.
- The series and **RLC circuit** mainly involves in signal processing and communication system.
- The Series resonant **LC circuit** is used to provide voltage magnification.



Dr. Vishwanath Karad

**MIT WORLD PEACE
UNIVERSITY | PUNE**

TECHNOLOGY, RESEARCH, SOCIAL INNOVATION & PARTNERSHIPS