

NAME: SHREERANG MHATRE
ROLLNO: 52
BATCH: A3

SCR CHARACTERISTICS

AIM: To study the characteristics of SCR.

APPARATUS: 1) Circuit board with SCR TYN614
2) 3½ & 4½ digit DMMs, ammeters & voltmeters.
3) Dual-trace CRO with probes.
4) 30V power supplies

THEORY:

The symbol and characteristics of a SCR are shown in Fig. 1,

CIRCUIT DESCRIPTION:

The circuit board is divided into two sections. The first section, shown in Fig. 4, is used for obtaining the V-I characteristics and latching & holding currents of the SCR

PROCEDURE:

1. V-I characteristics of SCR

- 1.1 Connect a DC ammeter, A1, in 100mA, between X3(+ve) & X4(-ve), in the anode circuit.
- 1.2 Set potentiometers R1(coarse adjustment), R2(media adjustment), & R3(fine adjustment) in the anode circuit to center position.
- 1.3 Connect a 4½ digit DMM, A2, in 20mA range, between X7(+ve) & X8(-ve), in the gate circuit.
- 1.4 Set potentiometers R5(coarse adjustment), R6(media adjustment), & R7(fine adjustment) in the gate circuit to center position.
- 1.5 Connect channel II(X) of the CRO between X9(live) and X11(common) to observe anode-cathode voltage v_{AK} .
- 1.6 Connect channel I(Y), **inverted**, of the CRO between X12(live) and X11(common) to observe a voltage $(i_A \times R_9)$ proportional to the anode current i_A .
- 1.7 Connect X13, SCR anode A1, to X9.
- 1.8 Connect X14, SCR gate G1, to X10.
- 1.9 Connect a DC supply, V_{GG} , in the gate circuit between X5(+ve) & X6(-ve). Set the DC supply voltage to 10V.

- 1.10 Connect a 32V AC supply, V_{AA} , in the anode circuit by connecting X17(16V) and X19(16V) on the transformer TR1 board to X1 and X2, respectively.
- 1.11 Using the X-Y mode of the CRO, observe the V-I characteristics of the SCR.
- 1.12 Adjust the gate current using V_{GG} , R5, R6 & R7 such that the forward breakover voltage V_{BO} is 40V. Measure the forward breakover current I_{BO} , reverse leakage current I_{BR} , on-state voltage V_T , and gate current I_G .
- 1.13 Sketch the V-I characteristics to **scale**.
- 1.14 Repeat step 1.12 for V_{BO} of 30V & 20V.
- 1.14 Switch-off all supplies and remove all connections on the circuit board **except** connections to the SCR anode and gate (steps 1.7 & 1.8).

2. Latching and holding currents of SCR

- 2.1 Connect a 4½ digit DMM, A1, in 20mA range, between X3(+ve) & X4(-ve), in the anode circuit.
- 2.2 Set potentiometers R1, R2 & R3 in the anode circuit to center position.
- 2.3 Short the gate circuit ammeter terminals X7 & X8.
- 2.4 Set potentiometers R5, R6 & R7 in the gate circuit to center position.
- 2.5 Connect channel II(X) of the CRO between X10(live) and X11(common) to observe gate-cathode voltage v_{GK} .
- 2.6 Connect channel I(Y), **inverted**, of the CRO between X12(live) and X11(common) to observe a voltage ($i_A \times R_9$) proportional to the anode current i_A .
- 2.7 Connect two DC supplies, in series, in the anode circuit, V_{AA} , between X1(+ve) & X2(-ve).
- 2.8 Connect a 16V AC supply, V_{GG} in the gate circuit by connecting X17(16V) and X18(0V) on the transformer TR1 board to X5 and X6, respectively.
- 2.9 Observe the v_{GK} & i_A waveforms on the CRO. Note that the i_A waveform is a square wave if the current is below the latching current I_L , while it is a DC value if it is above I_L .
- 2.10 Increase the anode current using V_{AA} , R1, R2 & R3 such that the anode current waveform **just** changes from a square wave to a DC value. Measure i_A which is now the **latching current**, I_L . Verify that the SCR is latched by removing the gate supply and checking that the SCR is still on.
- 2.11 With the gate supply removed, **slowly** reduce the anode current using current using V_{AA} , R1, R2 & R3 till the SCR **just** turns-off. Note the value of i_A at which this occurs, which is now the **holding current**, I_H .

2.12 Switch-off all supplies and remove all connections on the circuit board.

OBSERVATIONS:

1. V-I characteristics of SCR

Sr. No.	V_{BO} V	I_G mA	I_{BO} uA	I_{BR} uA	V_T V
1.	40				
2.	30				
3.	20				

2. Latching and holding currents of SCR

$$I_L = \quad \text{mA}, \quad I_L = \quad \text{mA}$$

CHARACTERISTICS & GRAPHS:

1. V-I characteristics of SCR to **scale** (step 1.13 of procedure).

CALCULATIONS: Calculate on-state resistance (reciprocal of slope in ohmic region), and output resistance (reciprocal of slope in active region) for each value of v_{GS} .

CONCLUSIONS:

LIST OF FIGURES:


Fig. 1

Thyristor (SCR) I-V characteristics


Fig. 2

Circuit for characteristics of SCR


Fig. 1 Thyristor (SCR) I-V Characteristics


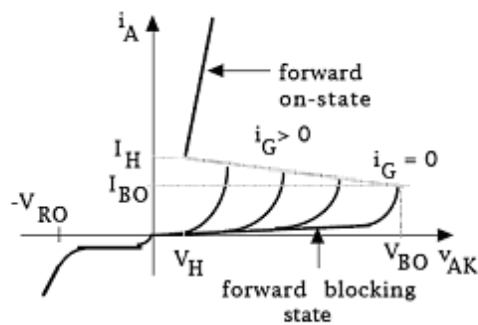


Thyristor circuit symbol.

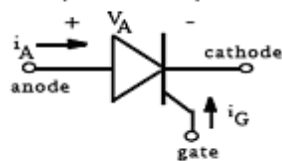

- SCR triggerable from forward blocking state to on-state by a gate current pulse.
- Thyristor latches on and gate cannot turn it off. External circuit must force SCR off.
- Current to several kiloamps for $V_{(on)}$ of 2-4 volts.
- Blocking voltages to 5-8 kilovolts.
- V_{BO} = breakover voltage ; I_{BO} = breakover current
- V_{RO} = **reverse** breakover voltage
- V_H = holding voltage I_H = holding current
- Maximum junction temperature = 125 C limited by temperature dependence of V_{BO} .

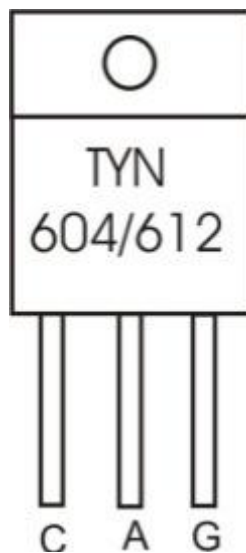

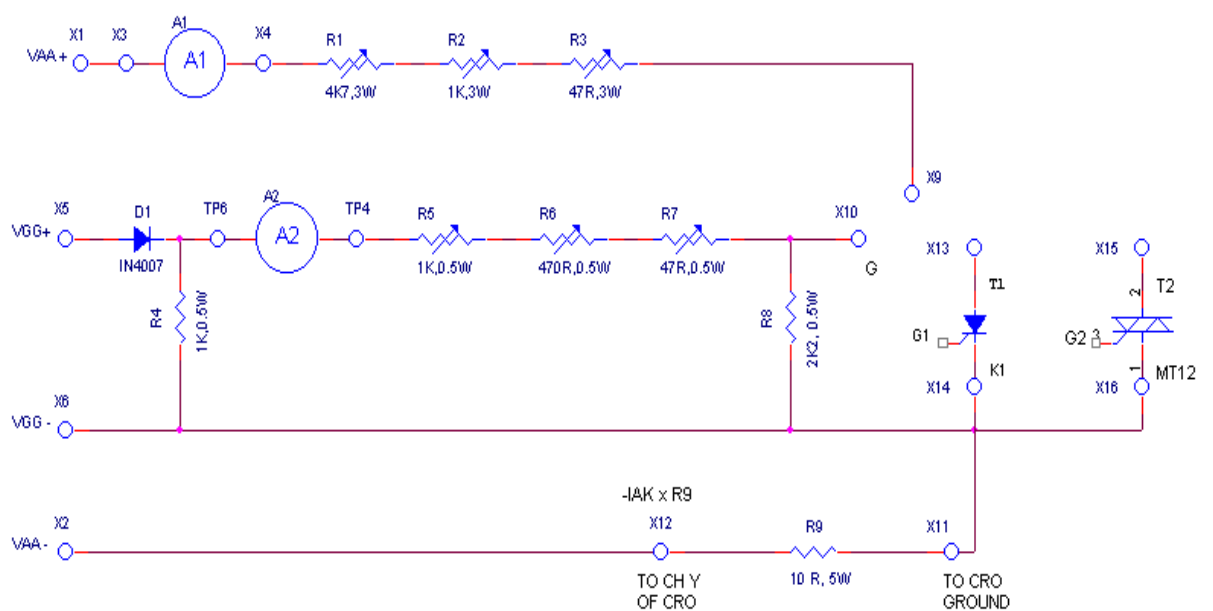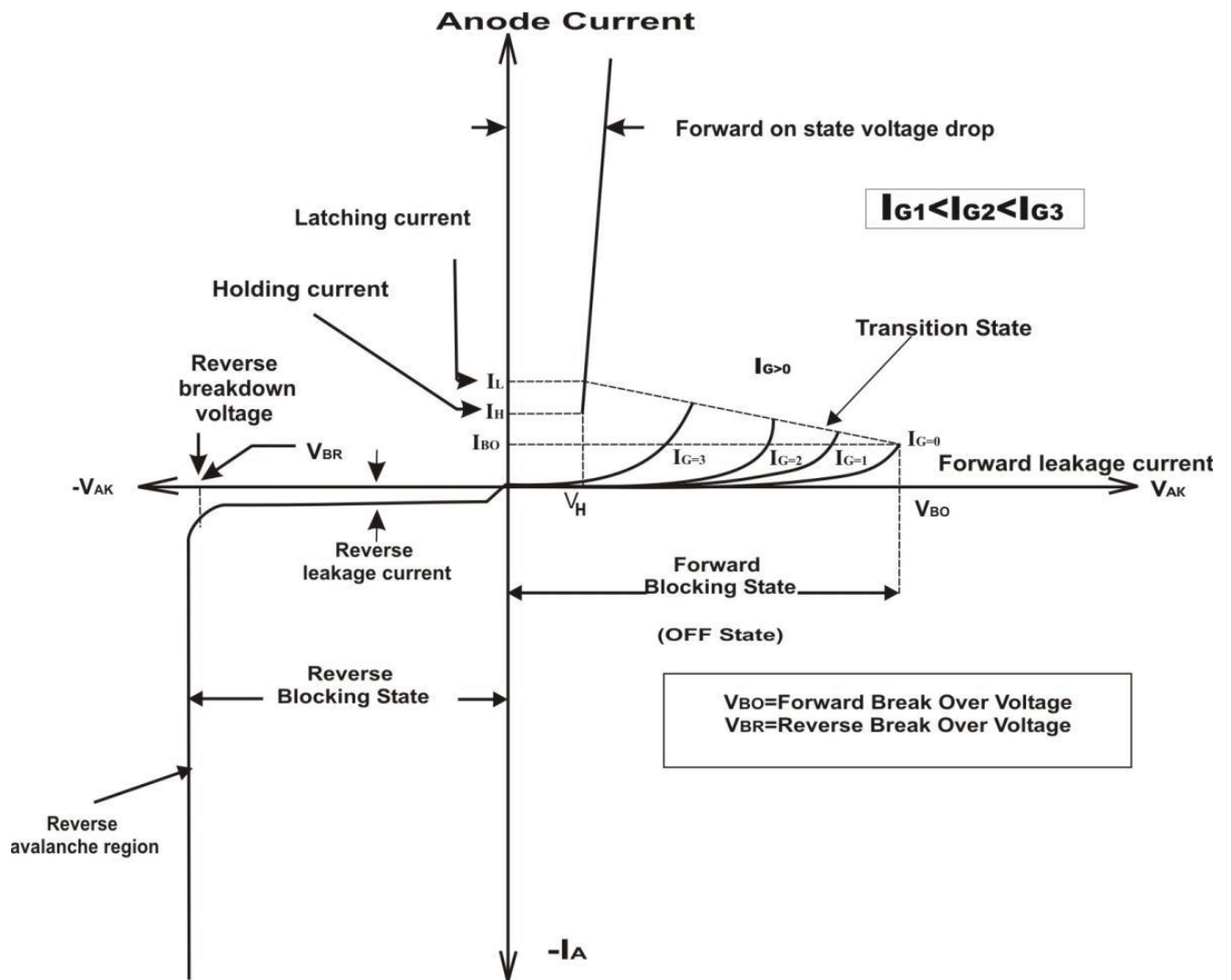

Exp-1 SCR

Name - Shreerang Mhatre

Rollno - 52

Batch - A3

AIM - To study the characteristics
of SCR

* Observations -

V-I characteristics of SCR

SrNo.	V_{BO} V	I_G mA	I_{BO} μA	I_{BR} μA	V_T V
1	40	4.74	20	-	7.2
2	30	4.76	15	-	7.2
3	20	4.79	10	-	6.8

V-I characteristics of SCR

